

Lecture 3.

Ohm's law (continued).

Grounding.

Electric power.

Terminal voltage vs EMF.

Last Time:

- Ohm's law

$$\Delta V_R = IR$$


- Kirchhoff's loop law

$$\sum_{\text{loop}} \Delta V = 0$$


- Sign conventions for voltage drops

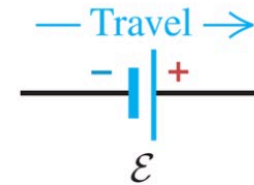(a) Sign conventions for emfs

$+\mathcal{E}$: Travel direction
from $-$ to $+$:




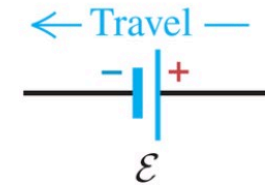$-\mathcal{E}$: Travel direction
from $+$ to $-$:




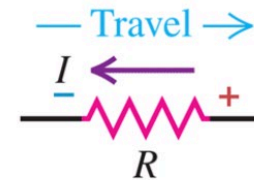(b) Sign conventions for resistors

$+IR$: Travel *opposite*
to current direction:



$-IR$: Travel *in*
current direction:

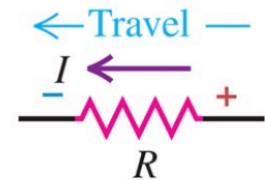


Simple DC Circuit with resistors.

In this circuit, $\varepsilon = 12\text{ V}$, $R_1 = 2\ \Omega$, and $R_2 = 3\ \Omega$.


- a) Calculate the current through R_1 .
- b) What is the current supplied by the battery?

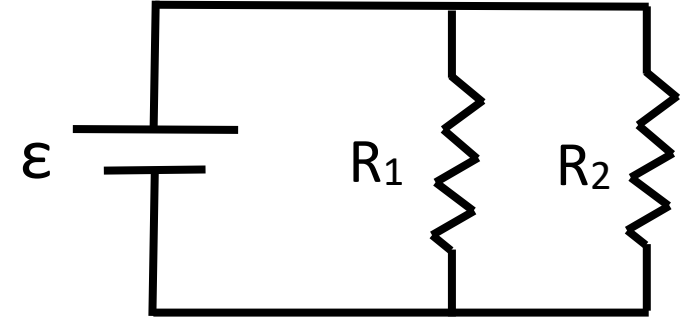- A. 2.4 A
- B. 4.0 A
- C. 6.0 A
- D. 8.0 A
- E. 10.0 A



Simple DC Circuit with resistors.

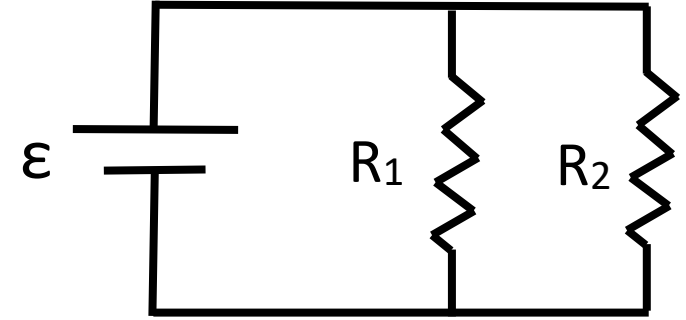In this circuit, $\varepsilon = 12\text{ V}$, $R_1 = 2\ \Omega$, and $R_2 = 3\ \Omega$.



- a) Calculate the current through R_1 .
- b) What is the current supplied by the battery?

A. 2.4 A • You can solve part b) using equivalent resistance:

B. 4.0 A

C. 6.0 A

D. 8.0 A

E. 10.0 A


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} \Rightarrow R_{eq} = \frac{R_1 R_2}{R_1 + R_2} = 1.2\ \Omega \quad \Rightarrow \quad I_{tot} = \frac{\varepsilon}{R_{eq}} = 10\text{ A}$$

- To answer part a), you need to figure out how this current splits between the two resistors – possible, but difficult and long! ☹

Simple DC Circuit with resistors.

In this circuit, $\varepsilon = 12\text{ V}$, $R_1 = 2\ \Omega$, and $R_2 = 3\ \Omega$.

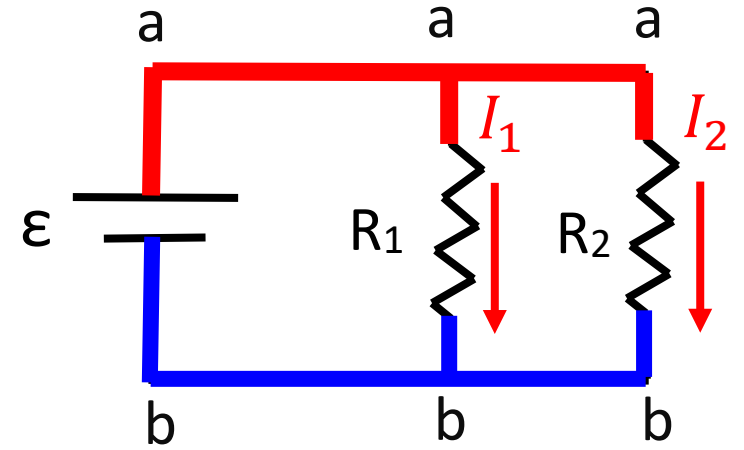- a) Calculate the current through R_1 .
- b) What is the current supplied by the battery?



- A. 2.4 A
- B. 4.0 A
- C. 6.0 A
- D. 8.0 A
- E. 10.0 A

- All three components are under the same voltage
(same voltage at all points of an ideal wire!)


$$I_1 = \frac{\varepsilon}{R_1} = 6\text{ A}$$

$$I_2 = \frac{\varepsilon}{R_2} = 4\text{ A}$$

$$I_{tot} = I_1 + I_2 = 10\text{ A}$$


How current splits?

- Common misconceptions.

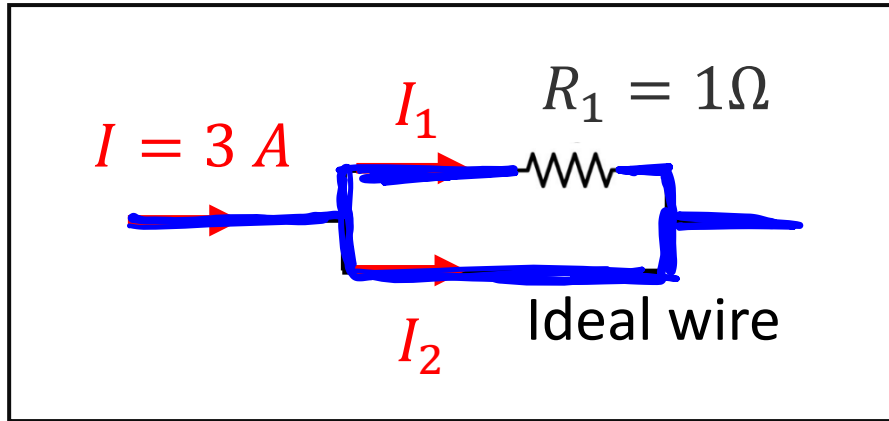

Compare:
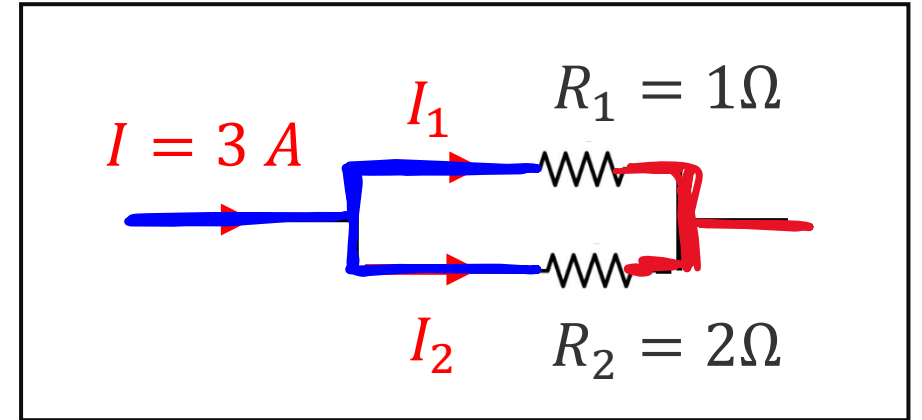
$$I_{R_1} = \frac{\Delta V_{R_1}}{R_1} = 0$$



Find currents I_1 and I_2 .

- A. $I_1 = 0$, $I_2 = 3\text{ A}$
- B. $I_1 = 1\text{ A}$, $I_2 = 2\text{ A}$
- C. $I_1 = 2\text{ A}$, $I_2 = 1\text{ A}$
- D. $I_1 = 3\text{ A}$, $I_2 = 0$
- E. Splits evenly (1.5 A each)


$$\begin{aligned} \text{i)} \quad & I_1 + I_2 = 3\text{ A} \\ & \Delta V_{\text{comb}} = I_1 R_1 = I_2 R_2 \end{aligned}$$

Find currents I_1 and I_2 .

- A. $I_1 = 0$, $I_2 = 3\text{ A}$
- B. $I_1 = 1\text{ A}$, $I_2 = 2\text{ A}$
- C. $I_1 = 2\text{ A}$, $I_2 = 1\text{ A}$
- D. $I_1 = 3\text{ A}$, $I_2 = 0$
- E. Splits evenly (1.5 A each)

How current splits?

- Common misconceptions.

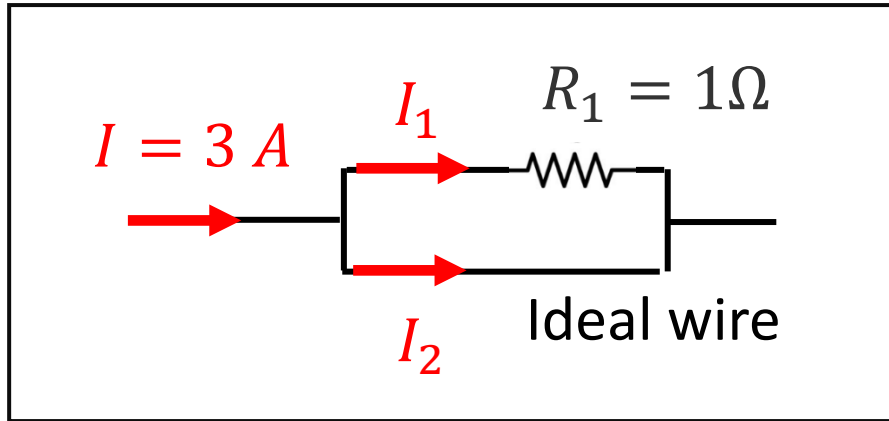

$$\Delta V_{R1} = \Delta V_{\text{wire}} \text{ (in parallel)}$$


$$\Delta V_{\text{wire}} = 0 \text{ (ideal wire!)} \Rightarrow \Delta V_{R1} = 0$$

$$I_1 = \frac{\Delta V_{R1}}{R_1} = \frac{0\text{ V}}{1\Omega} = 0$$

$$I_2 = I = 3\text{ A}$$

All current goes into the ideal wire!

Compare:

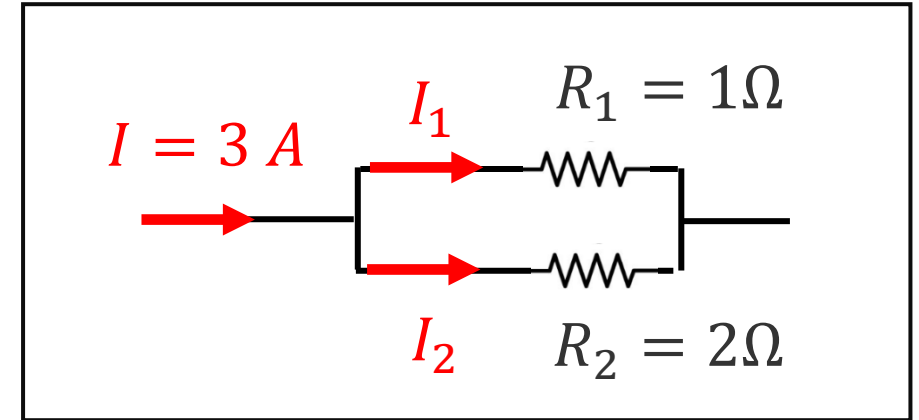

$$\Delta V_{R1} = \Delta V_{R2} \text{ (in parallel)}$$


$$R_{eq} = \frac{1 \cdot 2}{1 + 2} = \frac{2}{3}\Omega \Rightarrow \Delta V_{1,2} = IR_{eq} = 2\text{ V}$$

$$I_1 = \frac{\Delta V_{R1}}{R_1} = \frac{2\text{ V}}{1\Omega} = 2\text{ A}$$

$$I_2 = \frac{\Delta V_{R2}}{R_2} = \frac{2\text{ V}}{2\Omega} = 1\text{ A}$$

Current splits inversely proportional to R !


Grounding

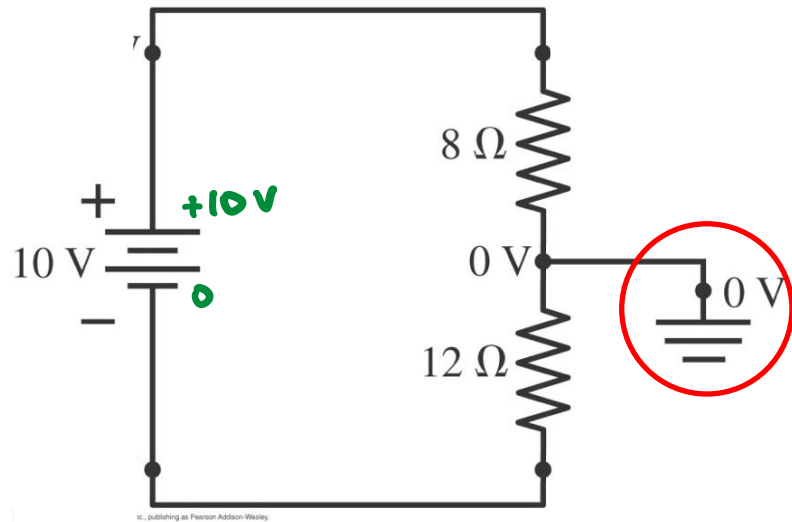

- **Grounding the circuit** does not change any of the currents, but it does allow us to define **specific values for the voltage** at each point in the circuit.
 - This allows us to **join different circuits together**, without any unexpected currents between them.
-
- **Spoiler:** grounding simply means connecting a point at your circuit to a big conductor (it can be Earth, but not necessarily). Later we will learn that the whole conductor always stays under the same “electric potential” => it has the same voltage everywhere, and this voltage is imposed onto the wires touching it.

Q: a) Find the current at each corner in the circuit.

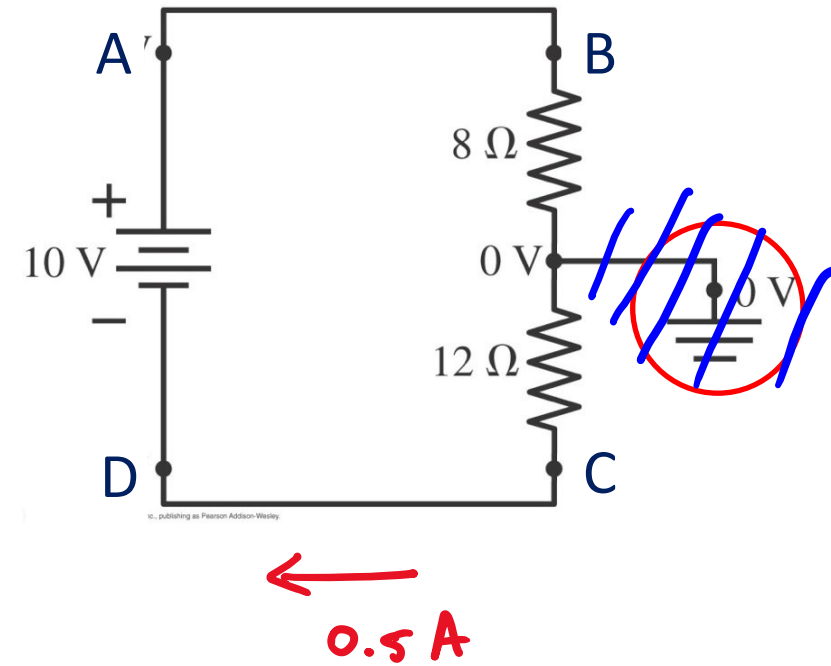- A. $I_A = 1.25\text{ A}$, $I_B = 1.25\text{ A}$, $I_C = 0.83\text{ A}$, $I_D = 0.83\text{ A}$
- B. $I_A = 1.25\text{ A}$, $I_B = 1.25\text{ A}$, $I_C = 1.25\text{ A}$, $I_D = 1.25\text{ A}$
- C. $I_A = 0.5\text{ A}$, $I_B = 0.5\text{ A}$, $I_C = 0.5\text{ A}$, $I_D = 0$
- D. $I_A = 0.83\text{ A}$, $I_B = 0.83\text{ A}$, $I_C = 0.83\text{ A}$, $I_D = 0.83\text{ A}$
- E. $I_A = 0.5\text{ A}$, $I_B = 0.5\text{ A}$, $I_C = 0.5\text{ A}$, $I_D = 0.5\text{ A}$



Q: a) Find the current at each corner in the circuit.


A. $I_A = 1.25\text{ A}$, $I_B = 1.25\text{ A}$, $I_C = 0.83\text{ A}$, $I_D = 0.83\text{ A}$

B. $I_A = 1.25\text{ A}$, $I_B = 1.25\text{ A}$, $I_C = 1.25\text{ A}$, $I_D = 1.25\text{ A}$

C. $I_A = 0.5\text{ A}$, $I_B = 0.5\text{ A}$, $I_C = 0.5\text{ A}$, $I_D = 0$

D. $I_A = 0.83\text{ A}$, $I_B = 0.83\text{ A}$, $I_C = 0.83\text{ A}$, $I_D = 0.83\text{ A}$

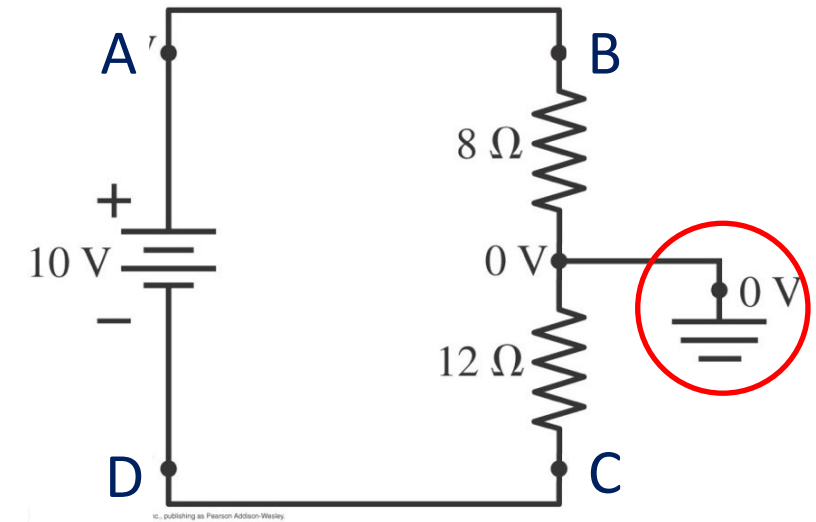E. $I_A = 0.5\text{ A}$, $I_B = 0.5\text{ A}$, $I_C = 0.5\text{ A}$, $I_D = 0.5\text{ A}$




Circuit: two resistors in series

$$R_{eq} = R_{8\Omega} + R_{12\Omega} = 20\ \Omega$$

$$I_{tot} = \frac{V}{R_{eq}} = \frac{10\text{ V}}{20\ \Omega} = 0.5\text{ A}; \quad I_{tot} = I_A = I_B = I_C = I_D$$

Q: b) Find the voltage at each corner in the circuit.

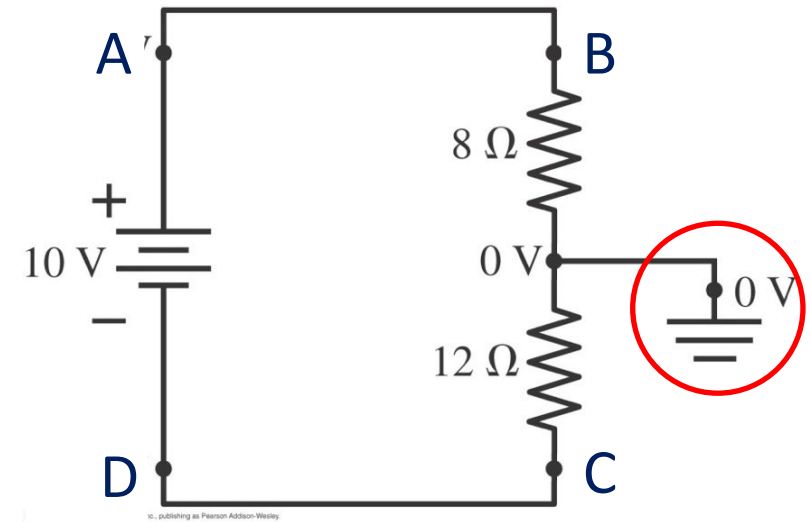- A. $V_A = 10\text{ V}$, $V_B = 10\text{ V}$, $V_C = 0$, $V_D = 0$
- B. $V_A = 10\text{ V}$, $V_B = 6\text{ V}$, $V_C = 4\text{ V}$, $V_D = 0\text{ V}$
- C. $V_A = 4\text{ V}$, $V_B = 4\text{ V}$, $V_C = 6\text{ V}$, $V_D = 6\text{ V}$
- D. $V_A = 4\text{ V}$, $V_B = 4\text{ V}$, $V_C = -6\text{ V}$, $V_D = -6\text{ V}$
- E. Something else




Q: b) Find the voltage at each corner in the circuit.

- A. $V_A = 10\text{ V}$, $V_B = 10\text{ V}$, $V_C = 0$, $V_D = 0$
- B. $V_A = 10\text{ V}$, $V_B = 6\text{ V}$, $V_C = 4\text{ V}$, $V_D = 0\text{ A}$
- C. $V_A = 4\text{ V}$, $V_B = 4\text{ V}$, $V_C = 6\text{ V}$, $V_D = 6\text{ V}$
- D. $V_A = 4\text{ V}$, $V_B = 4\text{ V}$, $V_C = -6\text{ V}$, $V_D = -6\text{ V}$**
- E. Something else

$$V_P - V_B = -0.5 \cdot 8 = -4$$

$$\Delta V_{8\Omega} = ?$$

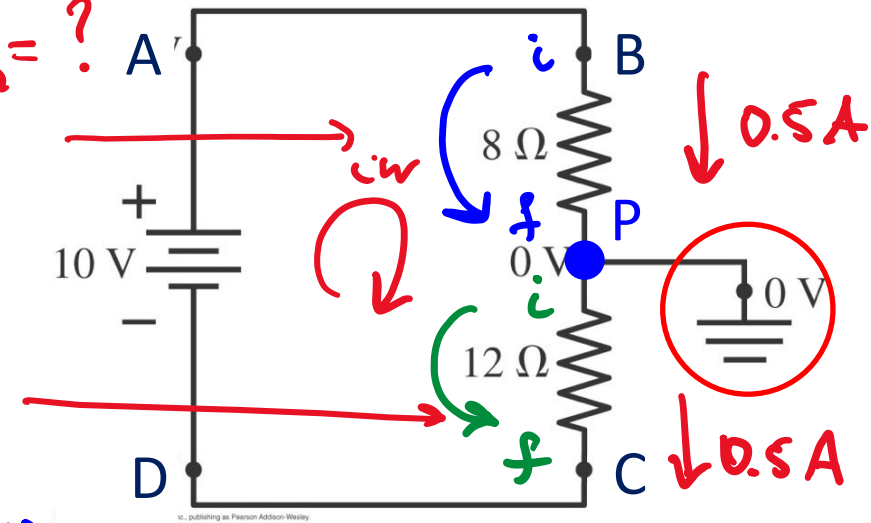

$$V_C - V_P = \Delta V_{12\Omega} = \dots$$

$$-0.5 \cdot 12 = -6 = V_C - V_P$$

1) $V_A = V_B$ and $V_C = V_D$ (these pairs belong to same ideal wire)

$$2) \Delta V_{8\Omega} = V_P - V_B = -IR_{8\Omega} = -0.5 \cdot 8 = -4\text{ V} \Rightarrow V_B = 4\text{ V}$$

$$\Delta V_{12\Omega} = V_C - V_P = -IR_{12\Omega} = -0.5 \cdot 12 = -6\text{ V} \Rightarrow V_C = -6\text{ V}$$

$$\Delta V = V_f - V_i$$

Electric power dissipated by a resistor


$$P = \frac{\Delta U}{\Delta t} = \frac{\text{Energy}}{\text{time}}$$

- Power: amount of energy dissipated by a resistor per unit time.

$$P_R = I\Delta V_R = I^2 R = \frac{(\Delta V_R)^2}{R}$$

- These three forms are equivalent, since $\Delta V_R = IR$

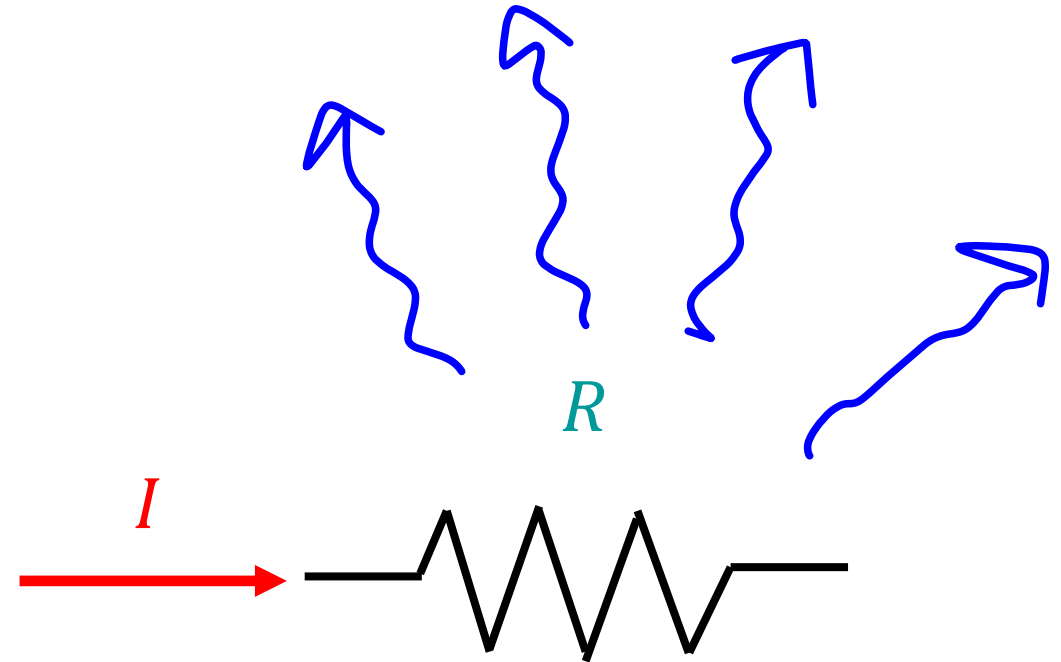- Light bulb: **brightness** = dissipated power



Q: Bulbs a, b, and c are identical, and are all glowing.

Suppose an additional wire is now connected between point 1 and point 2. What happens to each bulb? Does it get brighter, dimmer, stay the same, or go out?

A. $a = \uparrow, b = \uparrow, c = \downarrow$ (brighter = \uparrow , dimmer = \downarrow)

B. $a = \downarrow, b = \downarrow, c = \text{out}$

C. $a = \uparrow, b = \text{out}, c = \text{out}$

D. $a = \downarrow, b = \text{out}, c = \downarrow$


E. $a = \downarrow, b = \text{out}, c = \text{out}$

$$P_A = I_{\text{tot}}^2 \cdot R$$

$$\text{Before: } R_{\text{eq}} = R + \frac{R}{2} = \frac{3R}{2}$$

$$\text{After: } R_{\text{eq}} = R$$
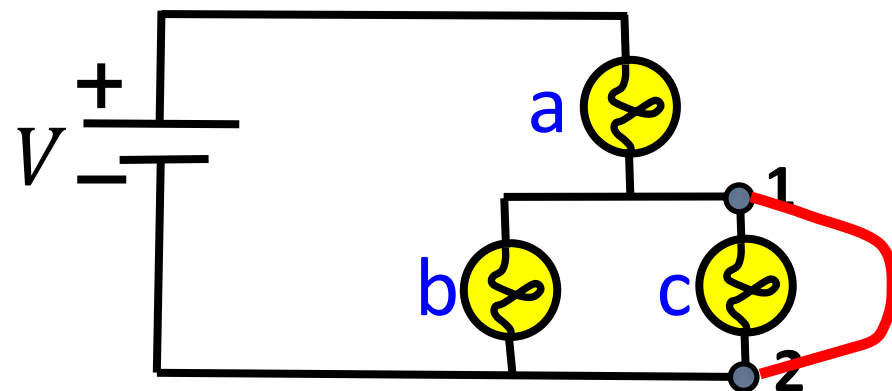
$$R_{\text{eq}} \downarrow \rightarrow I_{\text{tot}} \uparrow$$



Q: Bulbs a, b, and c are identical, and are all glowing.

Suppose an additional wire is now connected between point 1 and point 2. What happens to each bulb? Does it get brighter, dimmer, stay the same, or go out?

A. $a = \uparrow, b = \uparrow, c = \downarrow$ (brighter = \uparrow , dimmer = \downarrow)

B. $a = \downarrow, b = \downarrow, c = \text{out}$

C. $a = \uparrow, b = \text{out}, c = \text{out}$

D. $a = \downarrow, b = \text{out}, c = \downarrow$


E. $a = \downarrow, b = \text{out}, c = \text{out}$

This wire is assumed to be ideal \Rightarrow same potential along the whole wire $\Rightarrow \Delta V_{12} = 0 \Rightarrow I_b = \frac{\Delta V_{12}}{R_B} = 0$, and $I_c = \frac{\Delta V_{12}}{R_C} = 0$, so both of these bulbs **go out** (all current now goes through the wire).

• Without wire: $R_{eq} = R_a + R_{bc}$.

• With the wire: $R_{eq} = R_a \Rightarrow$

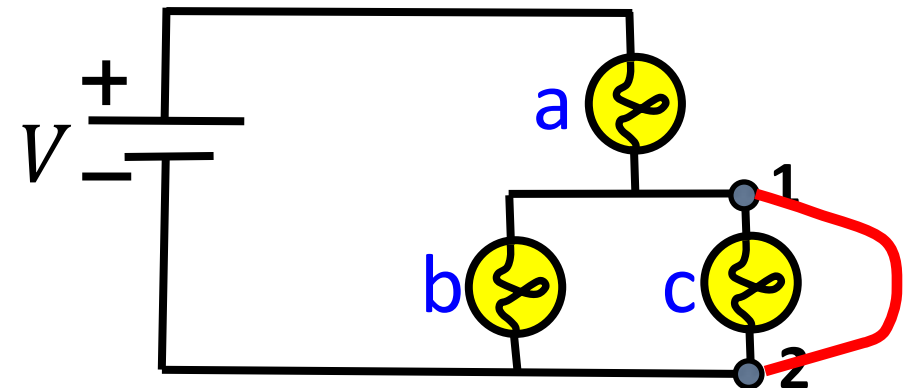$R_{eq} \downarrow \Rightarrow I_{tot} \uparrow$. The current through bulb a increases (since it receives I_{tot}) \Rightarrow **bulb a gets brighter.**





Q: a) What happens to the brightness of bulb 1, when bulb 2 burns out? Bulb 1 gets:

- A. Dimmer
- B. Brighter
- C. Stays the same
- D. Goes out
- E. Need to know R

$R_{eq} \uparrow \rightarrow I_{tot} \downarrow \rightarrow \text{Dimmer}$

OK


b) What happens to bulb 3?

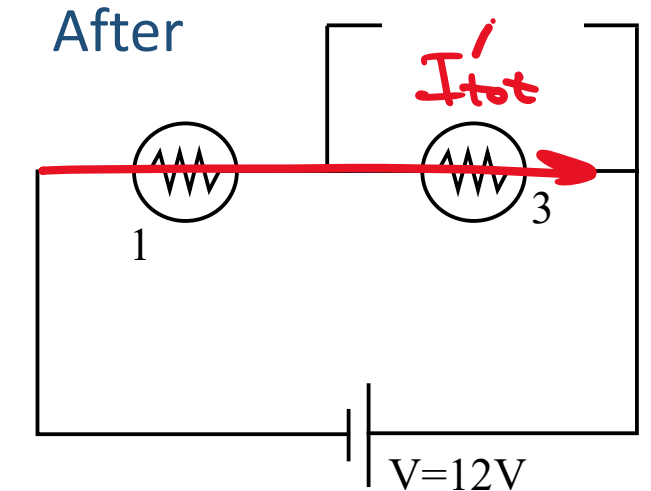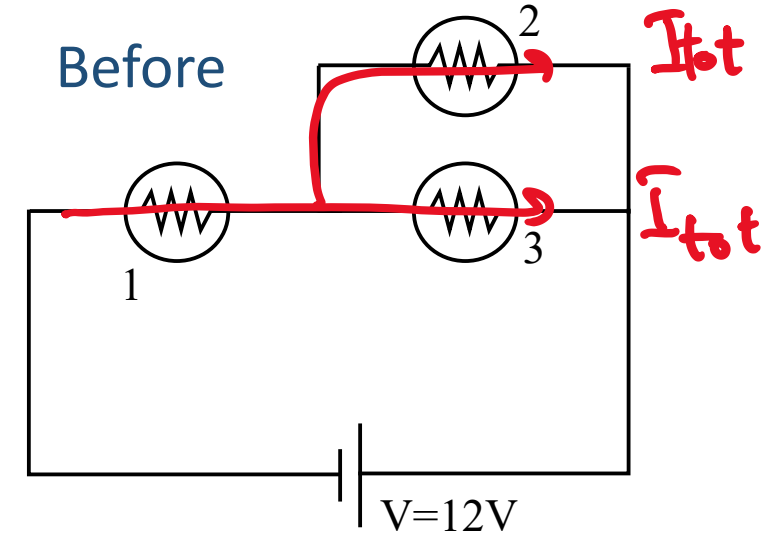

Q: a) What happens to the brightness of bulb 1, when bulb 2 burns out?


b) What happens to bulb 3?

$$P_R = I^2 R$$

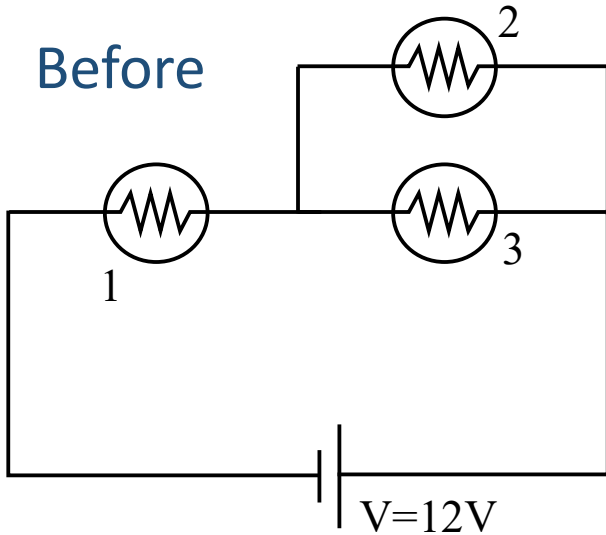

$$R_{eq} = R + \frac{R \cdot R}{R + R} = \frac{3R}{2}$$
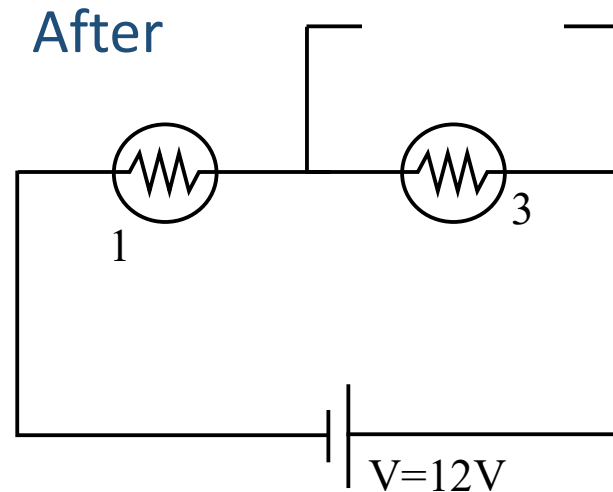
$$I_{tot} = \frac{V}{R_{eq}} = \frac{2V}{3R} = I_1; \quad I_2 = I_3 = \frac{I_1}{2} = \frac{V}{3R}$$



$$R'_{eq} = R + R = 2R$$

$$I'_{tot} = \frac{V}{R'_{eq}} = \frac{V}{2R} = I'_1 = I'_3$$

Compare ($P_R = I_R^2 R$):

- $I_2 \downarrow \Rightarrow P_2 \downarrow$: off
- $I_1 \downarrow \Rightarrow P_1 \downarrow$: dimmer
- $I_3 \uparrow \Rightarrow P_3 \uparrow$: brighter


Real batteries

- Battery produces **electromotive force** (emf): ε (from chemical reaction)
- But: user gets **terminal voltage**: ΔV_{bat}
 - Ideal battery: $\varepsilon = \Delta V_{bat}$
 - Real battery: $\varepsilon > \Delta V_{bat}$ (runs hot while you use it)
 - Losses can be modelled by an “**internal resistance**”, r
- What is the terminal voltage for a circuit with emf ε , internal resistance r and an external load R ?


$$\Delta V_{bat} = \varepsilon - Ir \qquad I = \frac{\varepsilon}{R_{eq}} = \frac{\varepsilon}{R + r}$$

$$\Delta V_{bat} = \varepsilon - \frac{\varepsilon}{R + r} r = \frac{R}{R + r} \varepsilon$$

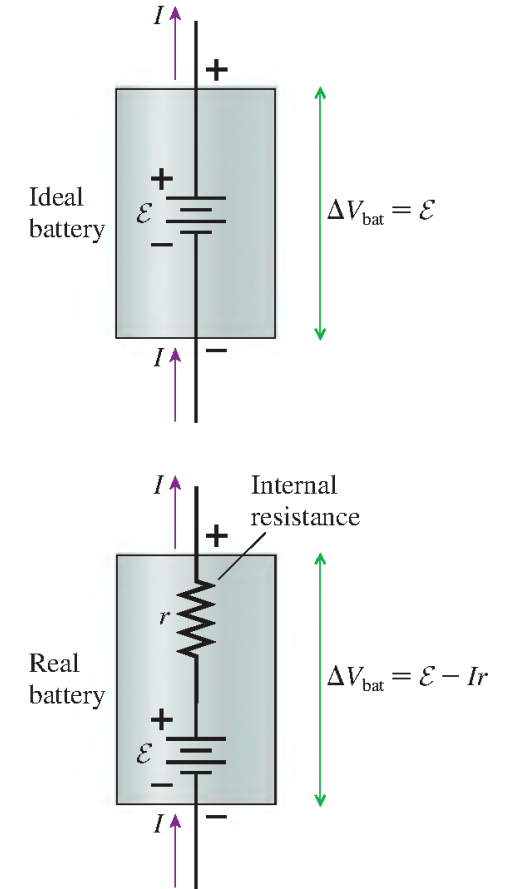- Terminal voltage depends on the external load!







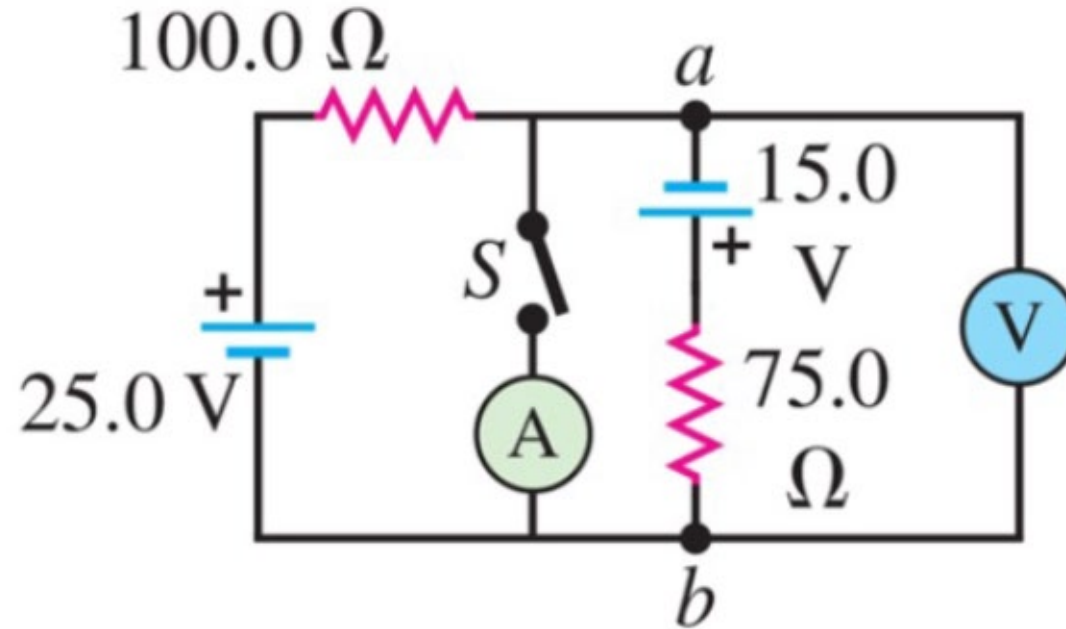
Electrical measuring instruments: Ch 26.3 (on your own)



- Ammeter \textcircled{A} measures current (in series)
- Voltmeter \textcircled{V} measures voltage drop (in parallel)

Q: You arrive in the lab and you find a 12 V battery, a 10 μF capacitor, and two resistors wired together as shown on the right. In order to correctly analyze the circuit response, you should **redraw the circuit yourself (on paper)**.

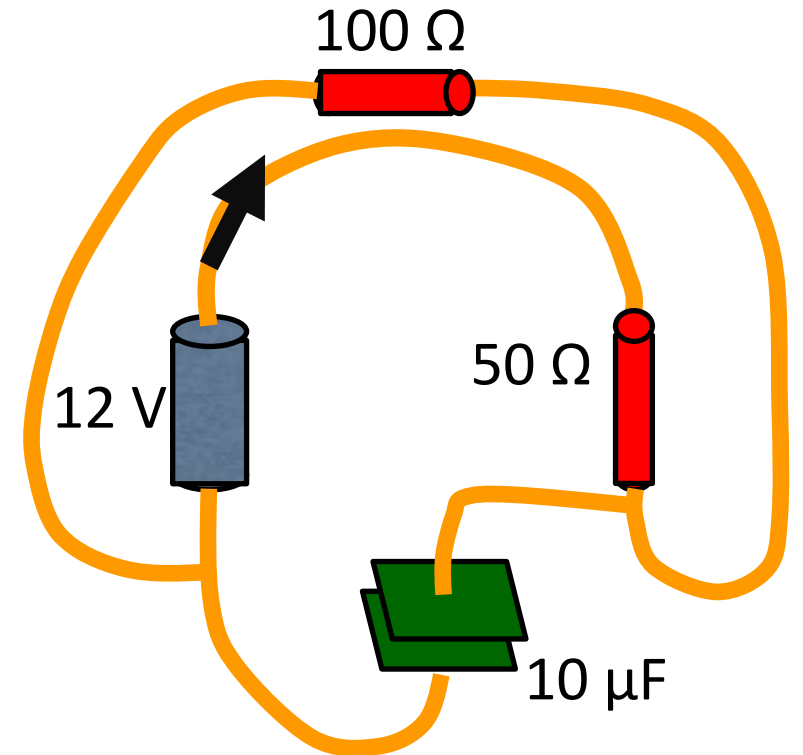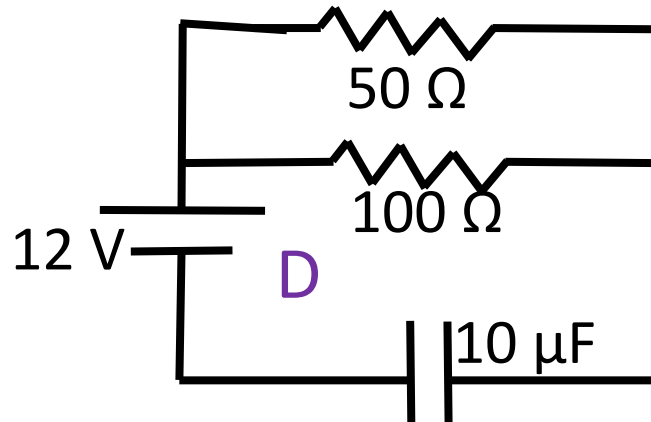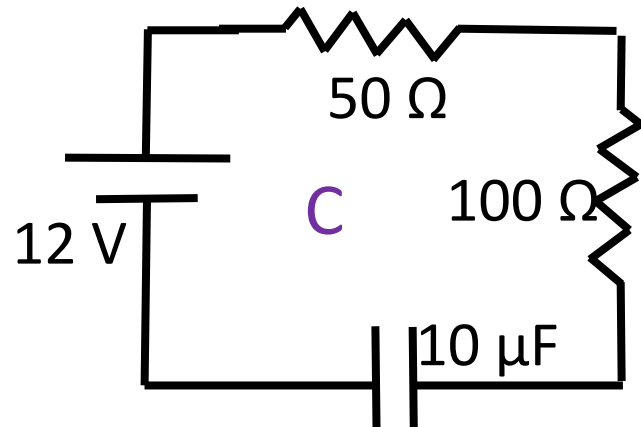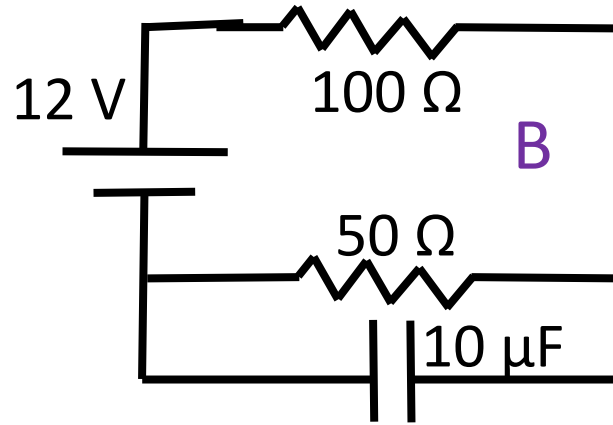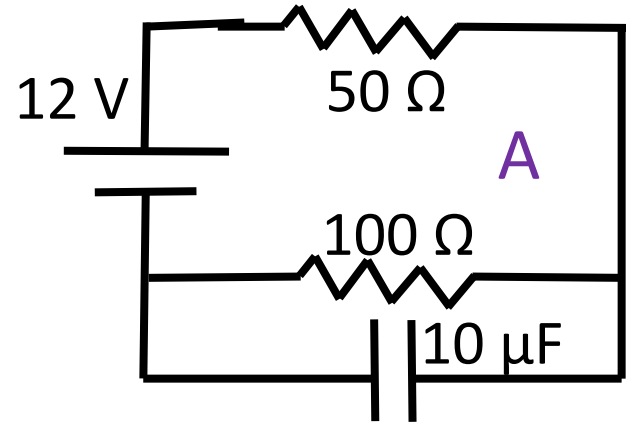Which circuit diagram below is the correct one?



Q: You arrive in the lab and you find a 12 V battery, a 10 μF capacitor, and two resistors wired together as shown on the right. In order to correctly analyze the circuit response, you should **redraw the circuit yourself (on paper)**.

Which circuit diagram below is the correct one?

