
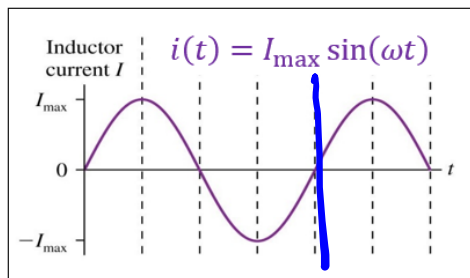
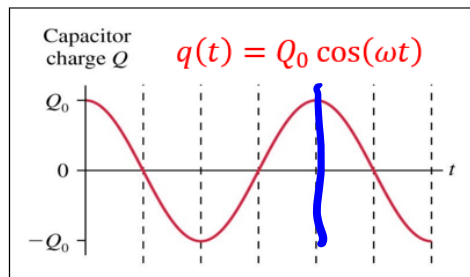


Announcements:

- Next Monday: 8:00 am class will have a midterm. Please wait in the lobby till ~8:55 (please wait until the TAs will open the doors and let you in)
- Recordings: S201, S202 will be recorded since next Monday
 - Posted: on Fridays
 - Please use them wisely! Recordings bring more harm than benefit if:
 - ❖ Recordings replace live lectures
 - ❖ When you start thinking: “I did not understand it today, but it’s okay, I’ll watch the recording some time later”
 - ❖ Please check [this information](#). Your decisions should be informed.

Lecture 9.

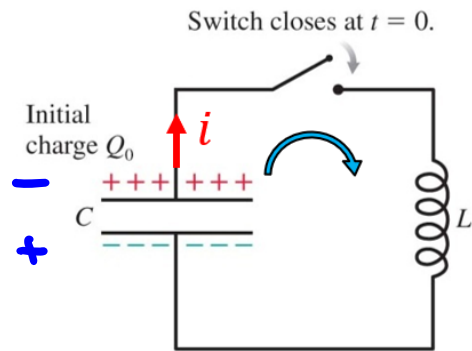LC circuits and LCR circuits.
Energy in LC and LCR circuits.



$$U_C(t) = \frac{q(t)^2}{2C}$$

$$U_L(t) = \frac{L i(t)^2}{2}$$

$$+ \frac{q(t)}{C} + L \frac{d^2 q(t)}{dt^2} = 0$$


• Solution:

$$q(t) = Q_0 \cos(\omega t)$$


$\omega = \frac{1}{\sqrt{LC}}$ Last Time:

$\frac{Q_0}{\sqrt{LC}} = I_0$



$$i(t) = Q_0 \omega \sin(\omega t)$$

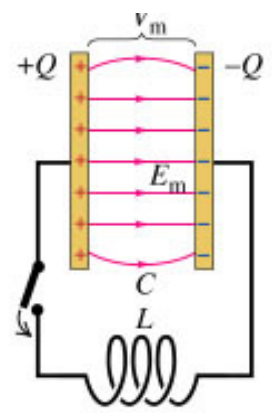

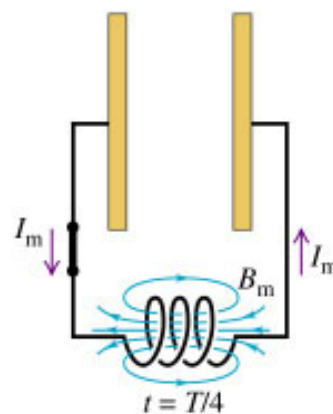
$t = 0$ and $t = T$
(close switch at $t = 0$)




$t = T/4$

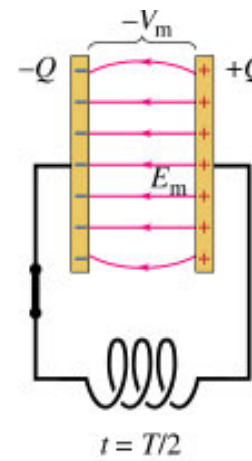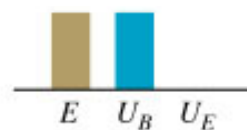

$t = T/2$

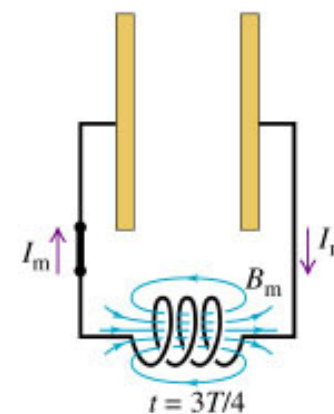

$t = 3T/4$

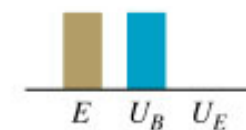

You're asked to build an LC circuit that oscillates at ~ 10 kHz. In addition, the maximum current must be 0.1 A and the maximum energy stored in the capacitor must be 10^{-5} J. What values of inductance and capacitance must you use? (Pick the closest answer)

- A. 0.2 mH and 0.1 μ F
- B. 2 mH and 0.1 μ F
- C. 2 mH and 1 μ F
- D. 20 mH and 1 μ F
- E. 20 mH and 10 μ F

You're asked to build an LC circuit that oscillates at ~ 10 kHz. In addition, the maximum current must be 0.1 A and the maximum energy stored in the capacitor must be 10^{-5} J. What values of inductance and capacitance must you use? (Pick the closest answer)

A. 0.2 mH and 0.1 μ F

☒ B. 2 mH and 0.1 μ F

C. 2 mH and 1 μ F

D. 20 mH and 1 μ F

E. 20 mH and 10 μ F

• Relevant equations:

$$\omega = \frac{1}{\sqrt{LC}} = 2\pi f \quad U_{L-C} = \frac{LI_{\max}^2}{2} = \frac{Q_0^2}{2C} \quad I_{\max} = \frac{Q_0}{\sqrt{LC}}$$

• $L = 2 \text{ mH}$ & $C = 0.1 \text{ }\mu\text{F}$ give:




$$\omega = \frac{1}{\sqrt{LC}} = 71,000 \frac{\text{rad}}{\text{s}} \quad \& \quad f = \frac{\omega}{2\pi} = 11.25 \text{ kHz} - \text{the closest to } 10 \text{ kHz.}$$

• If we use $L = 2 \text{ mH}$ and $I_{\max} = 0.1 \text{ A}$:


the energy is equal to $10^{-5} \text{ J} \Rightarrow$ it works!

• Note that I_{\max} (and hence U_{L-C}) are determined by the initial charge on the capacitor \Rightarrow you might need to think about how to restrict it, to not exceed maximum values

Application: Radio Receiver/Transmitter

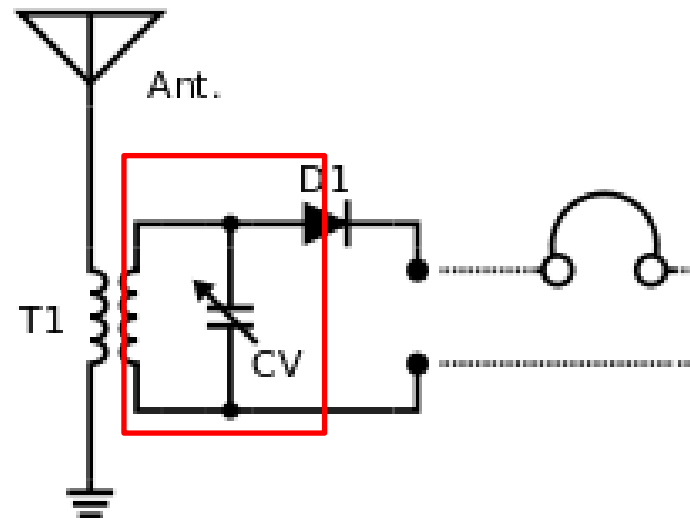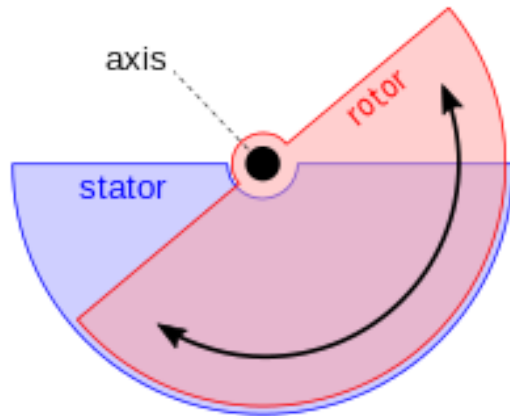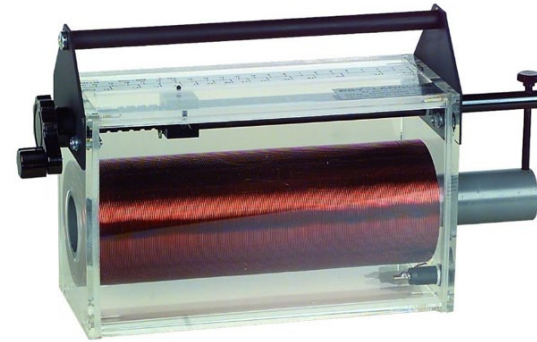

RLC circuits

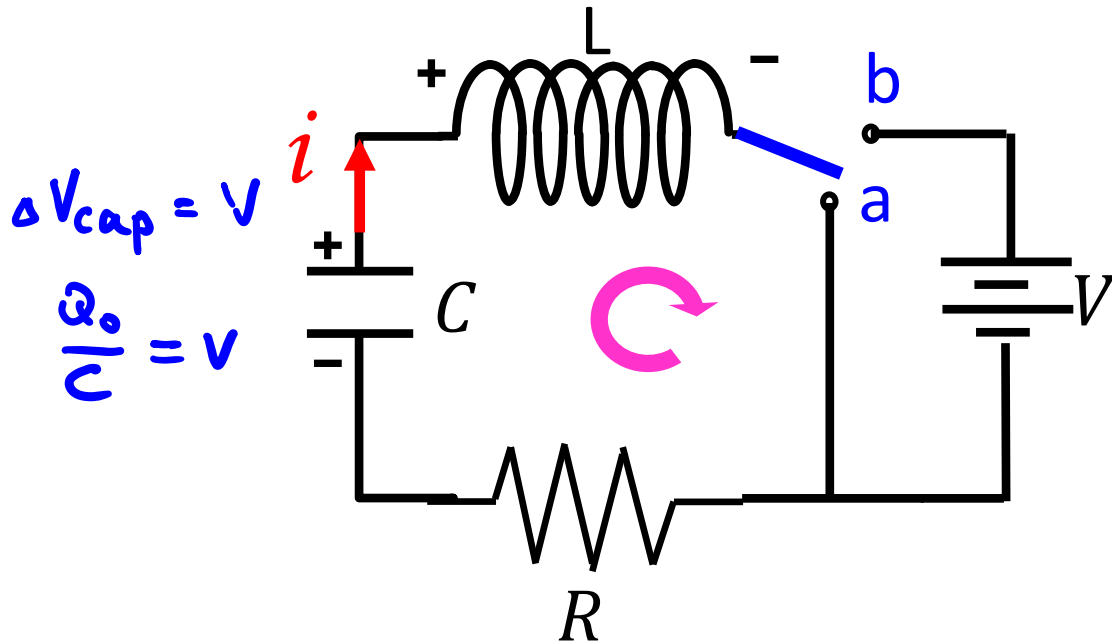

- Suppose $q(0) = Q_0$ and $i_0 = 0$ (switch connected to **b** for a long time)
- Then we move the switch from position **“b”** to **“a”** and discharge the capacitor (CW).

- Using Kirchhoff's loop voltage rule:

$$+\frac{q}{C} - L \frac{di}{dt} - Ri = 0$$

- Next, $i = -\frac{dq}{dt}$ (since $q \downarrow$ and $dq < 0$)

- We get:

$$L \frac{d^2 q}{dt^2} + R \frac{dq}{dt} + \frac{q}{C} = 0$$

equation for
charge in this
circuit

RLC circuits – generate **damped** current oscillations

$$L \frac{d^2 q}{dt^2} + R \frac{dq}{dt} + \frac{q}{C} = 0$$



$$q(t) = A e^{-t/\tau_d} \cos(\omega' t + \phi_0)$$

- It reminds us of:

with

$$\omega' = \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}} \quad \text{and} \quad \tau_d = \frac{2L}{R}$$

$$m \frac{d^2 x}{dt^2} + b \frac{dx}{dt} + kx = 0$$



$$x(t) = A_0 e^{-t/t_0} \cos(\omega' t + \phi_0)$$


with

$$\omega' = \sqrt{\frac{k}{m} - \frac{b^2}{4m^2}} \quad \text{and} \quad t_0 = \frac{2m}{b}$$

- It's a damped oscillation!



Damped oscillations

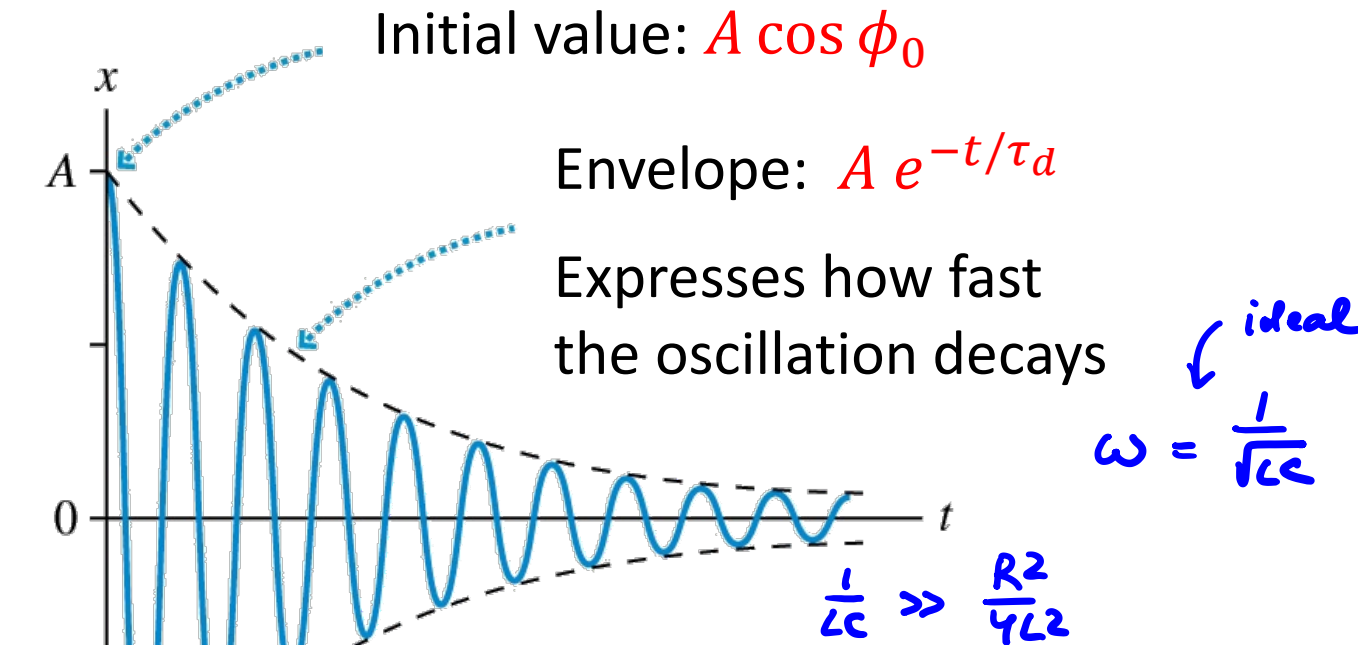


$$q(t) = A e^{-t/\tau_d} \cos(\omega' t + \phi_0)$$


with $\omega' = \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}$

and $\tau_d = \frac{2L}{R}$

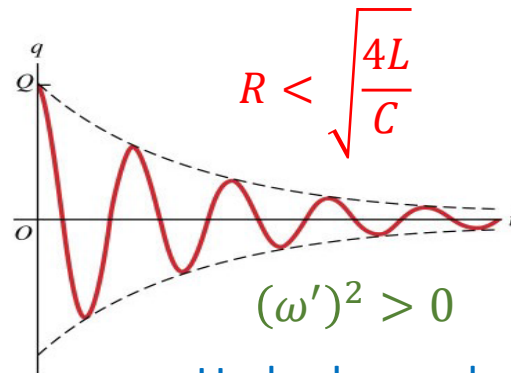
$\frac{1}{LC} = \frac{R^2}{4L^2}$ $\frac{1}{LC} \ll \frac{R^2}{4L^2}$



Underdamped circuit (small R)

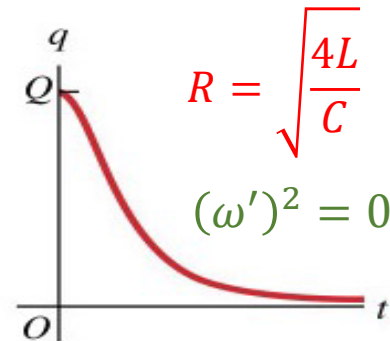

Critically damped circuit (larger R)

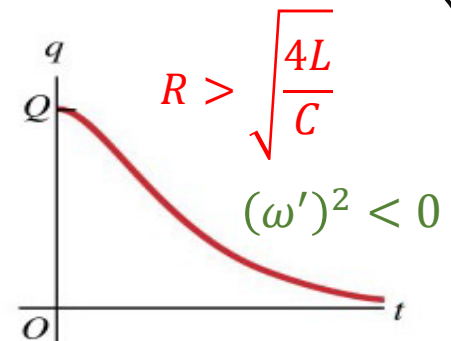

Overdamped circuit (very large R)

Q: You charge the capacitor for a very long time, then move S to position 2 at $t = 0$.

- Calculate I_L^{max} through the inductor.
- What is the first time at which the current is maximum?


$$E_{tot} = \frac{q^2}{2C} + \frac{Li^2}{2} = \frac{Q_0^2}{2C} = \frac{LI_{max}^2}{2}$$

$$I_0 = \frac{Q_0}{\sqrt{LC}}$$

$$\frac{Q_0}{C} = \Delta V_C = V_{bat}$$

$$\Delta V_R = 0$$

$$Q_0 = CV$$

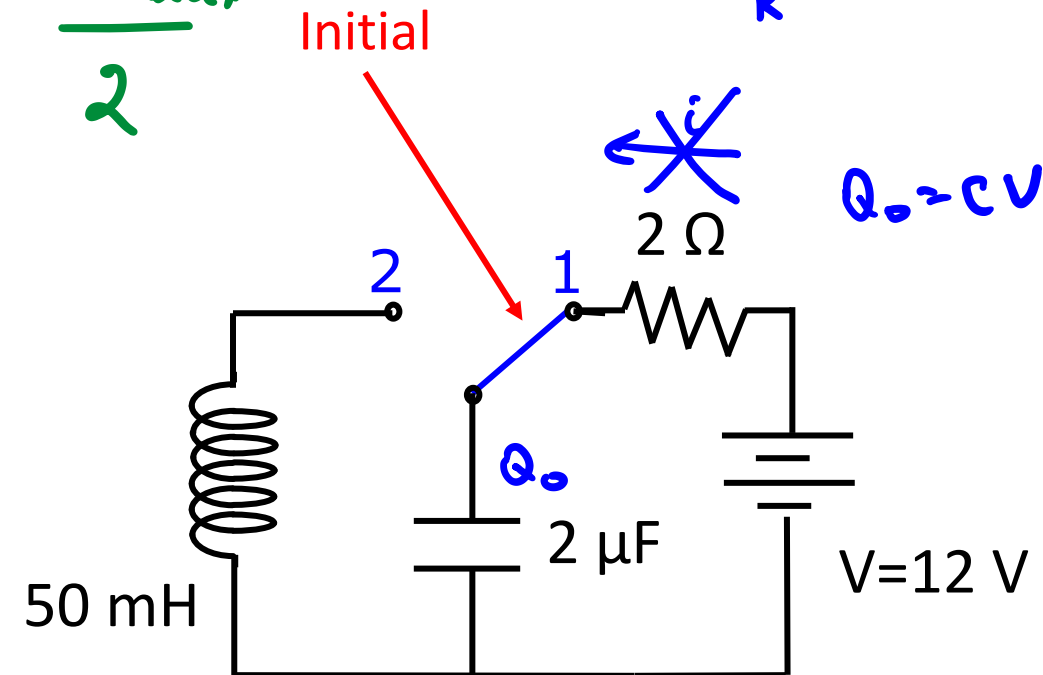

Q: You charge the capacitor for a very long time, then move S to position 2 at $t = 0$.

a) Calculate I_L^{max} through the inductor.

b) What is the first time at which the current is maximum?

- At $t = 0 +$: $\Delta V_C = 12 \text{ V}$ (no current through the resistor $\Rightarrow \Delta V_R = 0$)


$$Q_0 = C \Delta V_{C,\text{initial}} = (2\mu\text{F})(12 \text{ V}) = 24 \mu\text{C}$$

- So, the (electric) energy stored in the capacitor at $t = 0 +$ is:

$$U_C(t = 0 +) = \frac{Q_0^2}{2C} = 1.44 \times 10^{-4} \text{ J} = U_L = \frac{LI_{max}^2}{2}$$

- So the maximum current through the inductor is:

$$I_{max} = 75.9 \text{ mA}$$

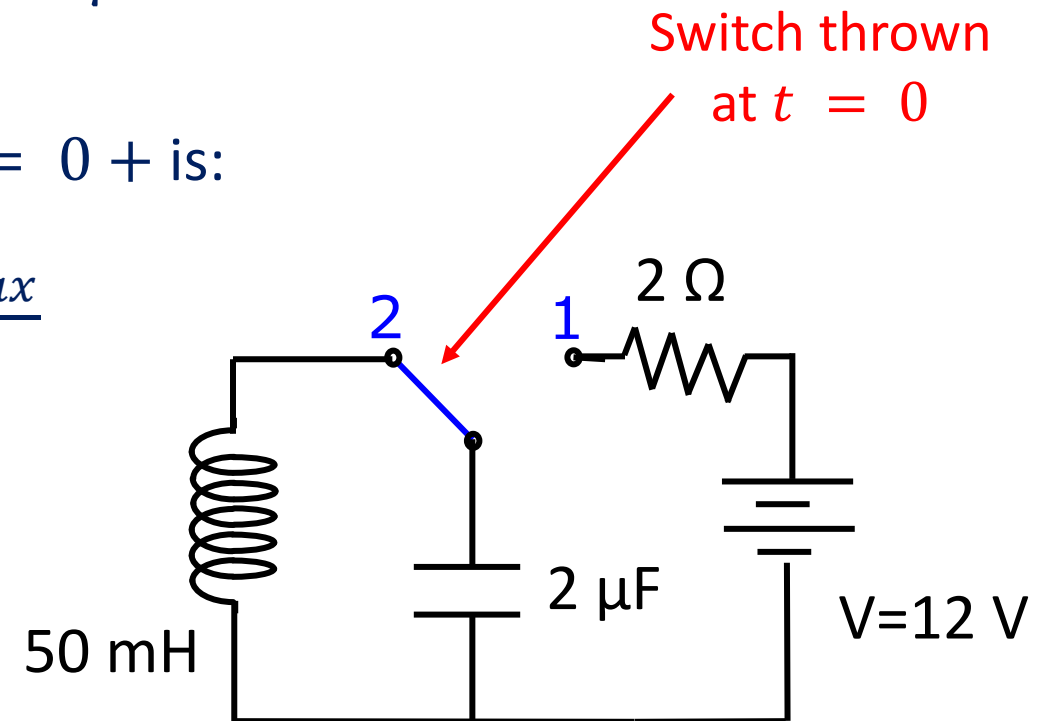

Q: You charge the capacitor for a very long time, then move S to position 2 at $t = 0$.

a) Calculate I_L^{max} through the inductor.

b) What is the first time at which the current is maximum?

• The current in the inductor is maximum for the first time at:


A. $t = \frac{T}{8}$

B. $t = \frac{T}{4}$

C. $t = \frac{T}{2}$

D. $t = \frac{3T}{4}$

E. $t = T$

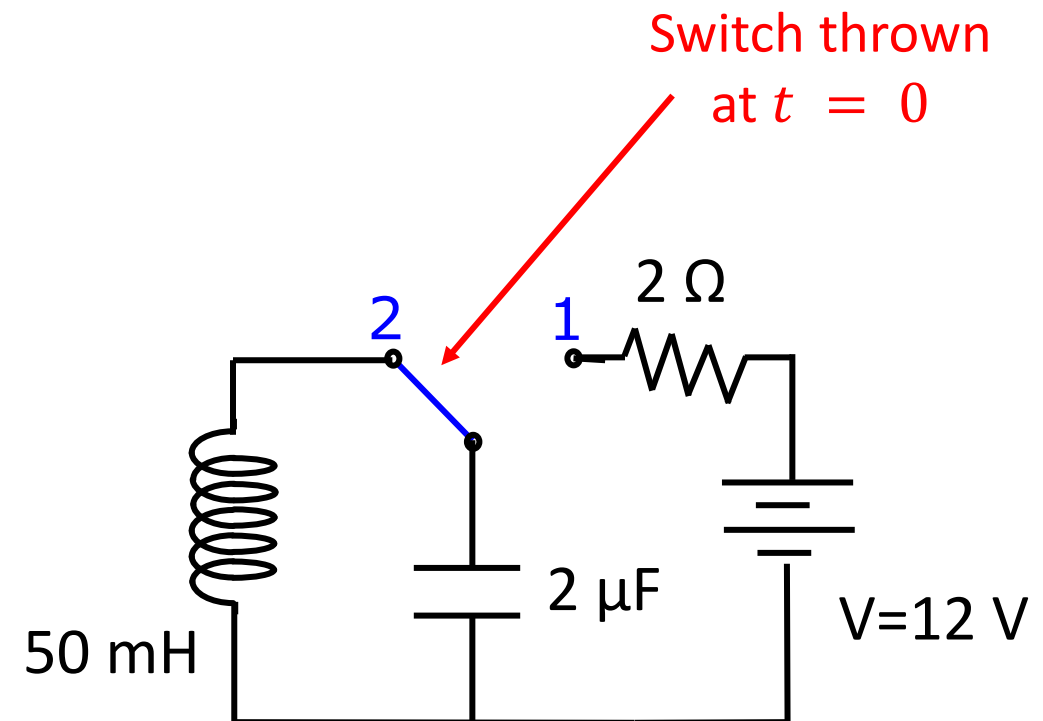

Q: You charge the capacitor for a very long time, then move S to position 2 at $t = 0$.

a) Calculate I_L^{max} through the inductor.


b) What is the first time at which the current is maximum?

$$\omega = \frac{1}{\sqrt{LC}}$$

$$T = \frac{2\pi}{\omega}$$

• After a time
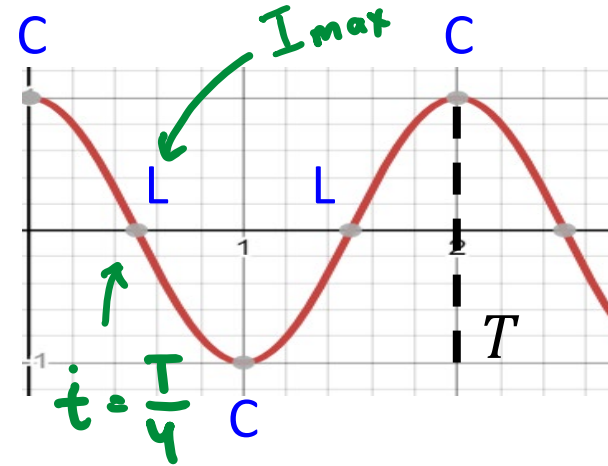
$$t = \frac{T}{4} = \frac{1}{4} \cdot \frac{2\pi}{\omega} = \frac{\pi}{2} \sqrt{LC}$$




Switch thrown
at $t = 0$

the energy initially stored in the capacitor is transferred to the inductor.

• Recall: $\omega = \frac{1}{\sqrt{LC}} = \frac{2\pi}{T}$

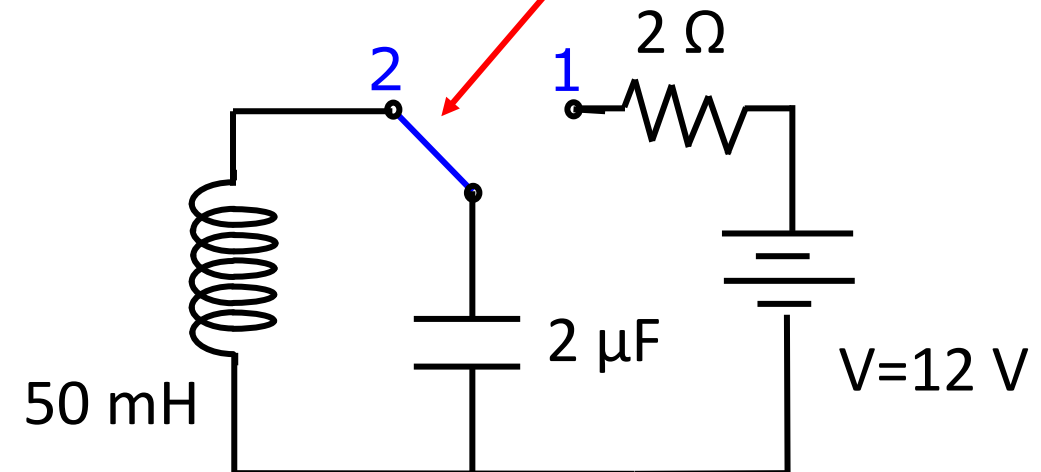
• Hence: $t = \frac{T}{4} = \frac{\pi}{2} \sqrt{LC} = 0.496 \text{ ms}$



Q: You charge the capacitor for a very long time, then move S to position 2 at $t = 0$.

In reality, room temperature wires always have a non-zero resistance. In this circuit, the resistance of the wires connecting L and C is $R = 0.1 \Omega$.

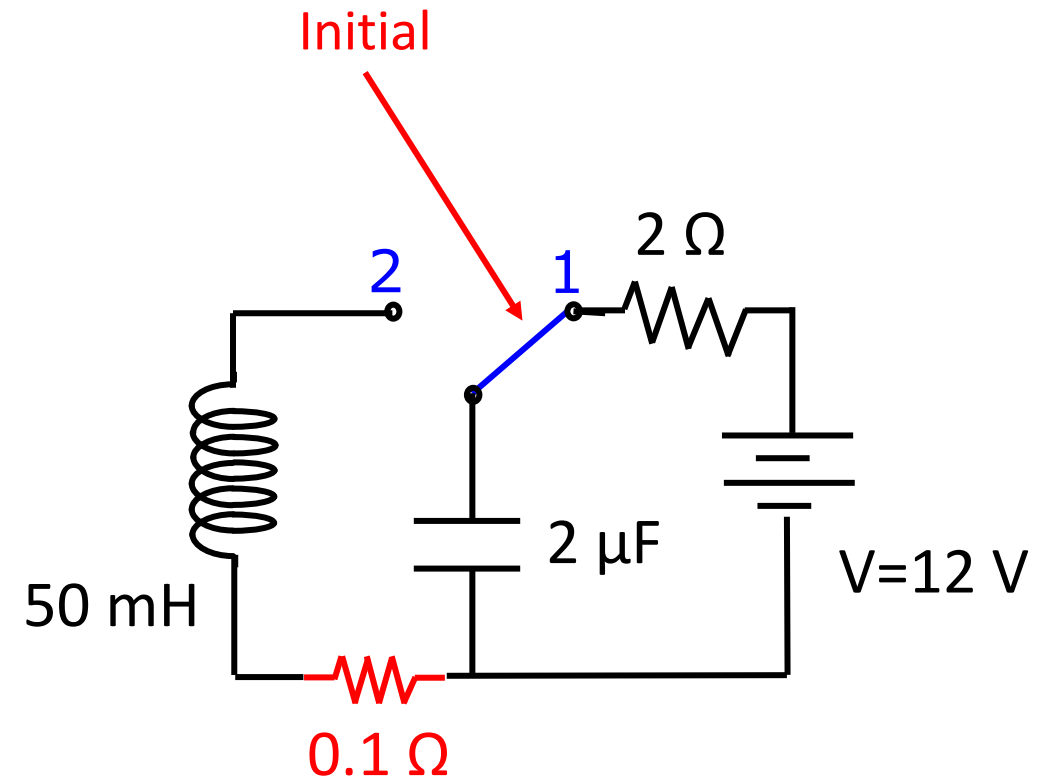Explain, in detail, how the 0.1Ω resistance of the wire affects the behaviour of the circuit.




Q: You charge the capacitor for a very long time, then move S to position 2 at $t = 0$.

In reality, room temperature wires always have a non-zero resistance. In this circuit, the resistance of the wires connecting L and C is $R = 0.1 \Omega$.


Explain, in detail, how the 0.1Ω resistance of the wire affects the behaviour of the circuit.

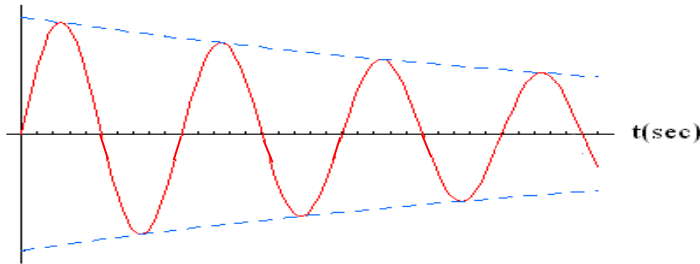- The small 0.1Ω resistance in the RLC circuit will damp out the oscillations in the current.



$$q(t) = Q_0 e^{-t/\tau_d} \cos(\omega' t) \quad i(t) = \left| \frac{dq}{dt} \right| = B e^{-t/\tau_d} \sin(\omega' t)$$

- The small 0.1Ω resistance will reduce the charge $q(t)$ on the capacitor to $1/e$ times its initial charge in a time $t = \tau_d = 2L/R = 1 \text{ sec}$.
- The oscillation frequency will be lowered slightly, from $\omega = \sqrt{\frac{1}{LC}}$ to $\omega' = \sqrt{\frac{1}{LC} - \frac{(1 \Omega)^2}{4L^2}}$.
- The oscillation will be under-damped: $\left(\frac{1}{\sqrt{LC}} \approx 3000 \right) \gg \left(\frac{1 \Omega}{2L} = 100 \right)$

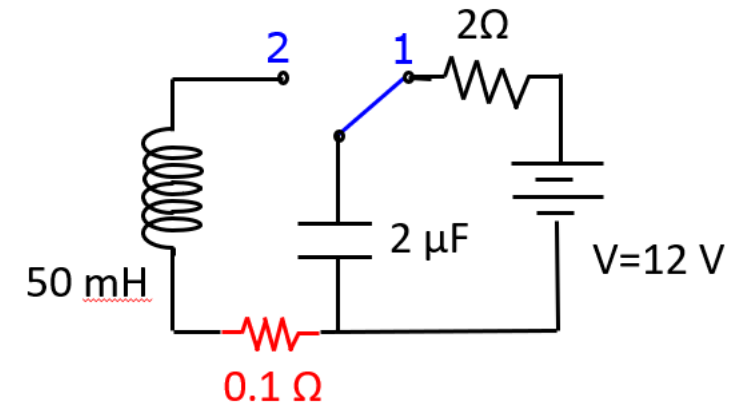

Q: At $t = 0$, the switch in the circuit below is quickly flipped from 1 to 2.

What resistance R is required to give an oscillatory frequency that is one-half the un-damped frequency?


$$\omega' = \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}$$

- A. 5Ω
- B. 15Ω
- C. 25Ω
- D. 35Ω
- E. 45Ω

$$\omega' = \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}$$

$$\omega = \frac{1}{\sqrt{LC}}$$

$$\omega = 2\omega'$$

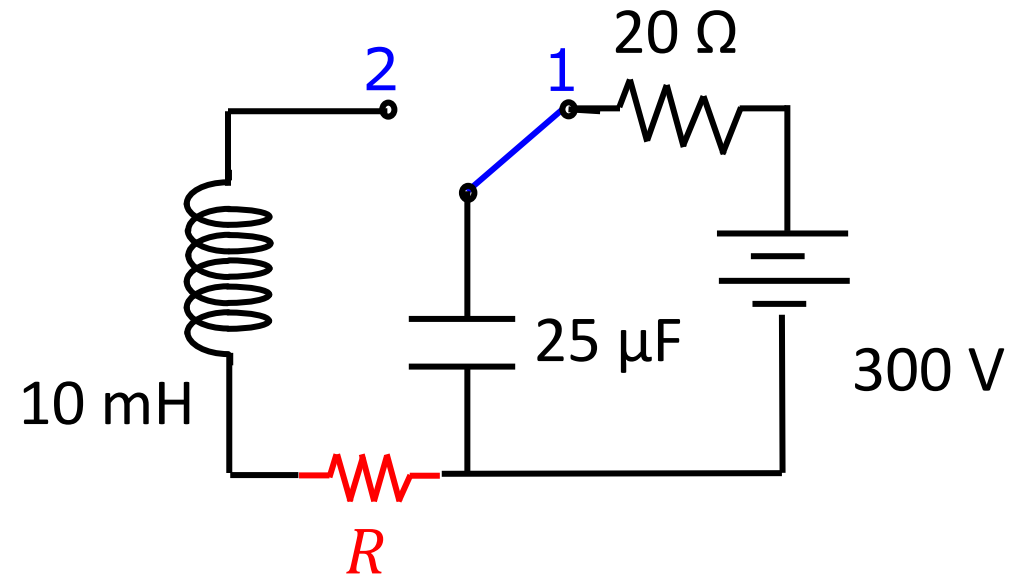

Q: At $t = 0$, the switch in the circuit below is quickly flipped from 1 to 2.

What resistance R is required to give an oscillatory frequency that is one-half the un-damped frequency?

$$\omega' = \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}$$

A. 5Ω

B. 15Ω

C. 25Ω

D. 35Ω


E. 45Ω

$$\frac{\omega'}{\omega} = \frac{1}{2} \Rightarrow 2\omega' = \omega \Rightarrow 2\sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}} = \sqrt{\frac{1}{LC}} \Rightarrow$$


$$4\left(\frac{1}{LC} - \frac{R^2}{4L^2}\right) = \frac{1}{LC} \Rightarrow$$

$$\frac{3}{LC} = \frac{4R^2}{4L^2} = \frac{R^2}{L^2} \Rightarrow$$


$$R = \sqrt{\frac{3L}{C}} = 35 \Omega$$

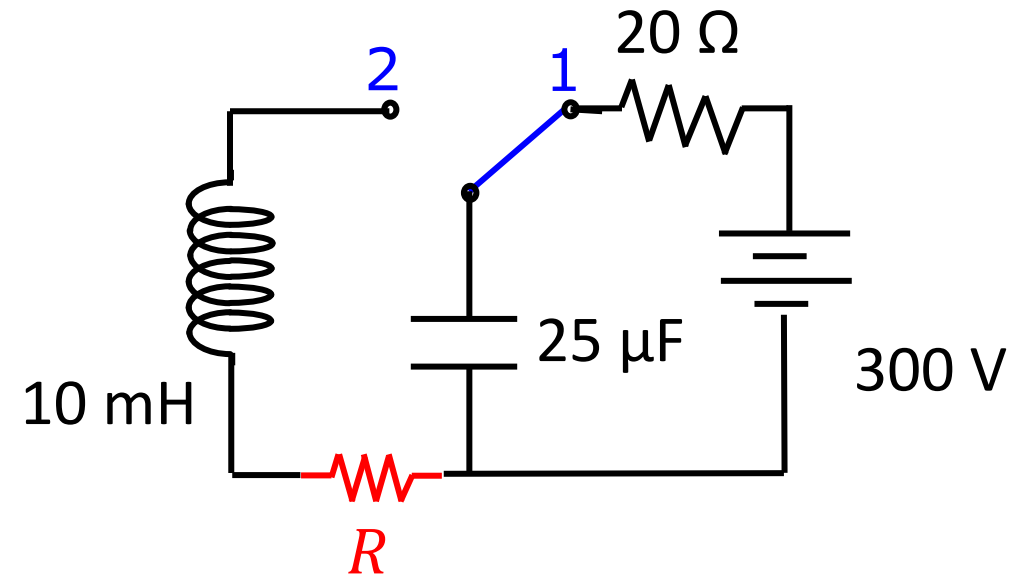

Combining Inductors

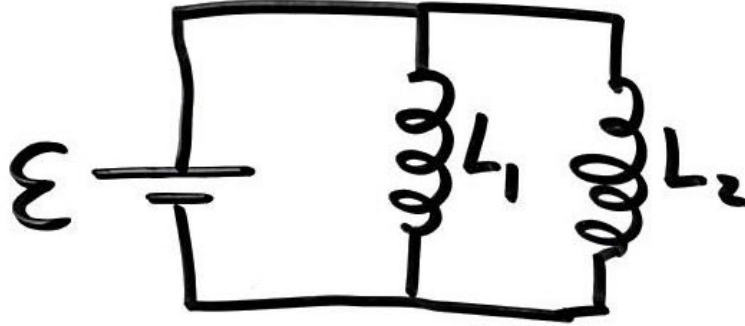
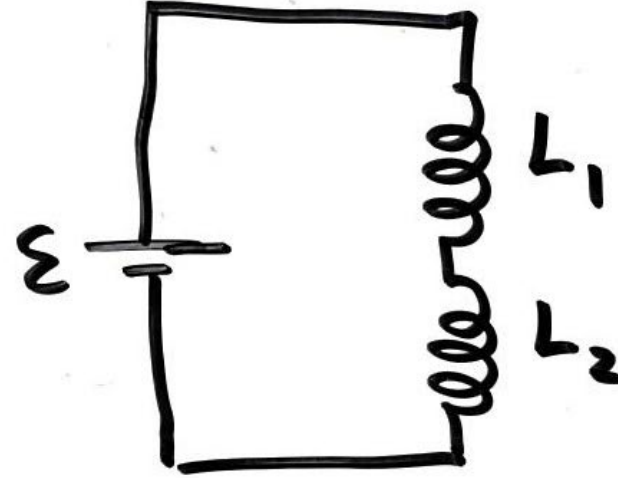
$$\frac{1}{L_{eq,p}} = \frac{1}{L_1} + \frac{1}{L_2}$$



$$L_{eq,s} = L_1 + L_2$$

Inductors in parallel and series add just like resistors


Demo: Big Bang Capacitor

Let's wrap it up!

How many things can you see in one capacitor?



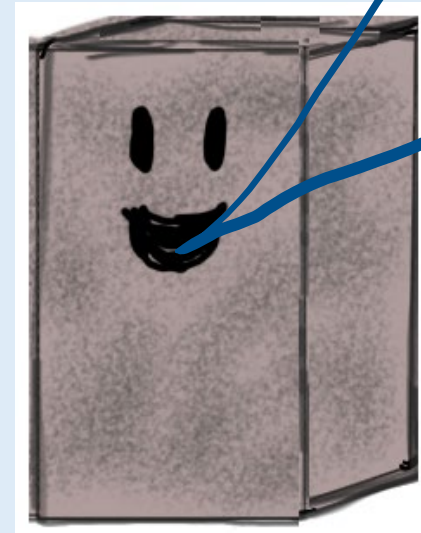- Name 3 (or more) concepts relevant to this demo



Last time in
Physics 157...

How many things can you see in one capacitor?

- It stores electric charge! (How much?)
- It stores electric energy! (How much?)
- Where does the energy go when we shorten the circuit?
- Why do we damage it when we shorten it? (Its C dropped by $1/6$ after 3 experiments!!)
- What will we get if we account for a small but finite resistance of the copper rod? How can we calculate this resistance?
-

- End DC Circuits