

Problem C4.2 (☆): An L-R-C series circuit, the components have the following values: $L = 2.0 \text{ mH}$, $C = 18 \mu\text{F}$, and $R = 15 \Omega$. The AC power source has an RMS voltage of 120 V with a frequency of 3.2 kHz .

- (a) Draw the impedance triangle for this circuit.
 (b) Calculate the impedance Z and the phase angle ϕ .

Your friend gives you a new power source with the same RMS voltage, but an unknown frequency.

- (c) You observe the power factor of $\cos \phi = 0.819$. What is the frequency of this source?

(a) $X_C = \frac{1}{\omega C} = 17.4 \Omega$
 $X_L = \omega L = 6.4 \Omega$
 $R = 15 \Omega$

(b) $Z = \sqrt{R^2 + (X_L - X_C)^2} = \underline{18.6 \Omega}$
 $\phi = \tan^{-1}\left(\frac{X_L - X_C}{R}\right) = -0.631 \text{ rad}$

(c) $\cos \phi = 0.819 \Rightarrow \phi = 0.611 \text{ rad}$

$$\tan \phi = \frac{\omega L - \frac{1}{\omega C}}{R}$$

$$\therefore \omega^2 LC - RC \tan \phi \omega - 1 = 0$$

$$\omega = \underline{8077} \text{ or } \cancel{-3700} \text{ rad/s}$$

negative soln. unphysical

Problem C4.3 (☆☆): You are given an L-R-C series circuit with unknown values for L , R , and C . You do have, however, an AC voltage source with $V_{RMS} = 8\text{ V}$ and a tunable frequency ω . You also have an Ammeter that measures the RMS current I_{RMS} and the power factor $\cos \phi$.

- (a) Devise a procedure to determine L , R , and C by measuring the circuit with the tools at hand.

(a) The RMS current and phase angle are given by

$$I_{RMS}(\omega) = \frac{V_{RMS}}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$$

$$\tan \phi = \frac{\omega L - \frac{1}{\omega C}}{R}$$

Measuring I_{RMS} and ϕ at several frequencies should be sufficient to determine R , L , and C .

A key simplification occurs at the resonance frequency $\omega_0 = \sqrt{\frac{1}{LC}}$, where $I_{RMS} = \frac{V_{RMS}}{R}$.

This is but one of many ways.

Problem C4.3 continued (☆☆): Using the same setup, suppose you measured I_{RMS} as a function of frequency and found that the maximum RMS current is 40 mA at $\omega_0 = 12.5 \text{ kHz}$.

- (b) What is the resistance R ? What does this tell you about L and C ?
- (c) What is the power factor at $\omega = \omega_0$?
- (d) In addition you find that at $\omega_1 = 17 \text{ kHz}$ the power factor is 0.5. Based on this information, what are the values of L and C ?

(b) At resonance, $I_{RMS}(\omega_0) = \frac{V_{RMS}}{R}$

$\therefore R = \underline{200 \Omega}$

At resonance, $\omega_0 = \sqrt{\frac{1}{LC}}$. Hence we have the equation to determine L & C .

(c) At resonance, $\tan \phi = \frac{\cancel{\omega L} - \cancel{\frac{1}{\omega C}}}{R} = 0$

$\therefore \underline{\cos \phi = 1}$

(d) At 17 kHz , $\cos \phi = 0.5 \Rightarrow \phi = 60^\circ$

$\therefore \tan(60^\circ) = \sqrt{3} = \frac{\omega_1 L - \frac{1}{\omega_1 C}}{R}$

From (a): $\omega_0^2 = \frac{1}{LC}$

$L \left(\omega_1 - \frac{\omega_0^2}{\omega_1} \right) = \sqrt{3} R \Rightarrow \underline{L = 44.3 \text{ mH}}$

$C = \frac{1}{L \omega_0^2} = \underline{144 \text{ nF}}$