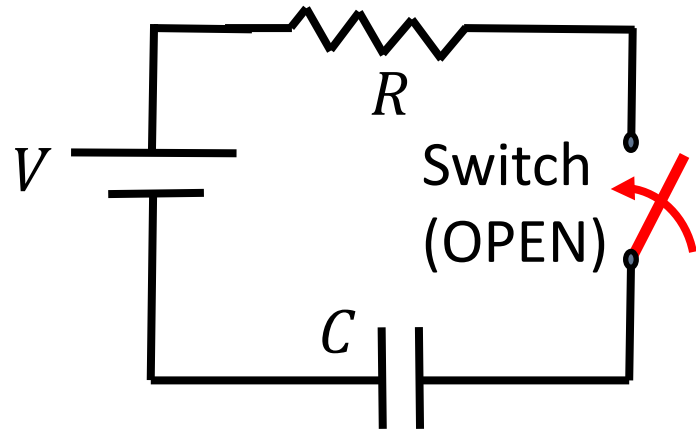


Lecture 6.

RC-circuits: circuits with dynamics

Last Time



initially uncharged

- Limiting cases:
 - Immediately after the switch is closed:
 - Path created \Rightarrow current starts flowing
 - At $t = 0$: $q = 0 \Rightarrow \Delta V_C = 0 \Rightarrow$
capacitor acts as ideal wire
 - After a very long time:
 - Capacitor is fully charged \Rightarrow does not accept more charge \Rightarrow no current
 - At $t = \infty$:
capacitor acts as an open switch
- What happens in between??

CASE 1: Charging a capacitor - 3

- Kirchhoff loop law (travel CW):

$$V - iR - \frac{q}{C} = 0$$


- Let's take time derivative:

$$0 - R \frac{di}{dt} - \frac{1}{C} \frac{dq}{dt} = 0$$

- Note that: $\frac{dq}{dt} = i$, hence: $-R \frac{di}{dt} - \frac{i}{C} = 0$.

Initial charge $q_c(t = 0) = 0$

Switch is suddenly
closed at $t = 0 +$

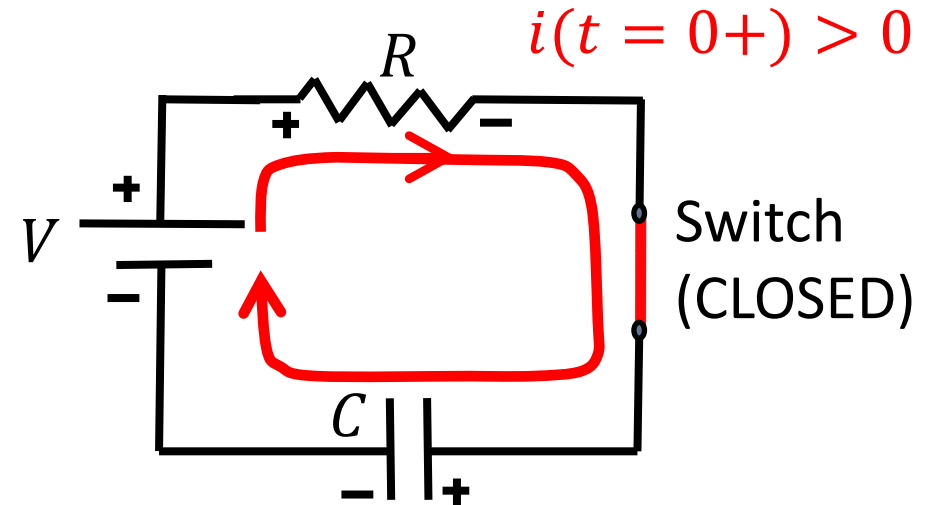


- Here we take $\frac{dq}{dt} = +i$ since current i brings + charge to the positive plate => charge on the plates increases => $\frac{dq}{dt} > 0$.

- We have got a differential equation for $i(t)$, and a connection between $q(t)$ and $i(t)$

CASE 1: Charging a capacitor - 4

$$\boxed{\frac{dq}{dt} = i,} \quad (1)$$
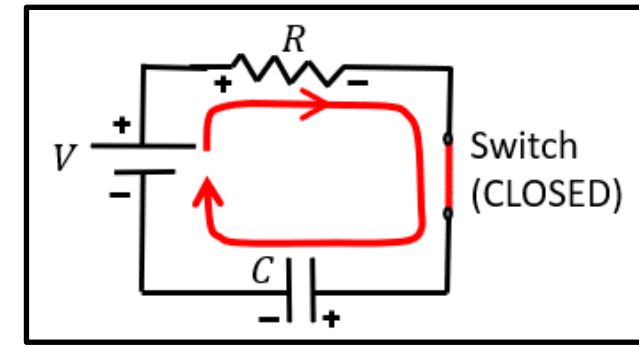
$$\boxed{-R \frac{di}{dt} - \frac{i}{C} = 0.} \quad (2)$$



- We need to find their solutions, $i(t)$ and $q(t)$, that satisfy **initial conditions**:

➤ For current: $i(t = 0) = I_0 = V/R$

➤ For charge: $q(t = 0) = Q_0 = 0$ & $q(t = \infty) = CV$


$$\boxed{i(t) = \frac{V}{R} e^{-\left(\frac{t}{RC}\right)}}$$

initial current $t \rightarrow \infty$

$$\boxed{q(t) = CV \left(1 - e^{-\left(\frac{t}{RC}\right)}\right)}$$

$$q(t = \infty) = CV$$

final charge

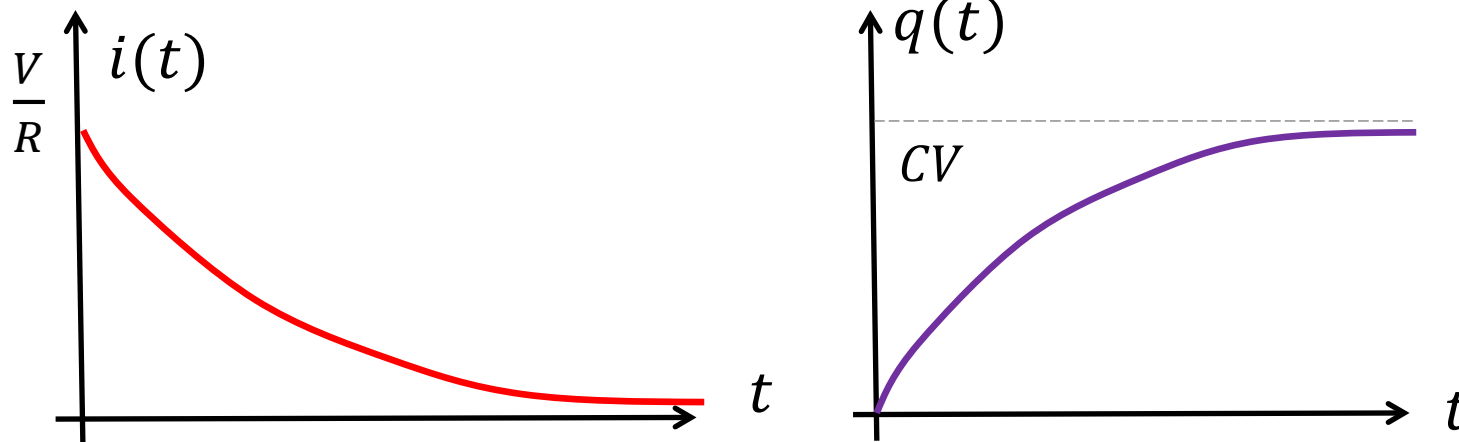

$$\boxed{\tau = RC}$$

time
constant

CASE 1: [Charging a capacitor - 5](#) Math details

Loop law


$$V - i(t)R - \frac{q(t)}{C} = 0$$

Take the derivative

$$0 - R \frac{di}{dt} - \frac{1}{C} \frac{dq}{dt} = 0, \quad i = \frac{dq}{dt}$$

Separate variables

$$\frac{di}{dt} = -\frac{1}{RC} dt = 0$$

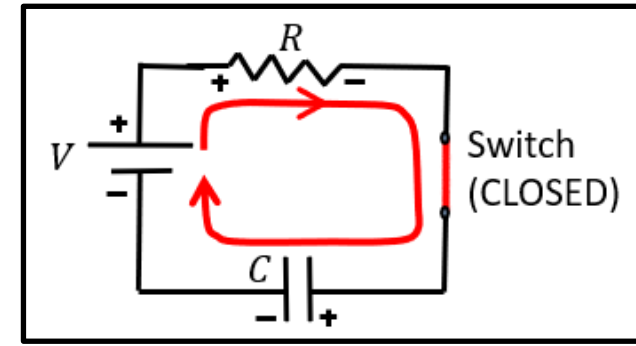

$$\int \frac{di}{i} = -\frac{1}{RC} \int dt$$

using $i(0) = V/R$

$$\ln(i) = -\frac{t}{RC} + \text{const}$$

$$i(t) = \text{const}' e^{-t/RC}$$

$$i(t) = I_0 e^{-t/RC} = \frac{V}{R} e^{-t/RC}$$

$RC = \tau =$
time
constant

Note that:

$$q(\infty) = CV = Q_f$$

$$i(t) = \frac{dq(t)}{dt} \Rightarrow q(t) = \int i(t) dt$$

$$q(t) = \frac{V}{R} \int e^{-\frac{t}{RC}} dt$$

$$q(t) = -RC \frac{V}{R} e^{-\frac{t}{RC}} + \text{const}$$

$$q(t) = -CV e^{-\frac{t}{RC}} + \text{const}$$


➤ Use $q(0) = 0$: $0 = -CV + \text{const}$

$$\Rightarrow \text{const} = CV$$

$$q(t) = CV (1 - e^{-t/RC})$$


CASE 2: Discharging a capacitor - 1

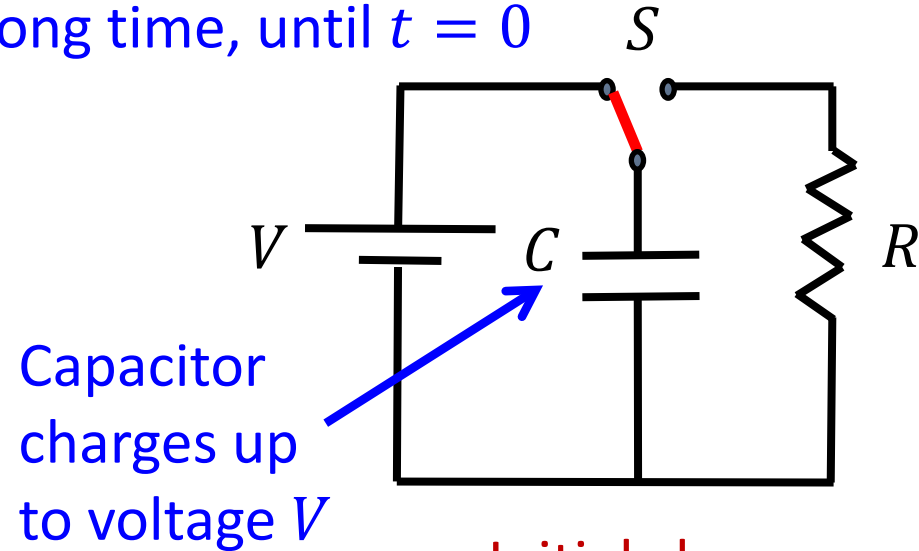Switch is at the left position for a very long time, until $t = 0$



Initial charge:
 $Q_0 = CV$

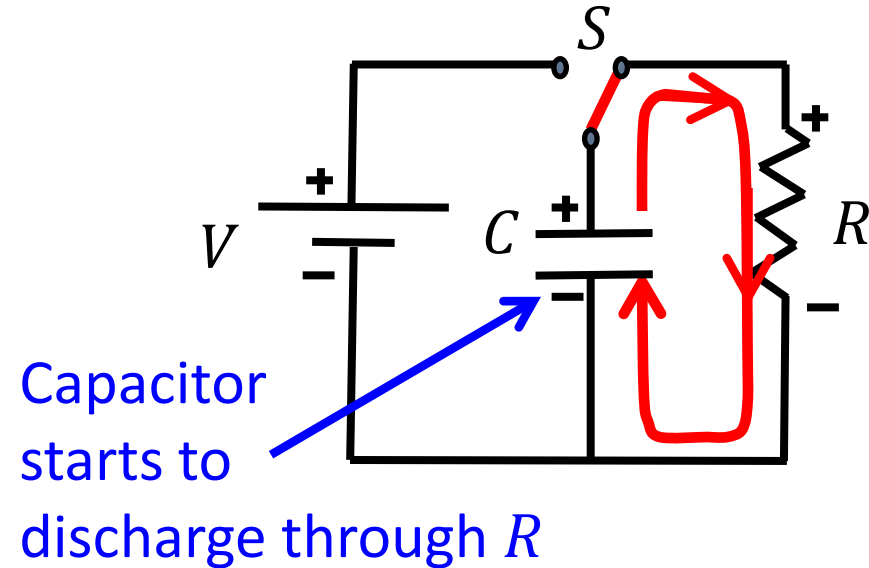Switch is suddenly flipped to the right at $t = 0 +$



- Now **the capacitor is discharging**: positive charges from the $+$ plate flow through the resistor and **recombine** (meet and annihilate) with negative charges on the $-$ plate.

- Once the switch is flipped to right, Kirchhoff's loop law gives: $\frac{q(t)}{C} - iR = 0$ $\curvearrowright i(t)$



CASE 2: Discharging a capacitor - 2 Math details

$$\frac{q(t)}{C} - i(t)R = 0 \quad \text{Note that here } i = -\frac{dq}{dt} \text{ since } q \text{ is decreasing.}$$

$$\frac{q}{C} + R \frac{dq}{dt} = 0 \Rightarrow \frac{dq}{q} = -\frac{1}{RC} dt \Rightarrow q(t) = \text{const } e^{-t/RC}$$

• Initial condition: $q(0) = CV \Rightarrow q(t) = Q_0 e^{-t/RC}$, with $Q_0 = CV$

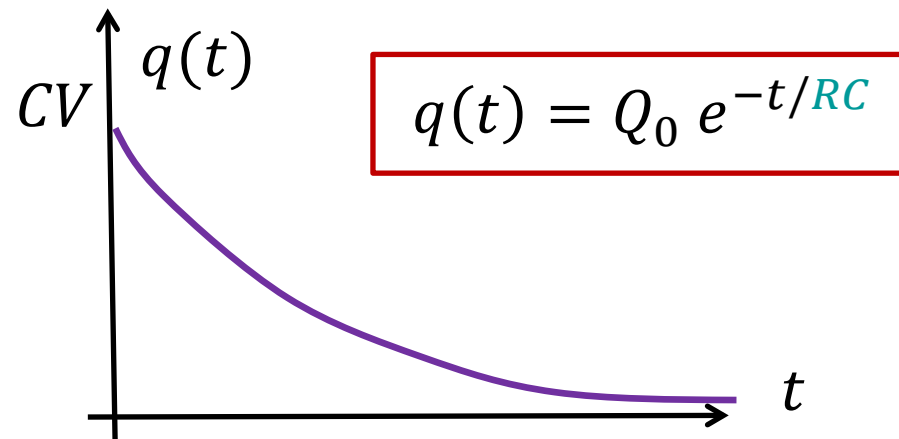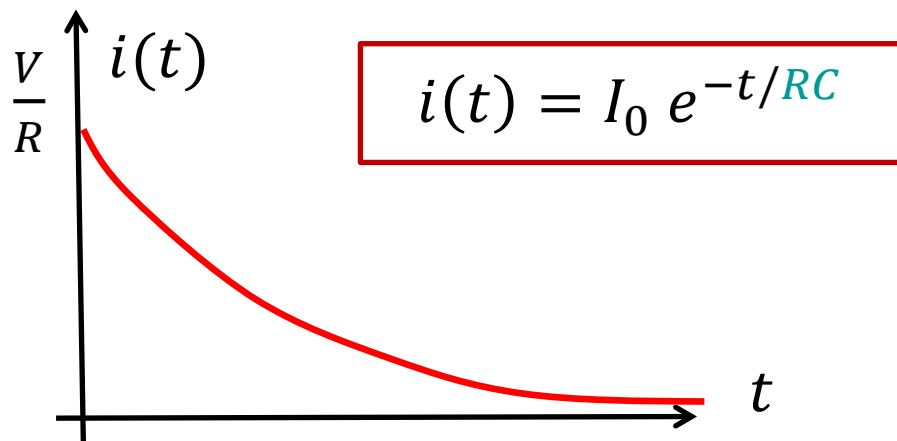• Current: $i = -\frac{dq}{dt} = -Q_0 \left(-\frac{1}{RC}\right) e^{-t/RC} = I_0 e^{-t/RC}$, with $I_0 = \frac{Q_0}{RC} = \frac{CV}{RC} = \frac{V}{R}$




$$\tau = RC$$

time constant

How long is *very long*?

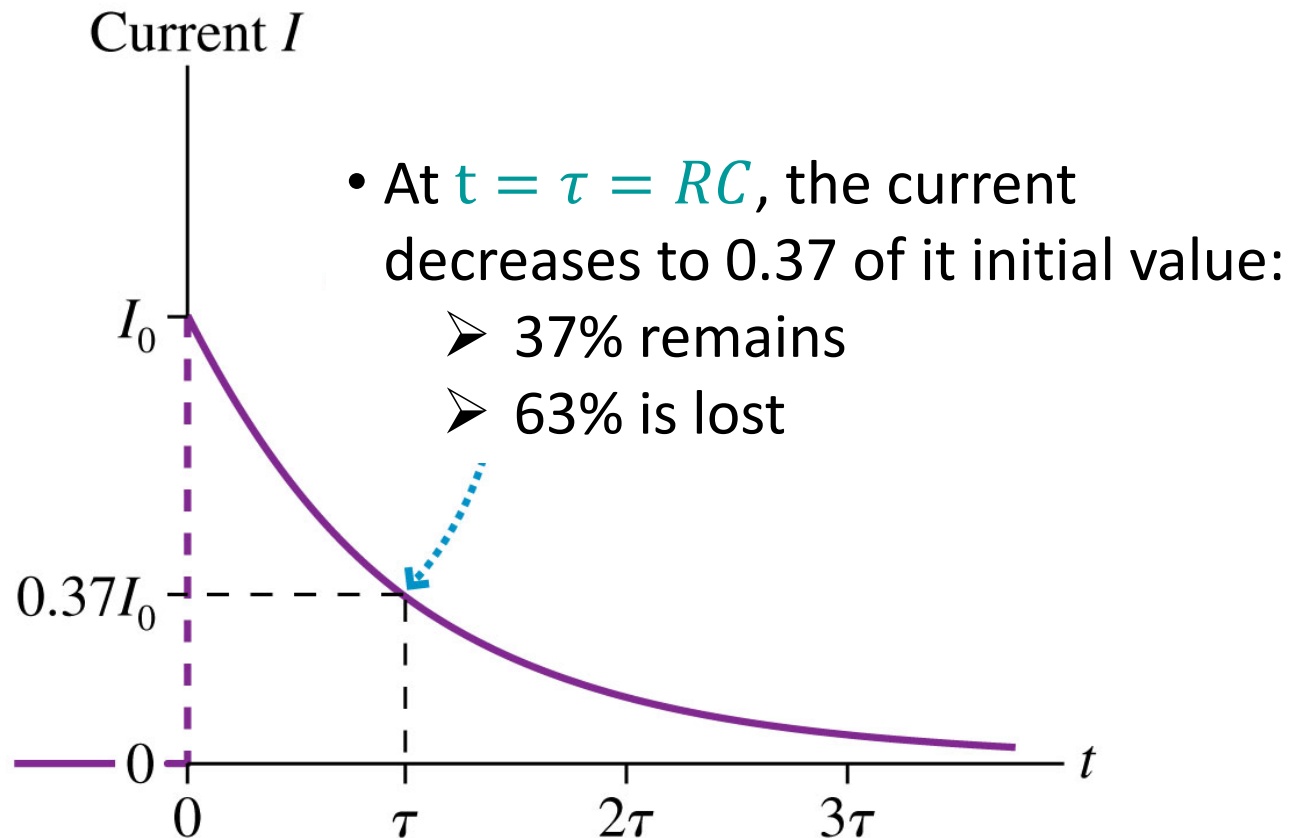- The relevant time scale is $\tau = RC$:



$$I(t) = I_0 e^{-\frac{t}{\tau}}, \quad \text{with } I_0 = V/R$$

$$I(t = \tau) = I_0 e^{-1} = \frac{I_0}{e} = \frac{I_0}{2.71} = 0.37 I_0$$

$$I(t = 2\tau) = 0.37 I(t = \tau) = 0.14 I_0$$



$$I(t = 3\tau) = 0.37 I(t = 2\tau) = 0.05 I_0$$

...

$$I(t = 6\tau) = 0.37 I(t = 5\tau) = 0.002 I_0$$



"Very long" means $t \gg \tau = RC$

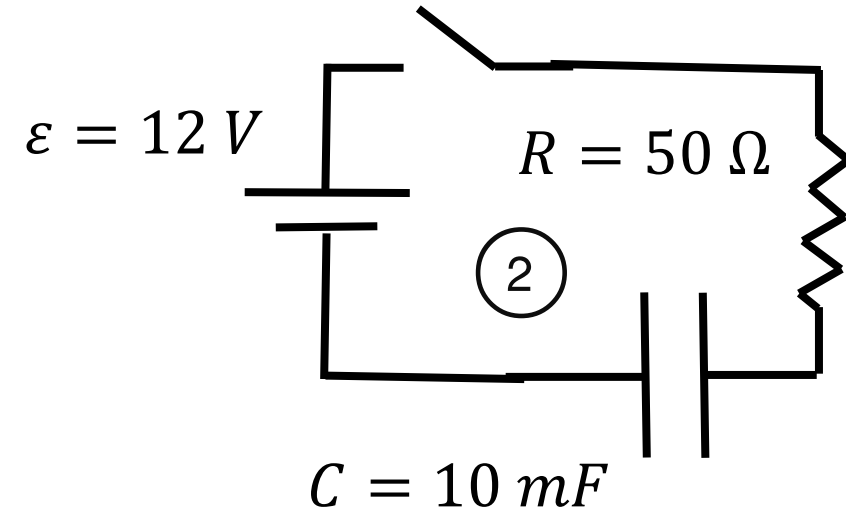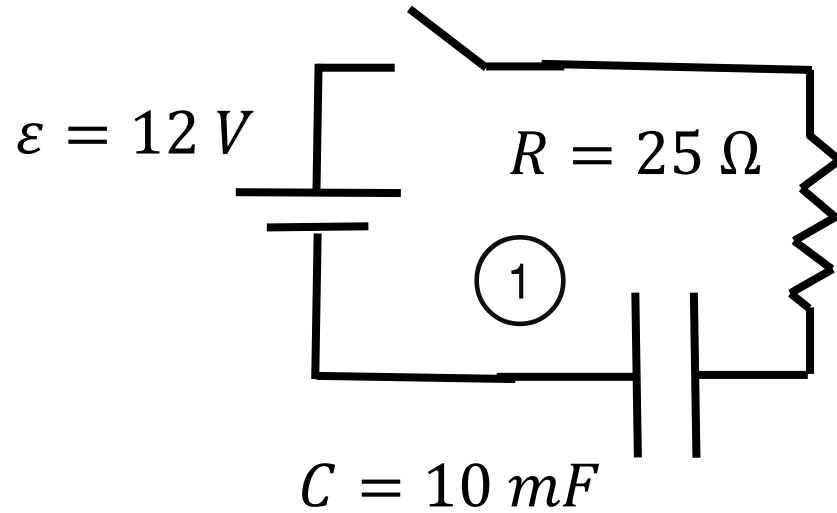Q: In which of these RC-circuits the charge decays faster?



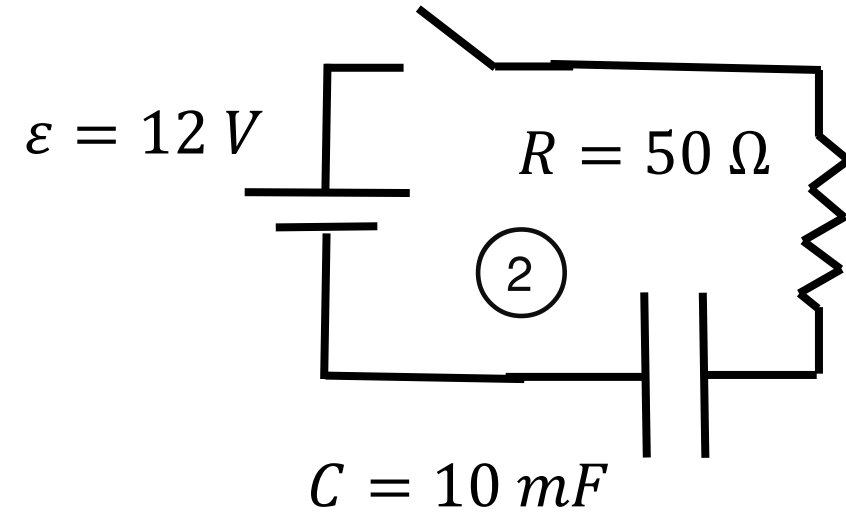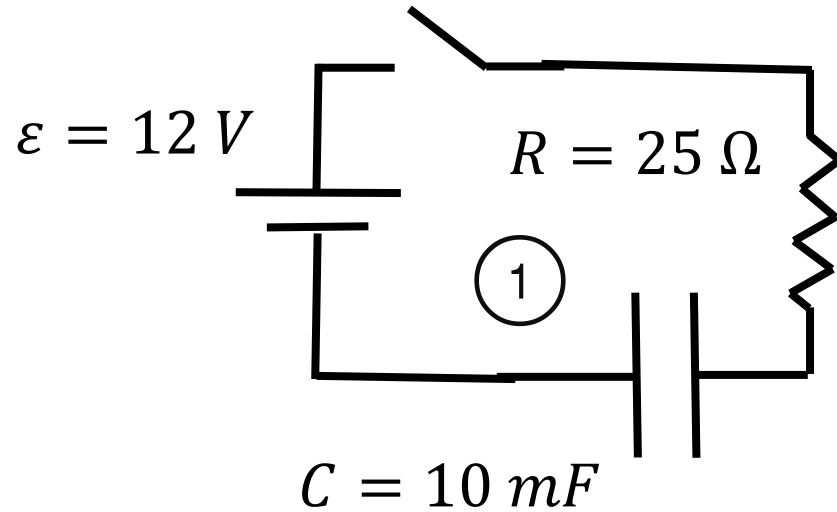- A. Faster in 1
- B. Faster in 2
- C. Decay at the same speed
- D. Not enough information

Q: In which of these RC-circuits the charge decays faster?



- $\tau_1 = 250\text{ ms}$, $\tau_2 = 500\text{ ms}$
- For circuit 2 it takes twice longer to lose 63% of charge =>
- Charge in circuit 1 decays faster.

A. Faster in 1

B. Faster in 2


C. Decay at the same speed

D. Not enough information

Q: $q_C(0-) = 0$. At time $t = 0$, the switch is closed.

What is the voltage across the capacitor immediately after the switch is closed ($t = 0+$) ?

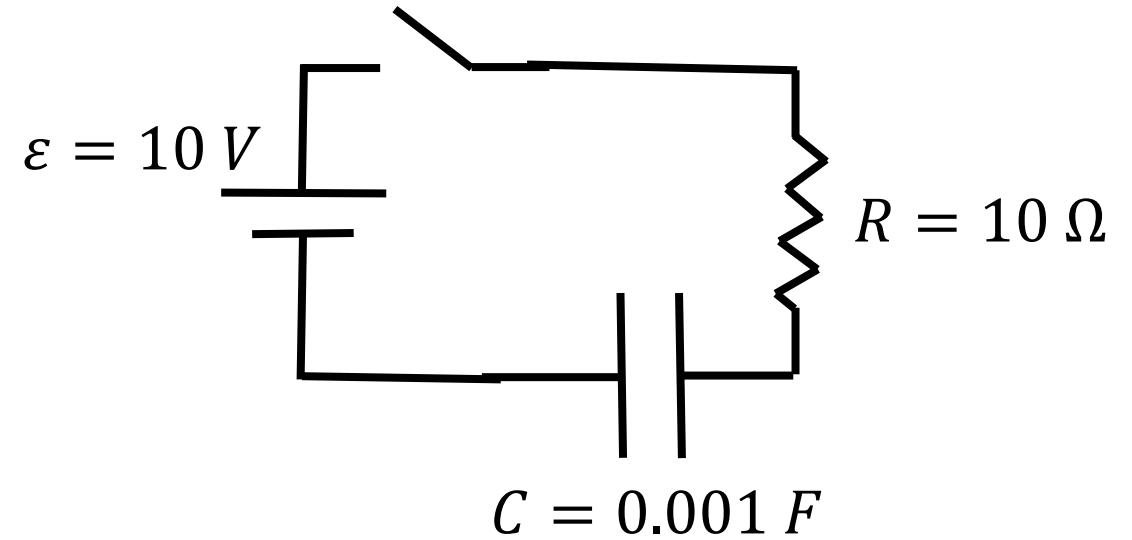- A. 0 V
- B. 10 V
- C. 5 V
- D. None of these.




Q: $q_C(0-) = 0$. At time $t = 0$, the switch is closed.


What is the voltage across the capacitor immediately after the switch is closed ($t = 0+$) ?

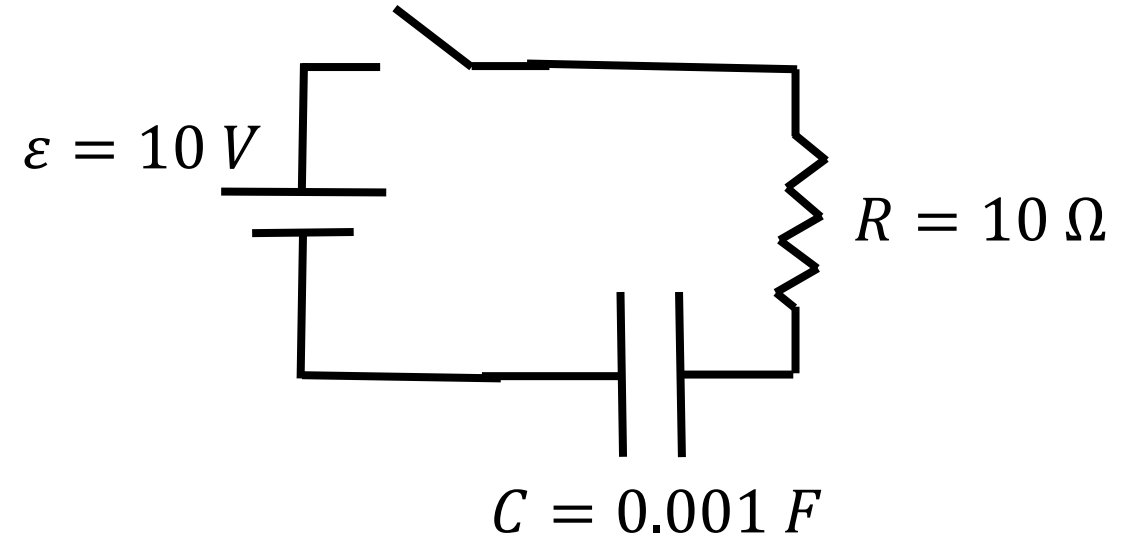- A. 0 V
- B. 10 V
- C. 5 V
- D. None of these.

$= 0$ \rightarrow $\Delta V_C = \frac{Q}{C} = 0$



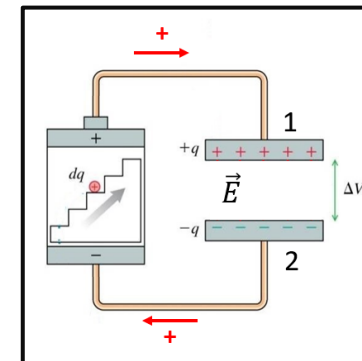- Since $q(0) = 0$, $\Delta V_C(0) = 0$
- Since $\Delta V_C(0) = 0$, immediately after the switch is closed it acts as an ideal wire (there is no charge flow through it, but there is a charge flow around it as if it was an ideal wire)




Q: This capacitor is fully charged. What is the magnitude of the voltage drop across the resistor?

$$I \equiv 0$$


$$|\Delta V_R| + |\Delta V_C| = \mathcal{E}$$

$$\hookrightarrow |\Delta V_R| = \frac{\mathcal{E}}{0} = \infty$$

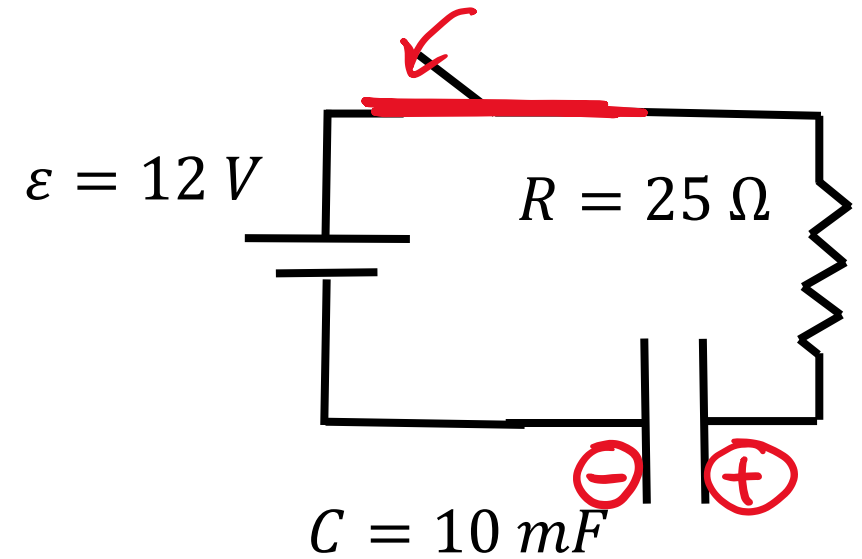- A. 0
- B. 4 V
- C. 6 V
- D. 8 V
- E. 12 V



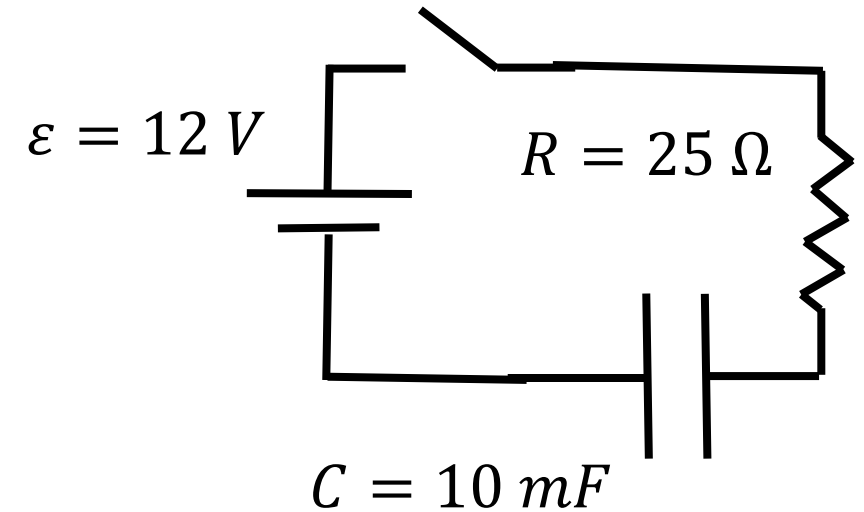Q: This capacitor is fully charged. What is the magnitude of the voltage drop across the resistor?



- When the capacitor is fully charged, there is no more current in the circuit (the capacitor does not accept more charge)


- The voltage drop across the resistor is:
 $\Delta V_R = IR = 0$ since $I = 0$

- A. 0
- B. 4 V
- C. 6 V
- D. 8 V
- E. 12 V

Q: Before we close the switch, $q_C = 0$.

1) Compute the current $i(t)$ as a function of time

2) Compute $q_C(t_1 = 250 \text{ ms})$

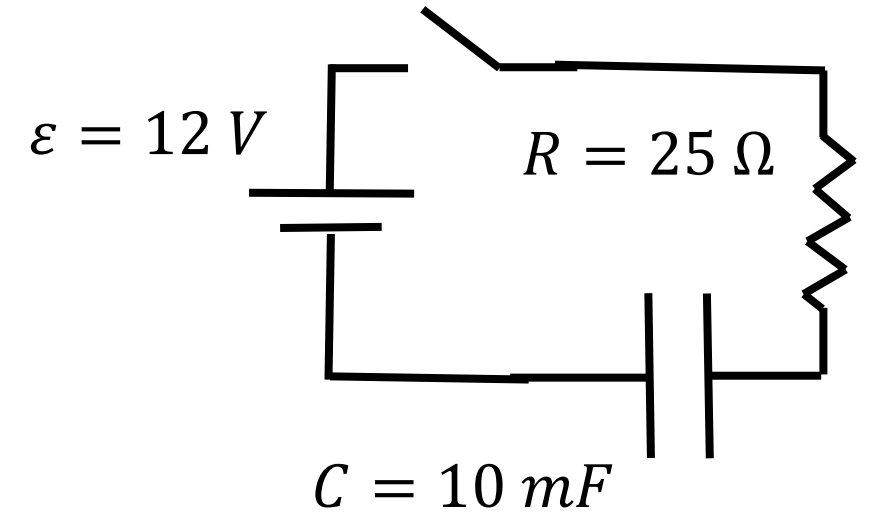


$$a) \quad i(t) = I_0 e^{-\frac{t}{\tau}} \quad q(t) = Q_f \left[1 - e^{-\frac{t}{\tau}} \right]$$

$$\tau = R \cdot C \quad I_0 = \frac{\mathcal{E}}{R}$$

(no cap)

$$Q_f = C \mathcal{E}$$

(no resistor)

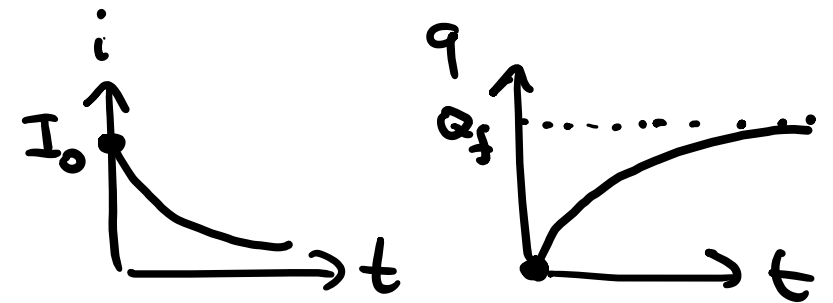


$$b) \quad q(t = 250 \text{ ms}) = Q_f \left[1 - e^{-\frac{250 \text{ ms}}{\tau}} \right] = \dots$$

Remember the graphs

Q: Before we close the switch, $q_C = 0$.

- 1) Compute the current $i(t)$ as a function of time
- 2) Compute $q_C(t_1 = 250 \text{ ms})$

- Here the capacitor is **charging** =>

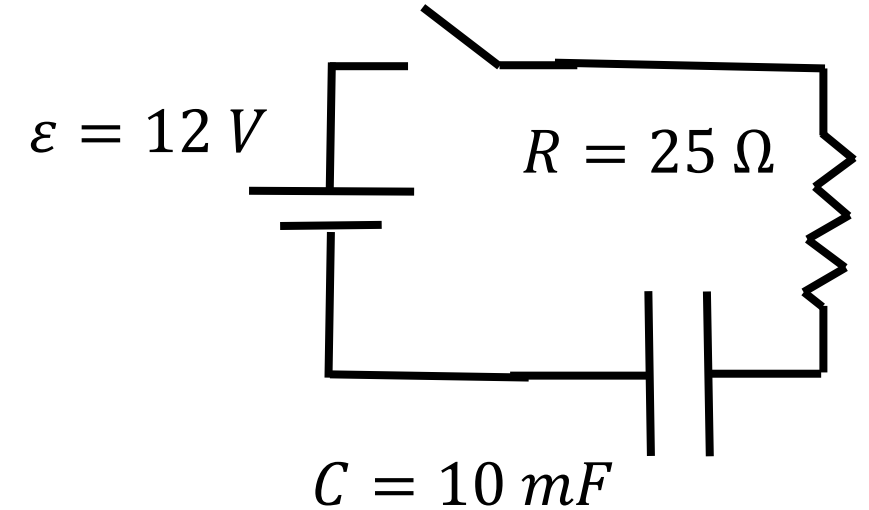

$$i(t) = I_0 e^{-t/RC}, \quad q(t) = Q_f (1 - e^{-t/RC})$$

• $\tau = RC = 0.25 \text{ ms}$ • $I_0 = \varepsilon/R = 12/25 = 0.48 \text{ A}$ • $Q_f = \varepsilon C = 12 \cdot 10^{-2} \text{ C}$

$$i(t) = 0.48 e^{-t/0.25} = 0.48 e^{-4t} \text{ Amper} = 0.48 e^{-t/0.25}$$

$$q(t = 0.25 \text{ s}) = 12 \cdot 10^{-2} (1 - e^{-\frac{0.25}{0.25}}) = 0.076 \text{ Coulomb}$$


Remember the graphs

Q: All the capacitors in the circuit below are initially uncharged.

- a) Find the current through the ammeter, $I_A(0+)$, just after the switch S is closed.
- b) Find $I_A(\infty)$ a long time after the switch S has been closed.

HINT--

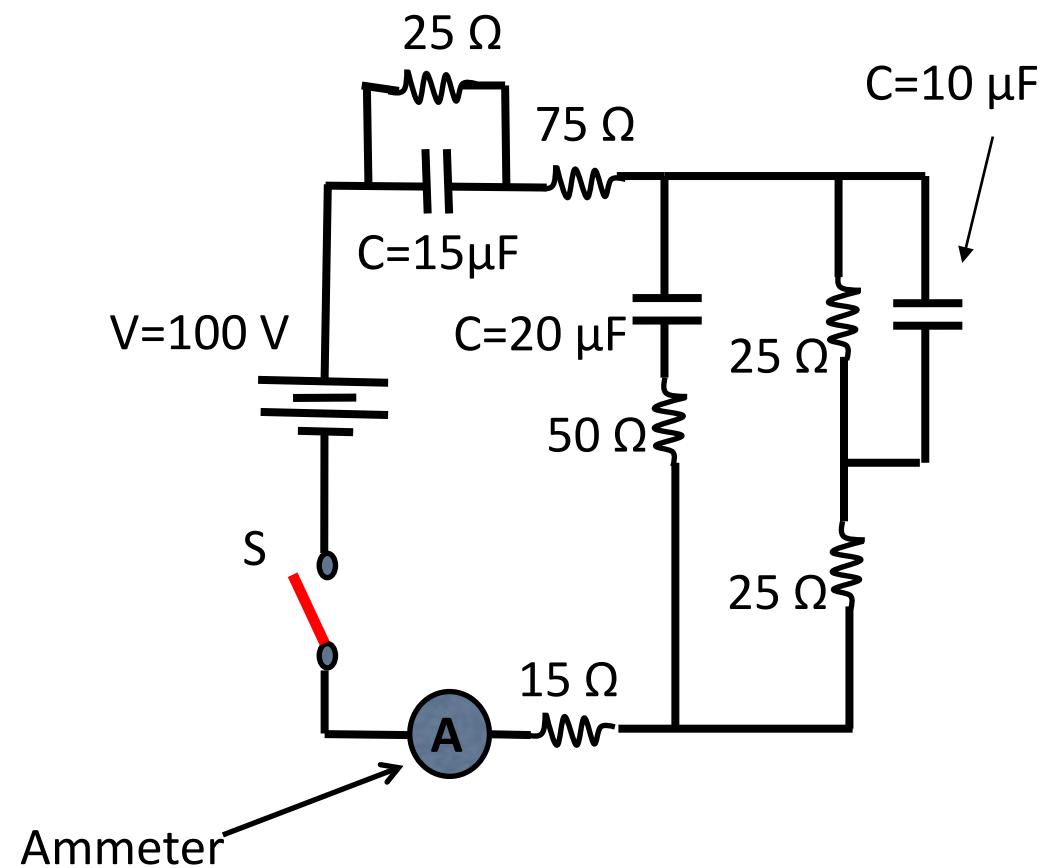- a) Redraw the circuit at $t = 0$
- b) Redraw the circuit at $t = \infty$



Q: All the capacitors in the circuit below are initially uncharged.

a) Find the current through the ammeter, $I_A(0+)$, just after the switch S is closed.

b) Find $I_A(\infty)$ a long time after the switch S has been closed.


• Right after the switch is closed, the capacitors **act as a wire!**

• Junction between an ideal wire and resistor =>
the resistor is short-cut

$$R_{eq} = 75 + \frac{50 \cdot 25}{50 + 25} + 15$$

$$= 106.7 \, \Omega$$
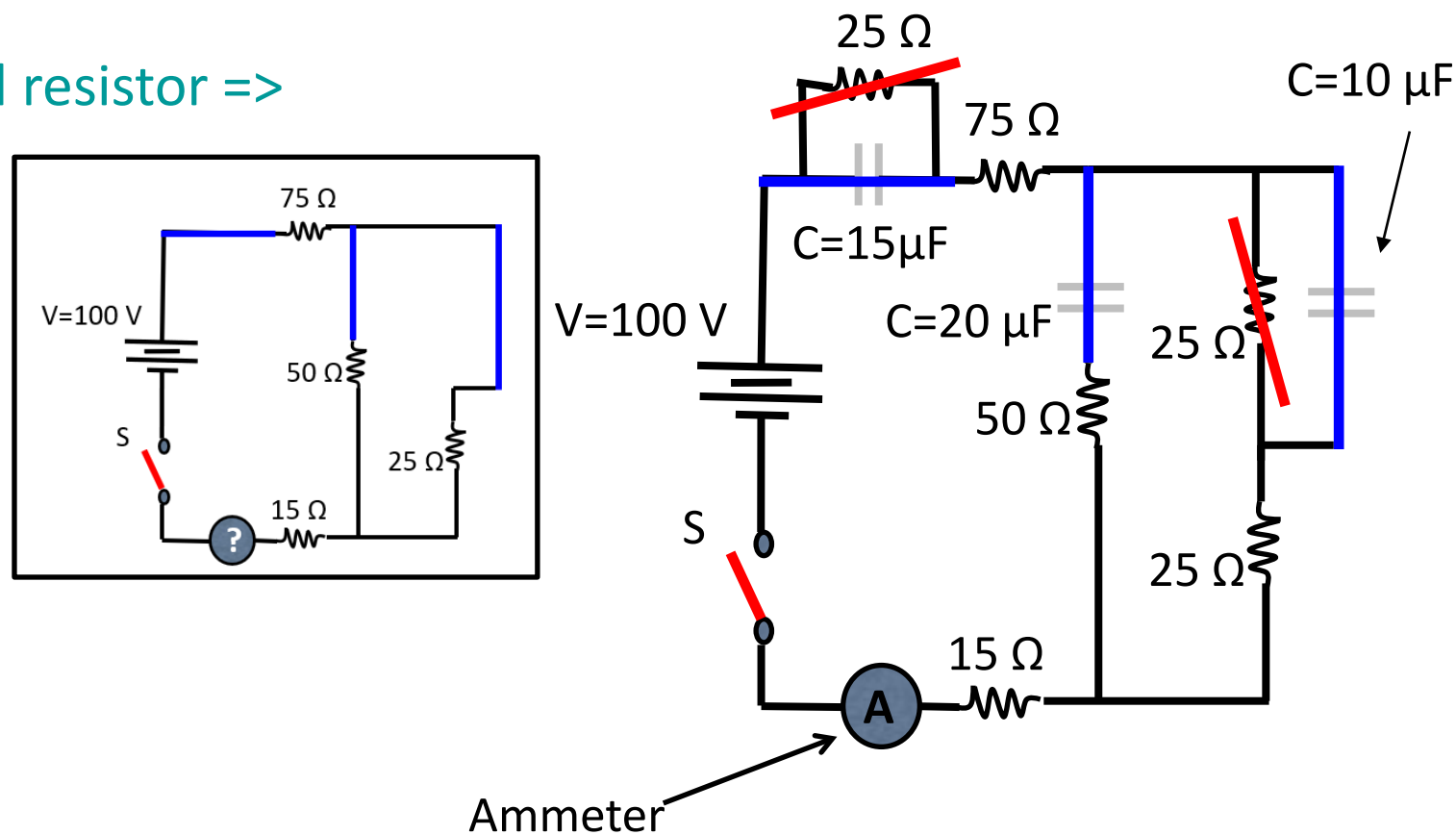
$$I_{tot}(0) = I_A = \frac{V}{R_{eq}} = 0.94 \, A$$



Q: All the capacitors in the circuit below are initially uncharged.


a) Find the current through the ammeter, $I_A(0+)$, just after the switch S is closed.

b) Find $I_A(\infty)$ a long time after the switch S has been closed.

- When a capacitor is fully charged, it does not let any charge to move around => it acts as an open switch!

$$R_{eq} = 25 + 75 + 25 + 25 + 15 \\ = 165 \Omega$$
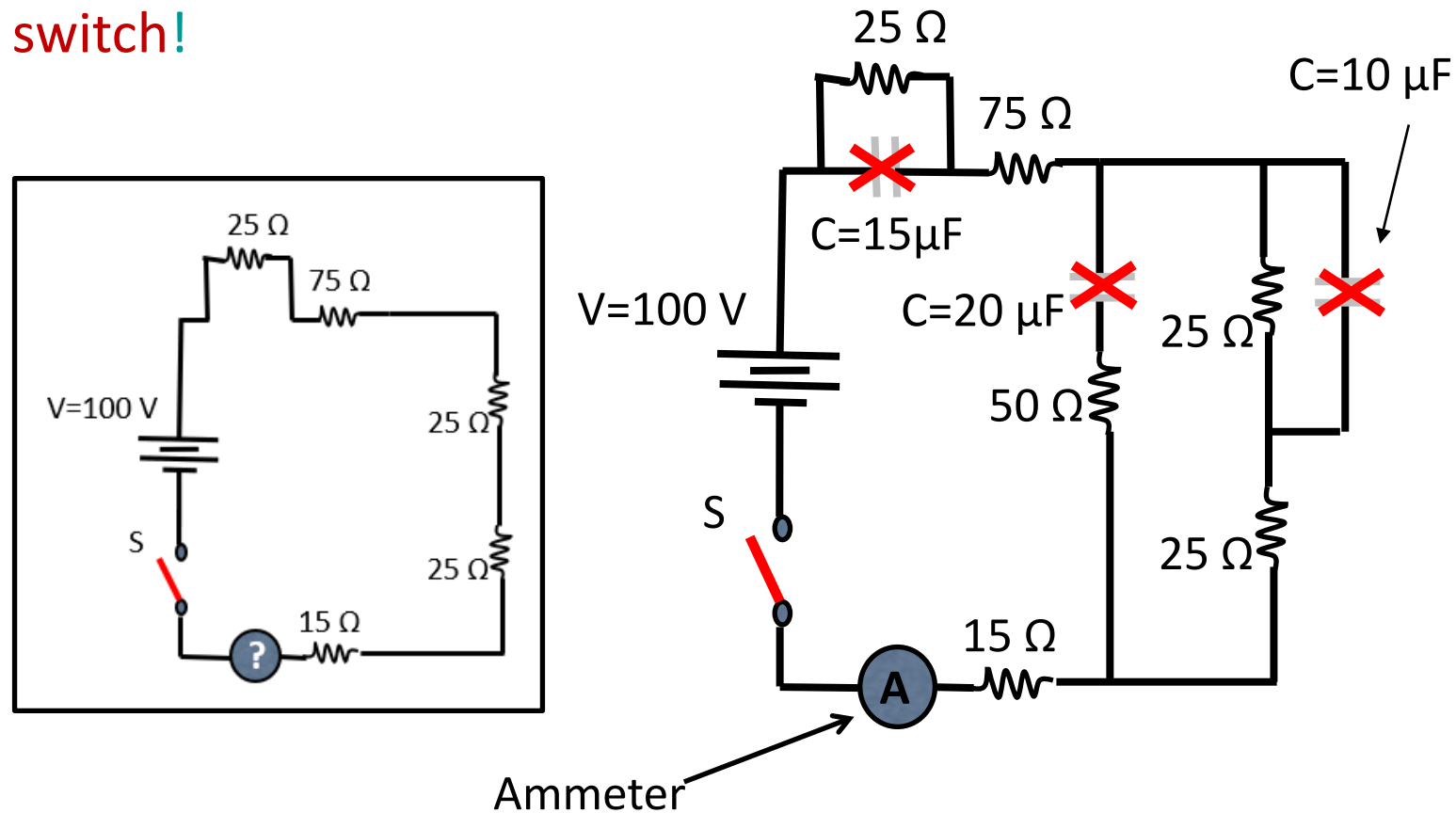
$$I_{tot}(\infty) = I_A = \frac{V}{R_{eq}} = 0.61 A$$



Summary

- Capacitors are circuit elements that store electric charge and electric energy. However, in circuits with dynamics they can “act as other circuit elements”:
 - Immediately after an empty capacitor is connected to a circuit, it acts as an ideal wire (there is no voltage drop across it)
 - After a capacitor is fully charged, it acts as an open switch (it does not accept more charge => no current flow around it)
- There is no voltage drop across a resistor if there is no current flowing through it (in a sense, it acts as an ideal wire)