

**Problem C2.1 (☆☆):** The capacitors shown left are both initially uncharged. The battery has  $V = 210 \text{ V}$  and the capacitances are  $C_1 = 3 \mu\text{F}$  and  $C_2 = 6 \mu\text{F}$ .

- (a) How much charge is drawn from the battery when the switch  $S_1$  is closed?


Equations we may need:

- Series capacitors:  $C_{eq} = \sum_k \frac{1}{C_k}$
- Parallel capacitors:  $C_{eq} = \sum_k C_k$

• Capacitor eqn:  $q = CV$   
Units:  $C = \text{F} \cdot \text{V}$

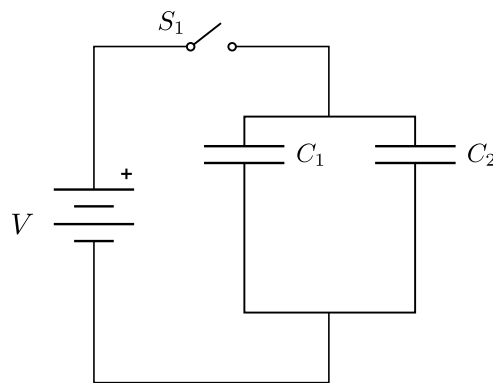
(a)  $C_{12} = (3 \mu\text{F} + 6 \mu\text{F}) = 9 \mu\text{F}$

$q_{12} = C_{12} V = (9 \mu\text{F})(210 \text{ V}) = \underline{1.89 \text{ mC}}$  ✓



Now an additional pair of capacitors is added to give the circuit diagram shown left.

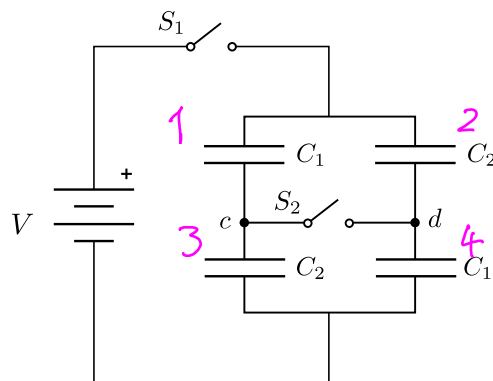- (b) How much charge is drawn from the battery now when the switch  $S_1$  is closed?  
(c) What is the potential difference across points  $c$  and  $d$ ?



(b)  $\frac{1}{C_{13}} = \frac{1}{C_{24}} = \frac{1}{C_1} + \frac{1}{C_3}$


∴  $C_{13} = \frac{1}{\left(\frac{1}{3 \mu\text{F}} + \frac{1}{6 \mu\text{F}}\right)} = 2 \mu\text{F}$

whilst  $S_2$  is open:

$q_{\text{tot}} = q_{13} + q_{24} = 2q_{13} = 2C_{13}V = 2(2 \mu\text{F})(210 \text{ V}) = 840 \mu\text{C}$

It is interesting to note that by adding two capacitors, we actually reduced the total charge drawn from the battery.

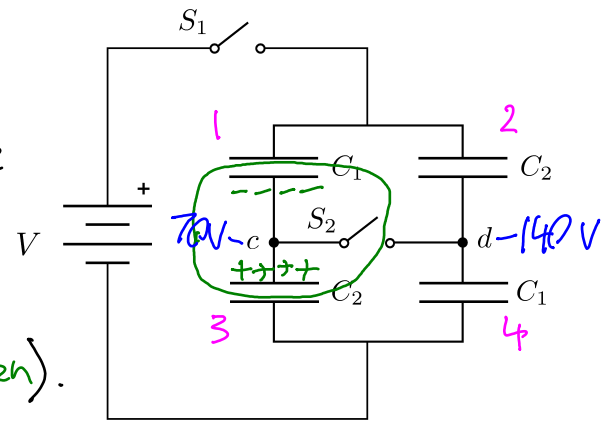(c) Capacitors in series have the same charge because the 2 plates connecting them must be neutral (see green).



$$\therefore q_1 = q_3 = q_{13} = 420 \mu\text{C}$$

$$q = CV \Rightarrow V_1 = \frac{q_1}{C_1} = \frac{420 \mu\text{C}}{3 \mu\text{F}} = 140 \text{V} = V_4$$

$$V_2 = \frac{q_2}{C_2} = \frac{420 \mu\text{C}}{6 \mu\text{F}} = 70 \text{V} = V_3$$


$$\therefore \Delta V_{cd} = V_c - V_d = \underline{\underline{-70 \text{V}}}$$

**Problem C2.1 (cont.):** Now the second switch  $S_2$  is closed.

(d) What is the potential difference across each capacitor?

(e) How much charge flowed across  $S_2$  when it was closed?

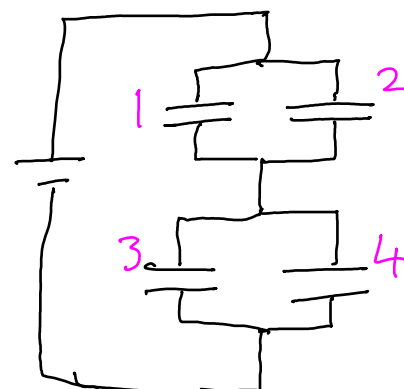(d) Now  $S_2$  has closed we can redraw our circuit as left.



Our equivalent capacitors are now the same as in part (a).

$$C_{13} = C_{24} = C_1 + C_3 = 9 \mu\text{F}$$

Because the equivalent capacitors are identical, we conclude that from symmetry:

$$V_{13} = V_{24} = \frac{V}{2} = \underline{105 \text{ V}}$$

(e) When  $S_2$  was open  $C_1$  &  $C_3$  had the same charge:

$$\Delta q = q_1 - q_3 = 0$$

when  $S_2$  was closed  $C_1$  &  $C_3$  have the same potential:


$$\Delta q = C_1 V_1 - C_3 V_3$$

$$= (3 \mu\text{F})(105 \text{ V}) - (6 \mu\text{F})(105 \text{ V})$$

$$= \underline{-315 \mu\text{C}}$$

So  $315 \mu\text{C}$  must have flowed across  $S_2$ .

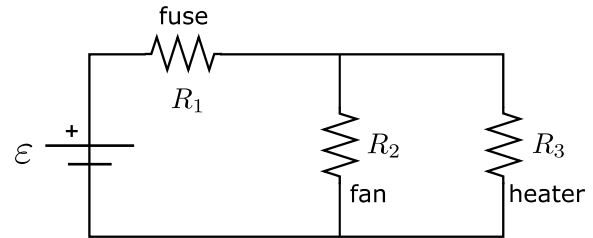**Problem C2.3 (☆☆):** Power sources used to feature a fuse\*, which is a small resistor (typically  $10\text{ m}\Omega$ ) that melts when the current drawn from the circuit becomes dangerous, thus breaking the circuit. Consider a standard  $120\text{ V}$  power socket, which is being used to power a hairdryer. The hairdryer uses a  $50\text{ W}$  fan and a  $1\text{ kW}$  heating element.




- (a) What is the resistance of the fan and the heating element, given their power output?
- (b) If the fuse melts after  $5\text{ J}$  of energy accumulation, how long would it take to melt with twice the operating current? Assume the fuse can dissipate  $1\text{ W}$  of heat.

(a) We will need Kirchhoff's laws:

KLR#1  $\mathcal{E} - I_1 R_1 - I_2 R_2 = 0$

KLR#2  $\mathcal{E} - I_1 R_1 - I_3 R_3 = 0$

KJR:  $I_1 = I_2 + I_3$

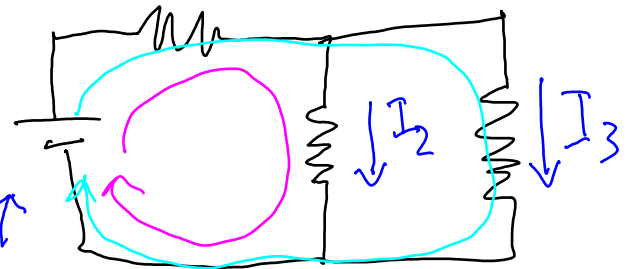

Whilst we don't know  $R_2$  or  $R_3$ , we do know their power, since  $P = VI = RI^2$ :

$$R_2 = \frac{P_2}{I_2^2} \quad \& \quad R_3 = \frac{P_3}{I_3^2}$$

Solving Kirchhoff's laws:

$$\mathcal{E} - I_1 R_1 - I_2 \frac{P_2}{I_2^2} = 0 \Rightarrow I_2 = \frac{P_2}{\mathcal{E} - I_1 R_1}$$

\*Modern circuit breakers use electromagnetics to open a switch when the current becomes too high and are thus reusable. We will learn how electromagnets can do this later in the course.

(a) Similarly  $I_3 = \frac{P_3}{\mathcal{E} - I_1 R_1}$

$$\therefore I_1 = \frac{P_2 + P_3}{\mathcal{E} - I_1 R_1} \Rightarrow R_1 I_1^2 - \mathcal{E} I_1 + (P_2 + P_3) = 0$$

This quadratic has 2 solutions:

$$I_1 = 8.756 \text{ A or } 11.991 \text{ A}$$

The second solution is unphysical and blows up to  $\infty$  as  $R_1 \rightarrow 0$ . Hence we discard it.

$$\therefore I_2 = 0.417 \text{ A} \Rightarrow \underline{R_2 = 288 \Omega}$$

$$I_3 = 8.340 \text{ A} \Rightarrow \underline{R_3 = 14.4 \Omega}$$

(b) Operating current is  $I_1 = 8.76 \text{ A}$ . So heat produced at  $2I_{op}$ :

$$P_{melt} = R_1 (2I_{op})^2 = 3.067 \text{ W}$$

But fuse can dissipate 1 w. So net heat buildup is:

$$P_{net} = P_{melt} - 1 = \frac{\Delta E}{\Delta t}$$

$$\therefore \Delta t_{melt} = \frac{\Delta E}{P_{net}} = \frac{5 \text{ J}}{2.067 \text{ W}} \frac{\cancel{\text{J}}}{\cancel{\text{J/s}}} \checkmark = \underline{2.419 \text{ s}}$$