

## Lecture 5.

Energy stored in capacitors: practice.

Capacitors and switches.


RC-circuits (intro).

# Last Time:

$$Q = C\Delta V_c$$

- $C$ : capacitance

- Charging a capacitor

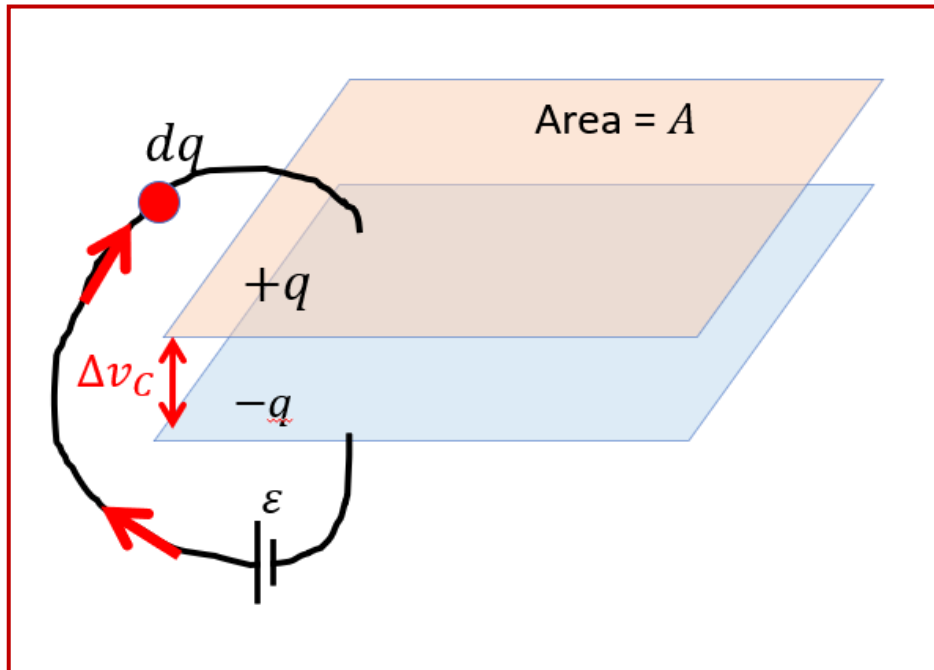

- Energy stored:



$$U_c = \frac{Q_f^2}{2C} = \frac{C\Delta V_f^2}{2}$$

$$Q_f = C \Delta V_f$$

- $Q_f$ : final charge at the plates
- $V_f$ : final voltage across the plates

Q: Rank the three capacitors according to their stored energy.
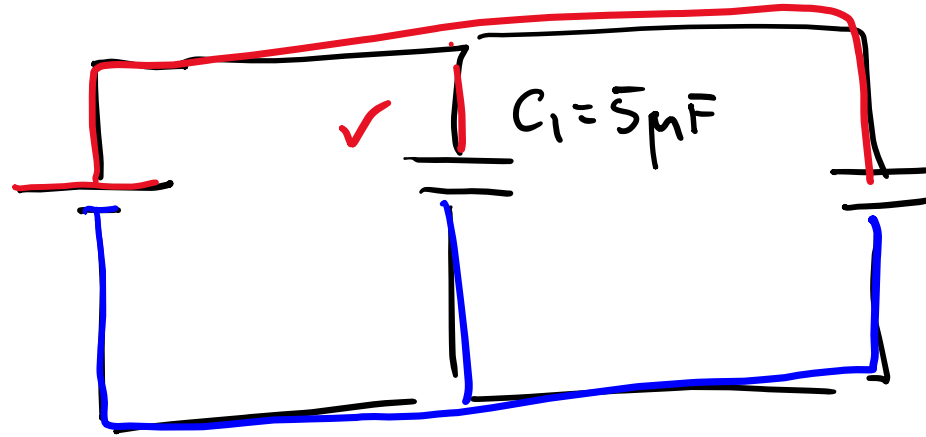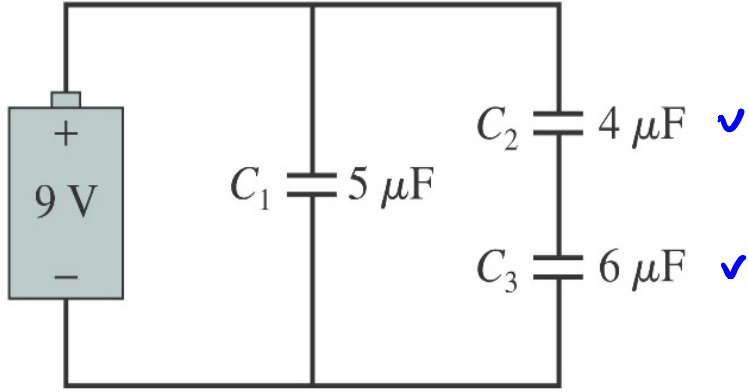
$$U_c = \frac{Q^2}{2C} = \frac{C(\Delta V_c)^2}{2}$$





$$C_{23} = \frac{6 \cdot 4}{6 + 4} = 2.4 \mu\text{F}$$

- A.  $U_1 > U_2 > U_3$
- B.  $U_3 > U_1 > U_2$
- C.  $U_1 > U_2 = U_3$
- D.  $U_2 > U_3 > U_1$
- E.  $U_1 > U_3 > U_2$

$$U_c = \frac{Q^2}{2C}$$

Q: Rank the three capacitors according to their stored energy.
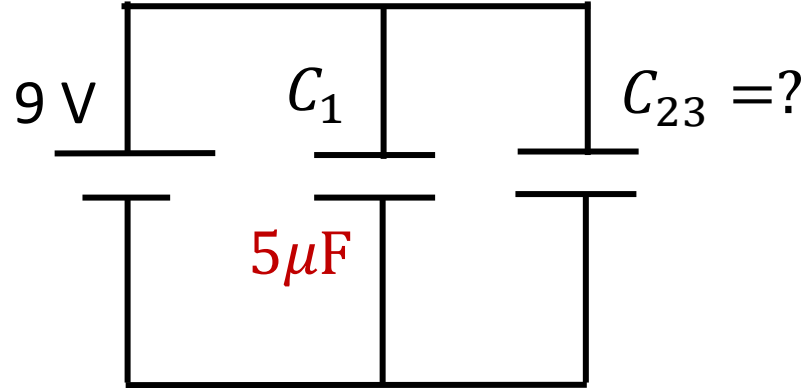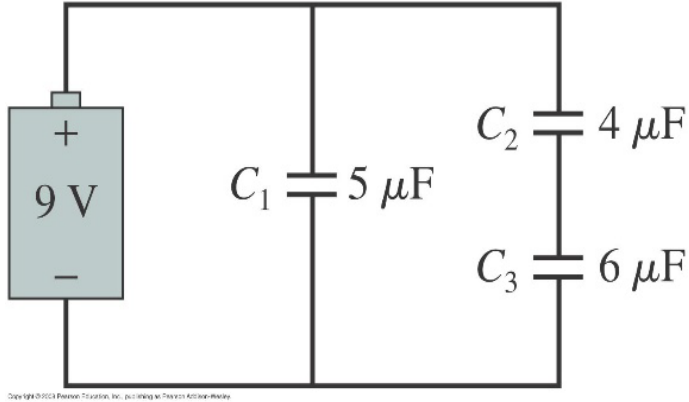
$$U_c = \frac{Q^2}{2C} = \frac{C(\Delta V_c)^2}{2}$$




$$C_{23} = \frac{4 \cdot 6}{(4 + 6)} = 2.4 \mu\text{F}$$

- A.  $U_1 > U_2 > U_3$
- B.  $U_3 > U_1 > U_2$
- C.  $U_1 > U_2 = U_3$
- D.  $U_2 > U_3 > U_1$
- E.  $U_1 > U_3 > U_2$

- $U_1 > U_{23}$ , using  $U_c = \frac{C(\Delta V_c)^2}{2}$  (since they have the same  $\Delta V_c$ , and we only need to compare  $C_1$  and  $C_{23}$ )
- $U_1$  is the largest of all. How we can compare  $U_2$  and  $U_3$ ?
- $U_2 > U_3$ , using  $U_c = \frac{Q^2}{2C}$  (since they have the same  $Q$  and we only need to compare  $C_2$  and  $C_3$ )


Q: Exercise, on your own: calculate the energies explicitly.
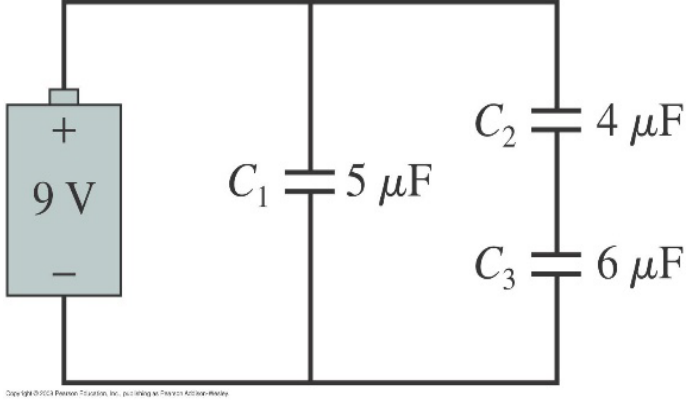
$$U_c = \frac{Q^2}{2C} = \frac{C(\Delta V_C)^2}{2}$$




Answer:  $U_1 = 203\ \mu\text{J}$ ;  $U_2 = 58\ \mu\text{J}$ ;  $U_3 = 39\ \mu\text{J}$

## Circuits with switches

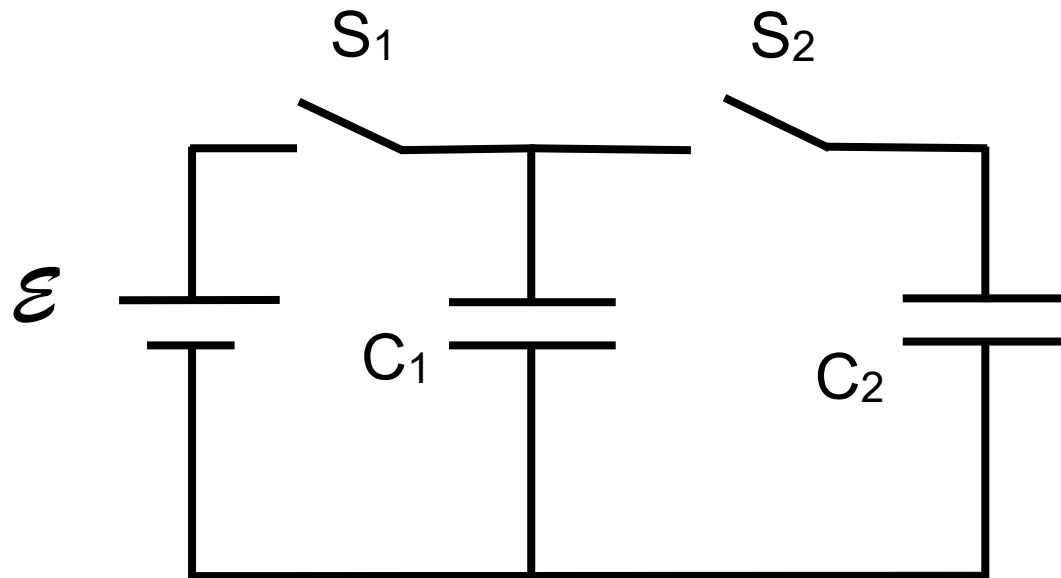

**Switches** change the characteristics of a circuit by providing or removing paths for current

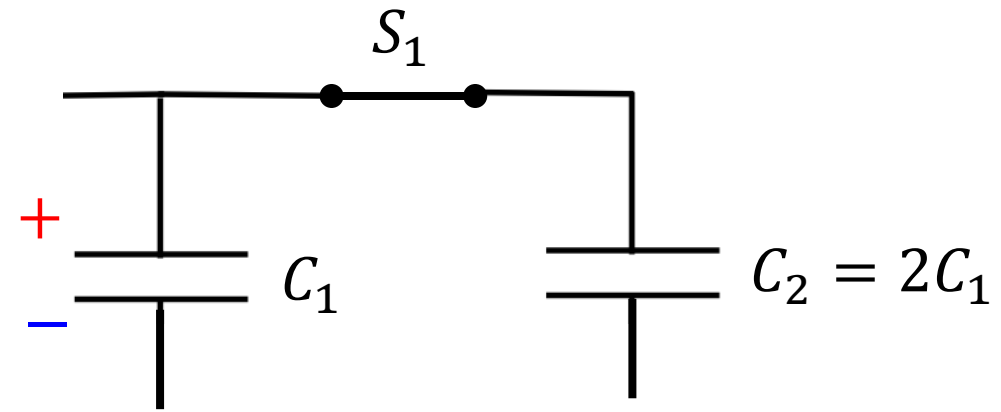Q: A Physics 159 student has wired the circuit below. Suppose  $C_1$  has charge  $Q$ , and  $C_2$  has charge  $= 0$  before the switch  $S_1$  is closed.




After  $S_1$  is closed the final charges on  $C_1$  and  $C_2$  are:

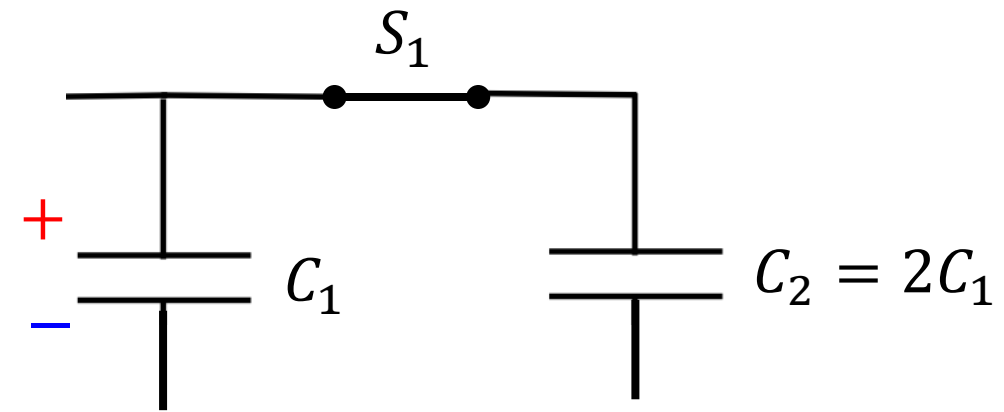
- A.  $Q_1 = Q/2, \quad Q_2 = Q/2$
- B.  $Q_1 = 0, \quad Q_2 = +Q$
- C.  $Q_1 = Q/4, \quad Q_2 = 3Q/4$
- D.  $Q_1 = Q, \quad Q_2 = 0$
- E. None of the above

Q: A Physics 159 student has wired the circuit below. Suppose  $C_1$  has charge  $Q$ , and  $C_2$  has charge  $= 0$  before the switch  $S_1$  is closed.

- The positive charges on the top plate repel each other and “want” to spread, but they are attracted by the negative charges at the bottom plate, which are “locked” at the lower plate if the bottom plates are not connected.



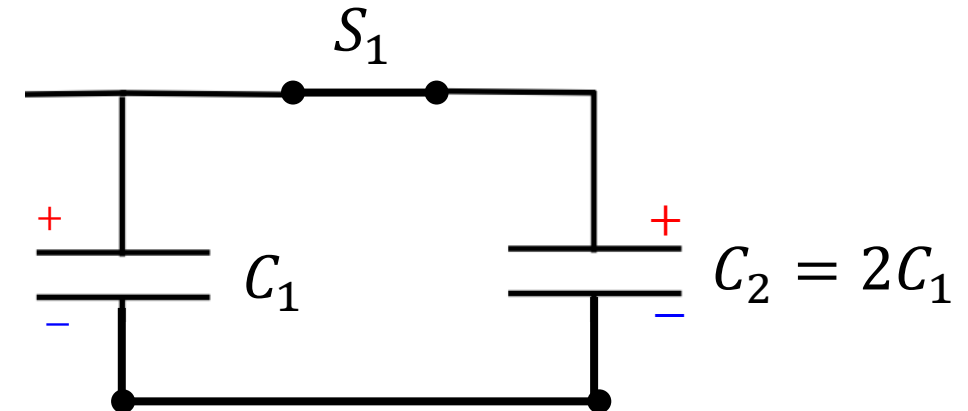- What happens if we close the circuit by connecting bottom plates?
- Now both + and – can spread over the two capacitors => the second capacitor gets charged!




After  $S_1$  is closed the final charges on  $C_1$  and  $C_2$  are:

- A.  $Q_1 = Q/2, Q_2 = Q/2$
- B.  $Q_1 = 0, Q_2 = +Q$
- C.  $Q_1 = Q/4, Q_2 = 3Q/4$
- ☒ D.  $Q_1 = Q, Q_2 = 0$
- E. None of the above



Q: Initially both capacitors are uncharged, switches are open. The following procedure is then performed:

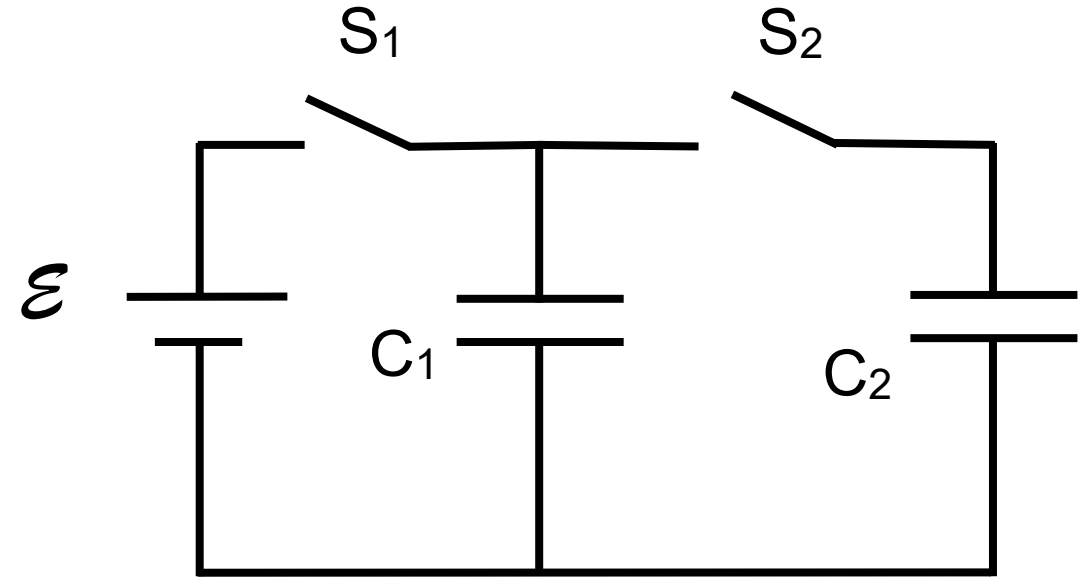1. Switch  $S_1$  is closed for a long time.
2. Switch  $S_1$  is opened.
3. Switch  $S_2$  is closed.




- a) What happens right after step 3, i.e. when switch  $S_2$  is closed? Explain.
- b) What is conserved in step 3? Explain.
- c) Calculate the final charges on both  $C_1$ . Use  $\mathcal{E} = 24\text{ V}$ ,  $C_1 = 2\text{ }\mu\text{F}$  and  $C_2 = 1\text{ }\mu\text{F}$ .

Q1: What is conserved in Step 3 (when  $S_2$  is closed)?

- A. Energy and Charge
- B. Energy
- C. Charge
- D. Voltage
- E. Voltage and Energy

Q2: After  $S_2$  is closed and new equilibrium is reached, what is true about the two capacitors?

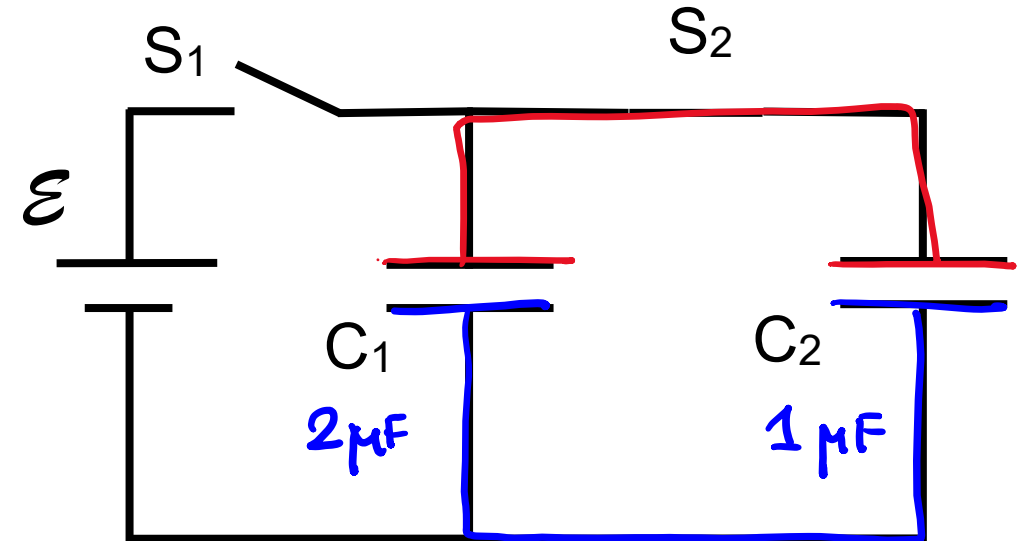- A. They must have the same charge across them
- B. They must have the same energy
- ☒ C. The voltage across them is the same ✓
- D. More than one is true



Q1: What is conserved in Step 3 (when  $S_2$  is closed)?

A. Energy and Charge

B. Energy

☒ C. Charge

D. Voltage

E. Voltage and Energy

- Net charge is always conserved (law of Nature).
- Whether or not energy conserves is to be verified (we are changing the system by closing the switch!)


Q2: After  $S_2$  is closed and new equilibrium is reached, what is true about the two capacitors?

A. They must have the same charge across them

B. They must have the same energy

☒ C. The voltage across them is the same


D. More than one is true

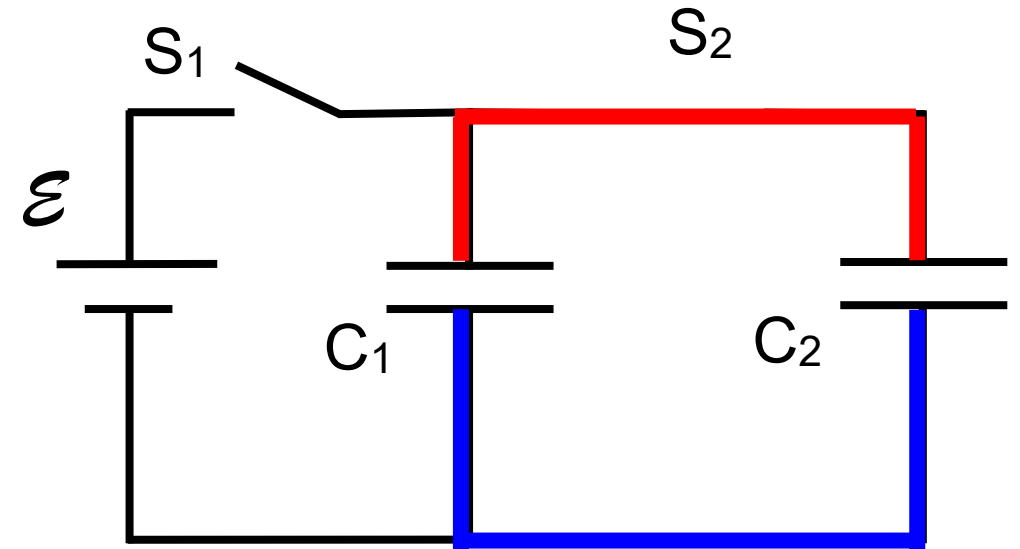

Q: The final charges  $Q_{1f}$  and  $Q_{2f}$  on  $C_1$  and  $C_2$  are:

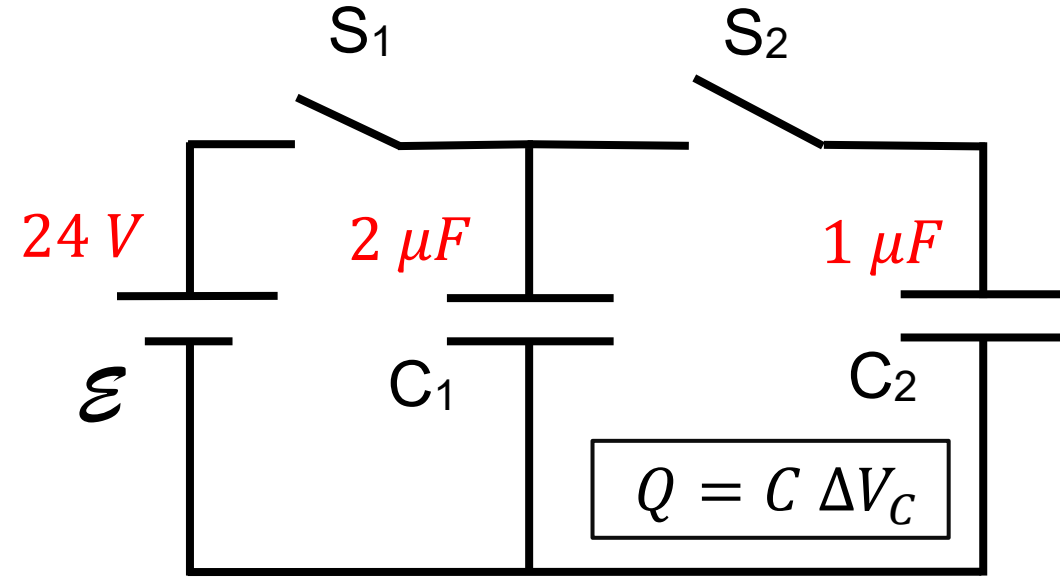- A.  $48\ \mu\text{C}$ ,  $48\ \mu\text{C}$
- B.  $24\ \mu\text{C}$ ,  $24\ \mu\text{C}$
- C.  $40\ \mu\text{C}$ ,  $20\ \mu\text{C}$
- D.  $48\ \mu\text{C}$ ,  $24\ \mu\text{C}$
- E.  $32\ \mu\text{C}$ ,  $16\ \mu\text{C}$

$$Q_i = C_1 \mathcal{E} = 48\ \mu\text{C}$$



Q: The final charges  $Q_{1f}$  and  $Q_{2f}$  on  $C_1$  and  $C_2$  are:

A.  $48 \mu\text{C}$ ,  $48 \mu\text{C}$

B.  $24 \mu\text{C}$ ,  $24 \mu\text{C}$

C.  $40 \mu\text{C}$ ,  $20 \mu\text{C}$

D.  $48 \mu\text{C}$ ,  $24 \mu\text{C}$


**E.  $32 \mu\text{C}$ ,  $16 \mu\text{C}$**

• **Step 1:**  $C_1$  is charged to:

$$Q_{1i} = (2 \mu\text{F})(24\text{V}) = 48 \mu\text{C},$$

and  $Q_{2i} = 0$  (disconnected).

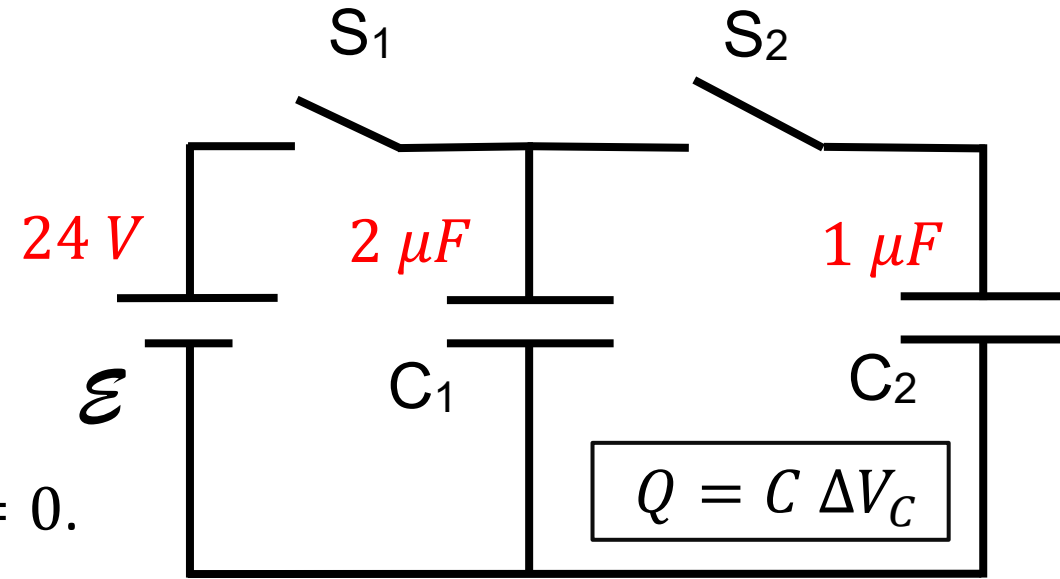• **Hence:**  $Q_{1i} = 48 \mu\text{C}$  and  $Q_{2i} = 0$ .



• **Step 2:** Charge is always conserved (Total charge before) = (Total charge after)

$$Q_{1f} + Q_{2f} = 48 \mu\text{C}$$

$$\frac{Q_{1f}}{C_1} = \frac{Q_{2f}}{C_2}$$

$Q_1 = 32 \mu\text{C}$   
 $Q_2 = 16 \mu\text{C}$

$$Q_{1i} + Q_{2i} = Q_{1f} + Q_{2f} = 48 \mu\text{C}$$

eq (1)

$$\Delta V_f = \frac{Q_{1f}}{C_1} = \frac{Q_{2f}}{C_2} \quad \text{eq (2)}$$

Two unknowns:  
 $Q_{1f}$  and  $Q_{2f}$

• **Note:** the **final voltage** is the same on  $C_1$  and  $C_2$ . If we call it  $\Delta V_f$ :

$$Q_{1f} + Q_{2f} = C_1 \Delta V_f + C_2 \Delta V_f = 48 \mu\text{C} \quad \Rightarrow \quad \Delta V_f = (48 \mu\text{C}) / (C_1 + C_2) = 16 \text{V}$$

• **We get:**  $Q_{1f} = C_1 \Delta V_f = (2 \mu\text{F})(16 \text{V}) = 32 \mu\text{C}$  and  $Q_{2f} = C_2 \Delta V_f = (1 \mu\text{F})(16 \text{V}) = 16 \mu\text{C}$

→ **alternative solution for  $Q_{1f}$  and  $Q_{2f}$**

## What about the energy?

- So  $\Delta V_i = \varepsilon = 24 \text{ V}$ , and  $\Delta V_f = \frac{48 \mu\text{C}}{3 \mu\text{F}} = 16 \text{ V}$

- Electrical Energy =  $U_c = \frac{C \Delta V_c^2}{2}$   $\frac{(48 \mu\text{C})^2}{2 (2 \mu\text{F})}$


$$U_i = \frac{C_1 \Delta V_{1i}^2}{2} = \frac{(2 \mu\text{F})(24 \text{ V})^2}{2} = 576 \mu\text{J} \quad (\text{initially there is no charge on } C_2)$$

$$U_f = \frac{C_1 \Delta V_{1f}^2}{2} + \frac{C_2 \Delta V_{2f}^2}{2} = \frac{(2 \mu\text{F} + 1 \mu\text{F})(16 \text{ V})^2}{2} = 384 \mu\text{J} \quad (\text{parallel combination})$$

$$\frac{(32 \mu\text{C})^2}{2 (2 \mu\text{F})} + \frac{(16 \mu\text{C})^2}{2 (1 \mu\text{F})}$$

$U_i$  is not equal to  $U_f$ !

Q: Where did the missing energy go?

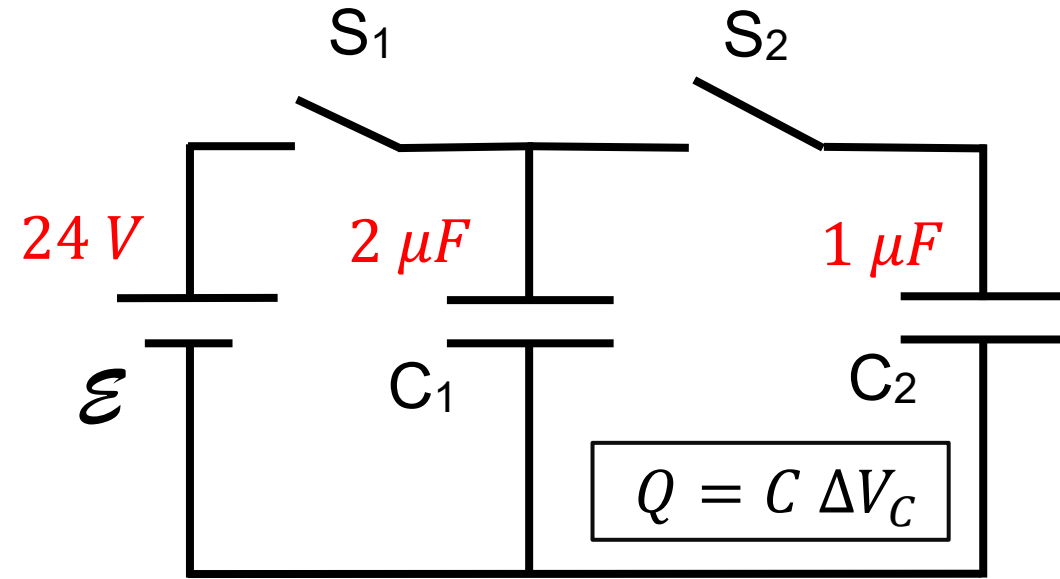

## Q: Where did the missing energy go?

Quoting from Wikipedia: “This problem has been discussed in electronics literature at least as far back as 1955.” In short:

- A model of a circuit with two capacitors and zero-resistance-wires is a bit “too ideal”. Though **it gives us correct predictions about the distribution of charges, voltages and stored energies**, it cannot explain where the energy goes. It also predicts infinite current when the switch is closed – unphysical!
- To remedy the situation, we need to account for small (but generally non-zero) **resistance in wires**. Then we can state that the missing energy was converted to **heat** and emitted as electromagnetic waves.
- This nicely brings us to the topic of RC-circuits (circuits with capacitors and resistors) which we are going to switch now.

$$\Delta V = IR \rightarrow I = \frac{\Delta V}{0} = \infty!$$

Time-dependent DC circuits



Time-dependent DC circuits: RC-circuits

Text: 26.4


- Charging a capacitor
- Discharging a capacitor
- Time constant ( $\tau = RC$ )



## Combining elements - **RC circuits** + switch

- Thus far we have considered only steady and continuous currents. However, many important circuit applications use combination of capacitors and resistors (and inductors) to produce **time-dependent** currents.
- **Examples:** Intermittent car wipers, filtering (or 'cleaning') wireless signals in a cordless phone, remote control, etc.

### Simple RC Series Circuit

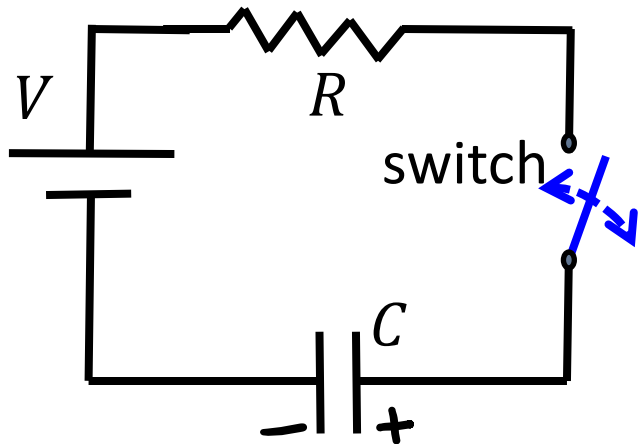


- When the switch is open:
  - No current can flow in the circuit.
  - The **charge** on the capacitor and the **voltage** across it both remain zero ( $\Delta V_C = Q/C$ ).
- After the switch has been closed for a very long time:
  - Charge on the capacitor is  $Q = CV$
  - Again, no current flows in the circuit (capacitor does not accept more charge).
- Intermediate times:
  - **Dynamics!**  $I \Rightarrow i(t)$ : current depends on time


## CASE 1: Charging a capacitor - 1

Switch is open until  $t = 0$

Initial charge  $q_c(t = 0) = 0$

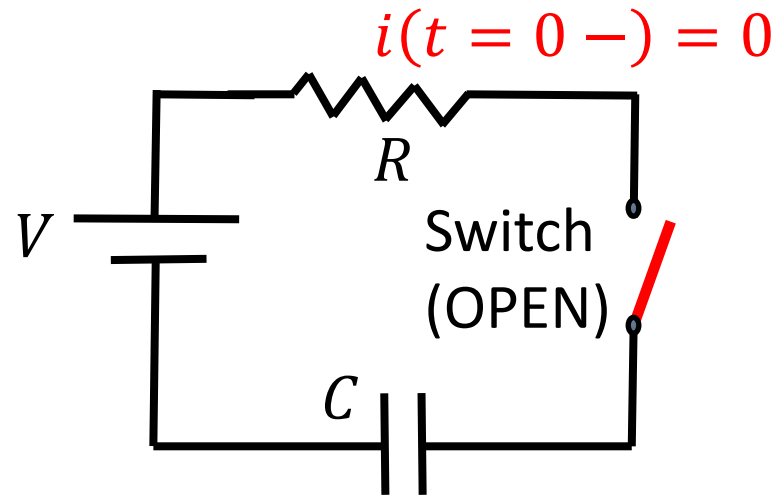

Switch is suddenly closed at  $t = 0 +$

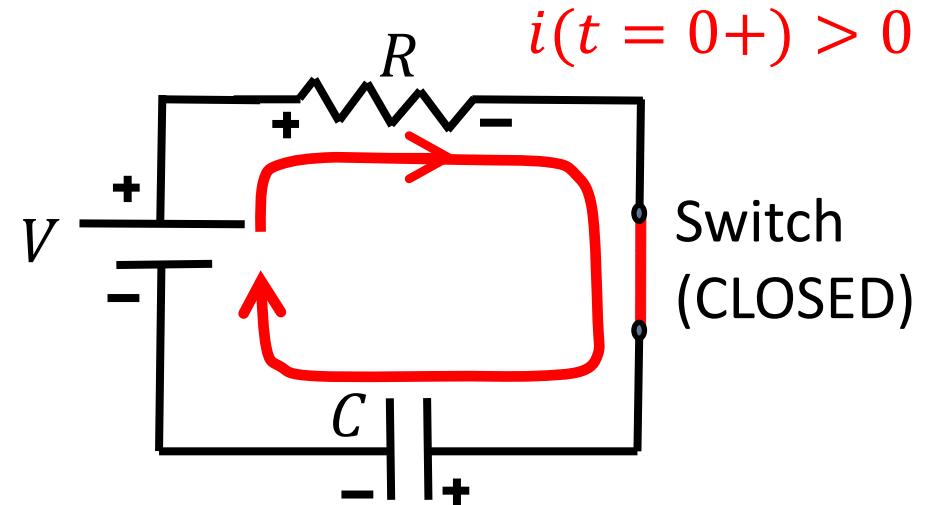


- Once the switch is closed, current starts flowing in the circuit.
- Electric charges cannot propagate through the empty space between capacitor's plates. However, what happens is that **the capacitor is charging**: battery is delivering charges to one plate and removes them from the other **as if** the current is passing through the capacitor.


## CASE 1: Charging a capacitor - 2

Switch is open until  $t = 0$

Initial charge  $q_c(t = 0) = 0$

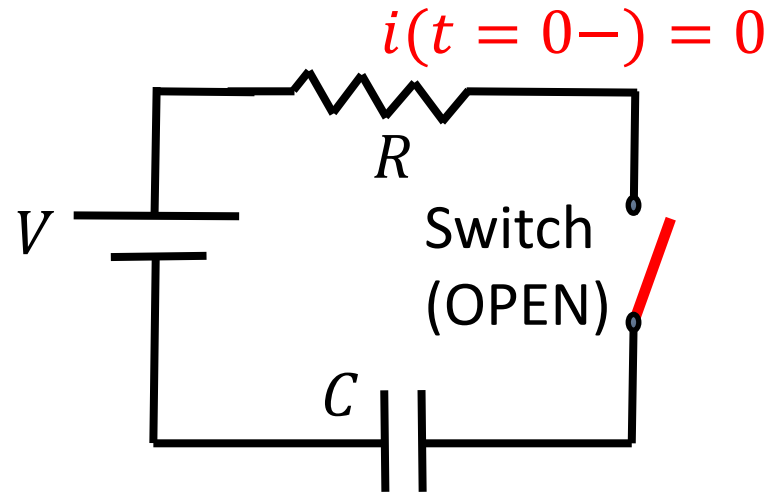

Switch is suddenly closed at  $t = 0 +$

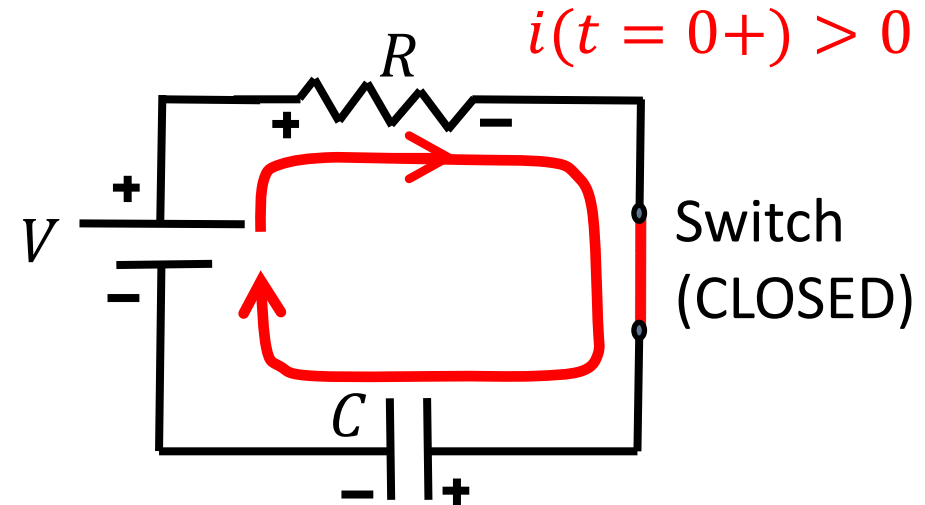

- Voltage drop across a capacitor:

➤ Magnitude:  $\Delta V_c = \frac{q}{C}$  with  $q = q(t) \Rightarrow$  hence  $\Delta V_c = \Delta V_c(t)$

➤ Sign: voltage is higher at the plate that carries positive charge

- Note that **immediately after the switch is closed**, the capacitor acts like an ideal wire (short circuit). There is no charge on the capacitor so  $\Delta V_c = 0$  and  $i(0+) = V/R$

## CASE 1: Charging a capacitor - 3

- Kirchhoff loop law (travel CW):

$$V - iR - \frac{q}{C} = 0$$


- Let's take time derivative:

$$0 - R \frac{di}{dt} - \frac{1}{C} \frac{dq}{dt} = 0$$

- Note that:  $\boxed{\frac{dq}{dt} = i,}$  hence:  $\boxed{-R \frac{di}{dt} - \frac{i}{C} = 0.}$

Initial charge  $q_c(t = 0) = 0$

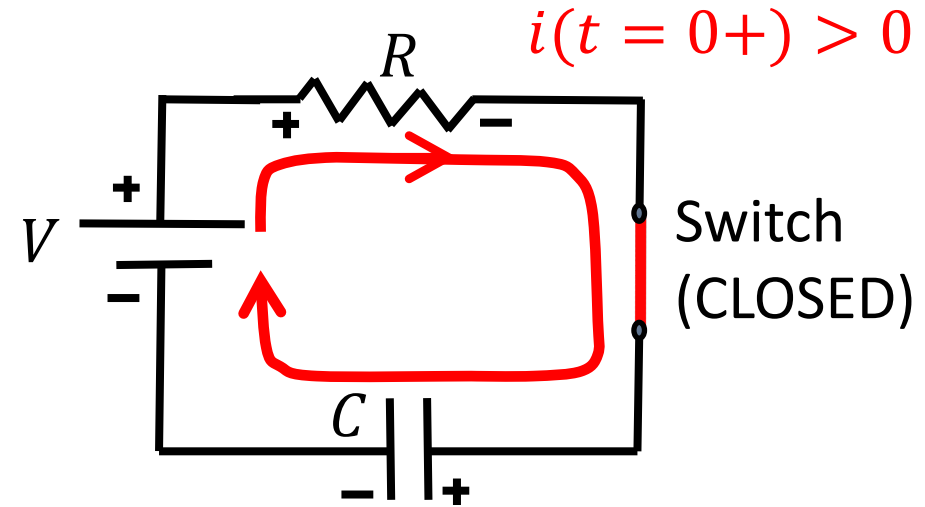Switch is suddenly  
closed at  $t = 0 +$



- Here we take  $\frac{dq}{dt} = +i$  since current  $i$  brings + charge to the positive plate => charge on the plates increases =>  $\frac{dq}{dt} > 0$ .

- We have got a differential equation for  $i(t)$ , and a connection between  $q(t)$  and  $i(t)$