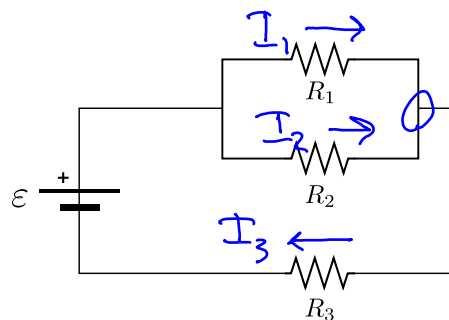


Problem C1.1 (☆): the diagram to the left depicts a circuit where the components have $R_1 = 2\ \Omega$, $R_2 = 6\ \Omega$, and $R_3 = 4\ \Omega$. The current through R_2 is $I_2 = 0.8\text{ A}$.

(a) What are the currents I_1 and I_3 ?

(b) What is the EMF of the battery?



Some equations we may need:

• Ohm's law: $V = IR$

• Kirchhoff's loop rule: $\sum_k V_k = 0$

• Kirchhoff's Junction rule: $\sum_k I_k = 0$

(a) R_1 & R_2 in parallel. $\therefore V_1 = V_2$

$$\therefore I_1 R_1 = I_2 R_2 \Rightarrow I_1 = \frac{I_2 R_2}{R_1} = \frac{(0.8\text{ A})(6\ \Omega)}{2\ \Omega} = \underline{\underline{2.4\text{ A}}}$$

For I_3 , we can use Kirchhoff's Junction rule:


$$\begin{array}{c} I_1 \downarrow \\ \uparrow I_2 \end{array} \rightarrow I_3 \Rightarrow I_3 = I_1 + I_2 = \underline{\underline{3.2\text{ A}}}$$

(b) Drawing a Kirchhoff loop law:

$$\mathcal{E} - I_2 R_2 - I_3 R_3 = 0$$

$$\mathcal{E} = I_2 R_2 + I_3 R_3$$

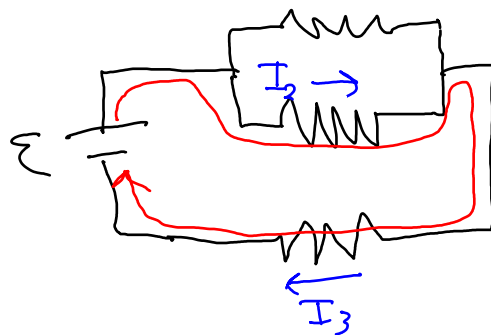
$$= (0.8\text{ A})(6\ \Omega) + (3.2\text{ A})(4\ \Omega) = \underline{\underline{17.6\text{ V}}}$$



Unit check:

$$V = IR \Rightarrow V = \text{A}\Omega \quad \checkmark$$

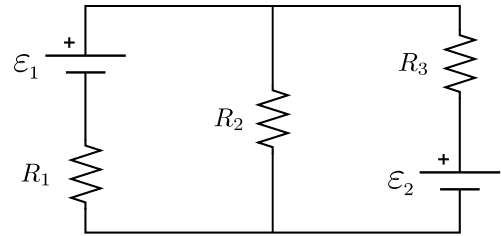Problem C1.2 (☆): the diagram to the left depicts a circuit with where the components have resistance $R_1 = 4 \Omega$, $R_2 = 8 \Omega$, and $R_3 = 6 \Omega$ and batteries have emf $\mathcal{E}_1 = 12 V$ and $\mathcal{E}_2 = 6 V$.




- (a) What is the current through resistor R_2 ?
 (b) Are both batteries discharging, or is one charging the other? If so which one?

Some equations we may need:

- Kirchhoff's loop rule: $\sum_k V_k = 0$ • Kirchhoff's junction rule: $\sum_k I_k = 0$

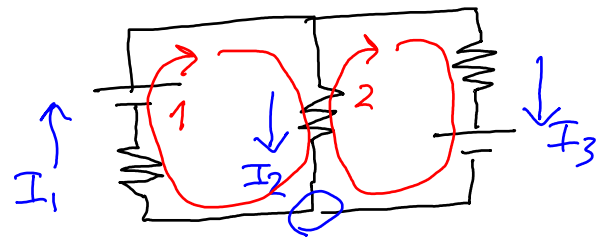- (a) To work out how the batteries combine, we need to use 3 Kirchhoff laws to determine 3 unknowns: the branch currents.



We can guess their directions:

KLR #1: $\mathcal{E}_1 - I_2 R_2 - I_1 R_1 = 0$ ①

KLR #2: $+I_2 R_2 - I_3 R_3 - \mathcal{E}_2 = 0$ ②

KJR: $I_2 + I_3 = I_1$ ③

From ①: $I_1 = \frac{1}{R_1} (\mathcal{E}_1 - I_2 R_2)$ From ②: $I_3 = \frac{1}{R_3} (I_2 R_2 - \mathcal{E}_2)$

Sub ③: $\therefore I_2 \left(1 + \frac{R_2}{R_3} + \frac{R_2}{R_1} \right) - \frac{\mathcal{E}_1}{R_1} - \frac{\mathcal{E}_2}{R_3} = 0$

$$I_2 = \frac{\left(\frac{12V}{4\Omega} + \frac{6V}{6\Omega} \right)}{\left(1 + \frac{8\Omega}{6\Omega} + \frac{8\Omega}{4\Omega} \right)} = 0.923 A$$

A positive answer means we guessed right for I_2 .

Problem C1.2 cont:

(b) To determine whether the batteries are charging, we need to work out the direction of I_2 & I_3 :

From ①: $I_1 = \frac{1}{R_1} (\mathcal{E}_1 - I_2 R_2) = \frac{1}{4\Omega} (12V - (0.923A)(8V)) = 1.15 A$

From ②: $I_3 = \frac{1}{R_3} (I_2 R_2 - \mathcal{E}_2) = \frac{1}{6\Omega} ((0.923A)(8V) - 6V) = 0.231 A$

Thus we guessed right for both I_1 and I_3 because our answers are positive.

Thus \mathcal{E}_1 is discharging because current is flowing from +ve to -ve terminal.

However \mathcal{E}_2 is charging, as current is flowing into the +ve terminal.