

Lecture 10.

AC circuits and how to deal with them.
Phasors. Impedance.

AC circuits

Text: 31.1-6

- Ch 30.1: Sinusoidal alternating $v(t)$ and $i(t)$, Phasors, RMS values
- Ch 31.2: AC circuits with R, L, C
- Ch 31.3: AC L-R-C series circuit:
- Ch 31.4: Power in AC circuits:
- Ch 31.5: Resonance in AC circuits

AC circuits

- The electrical voltage/current delivered to our houses oscillates at 60Hz
- In much of the rest of the world, electrical AC power is delivered at 50Hz



AC power for
home or
industrial use




NOTE: AC circuits are not limited to 60Hz (or 50Hz) !!

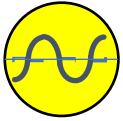Examples: AM/FM radio stations (AM~500kHz, FM~100MHz);

Audio, Television, and all other telecommunications range from 100 Hz to 10^9 Hz

Voltage in an AC circuits: Root-Mean-Square average




- AC source produces alternating voltage:

$$v(t) = V_{\max} \cos(\omega t)$$

- It's time average value is zero ☹

v

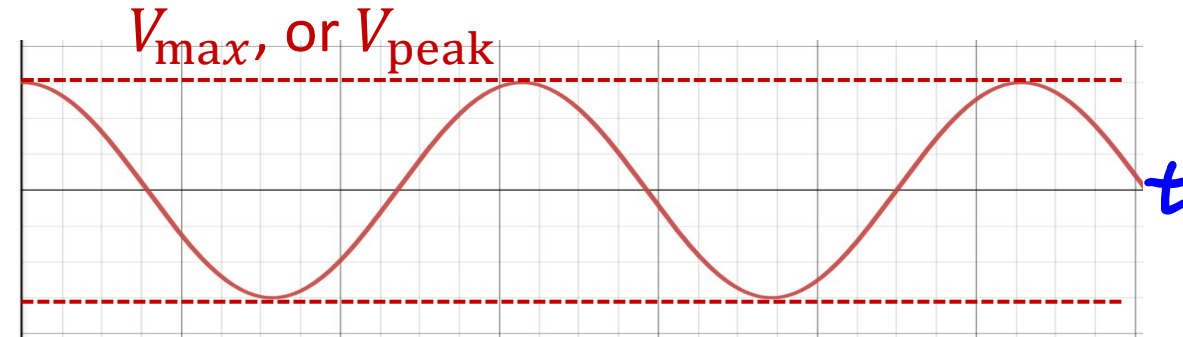

- The time average of $v^2(t) = V_{\max}^2 \cos^2(\omega t)$ is not zero! ☺





$$\begin{aligned} \bullet \langle f(t) \rangle &= \frac{1}{T} \int_0^T f(t) dt \\ \bullet V_{rms}^2 &= \frac{V_{\max}^2}{T} \int_0^T \cos^2(\omega t) dt = \frac{V_{\max}^2}{T} \cdot \frac{T}{2} = \frac{V_{\max}^2}{2} \end{aligned}$$

- Physical meaning: in AC circuits, ammeter and voltmeter read RMS, not instantaneous or peak values

$$V_{rms} = \sqrt{\langle v^2(t) \rangle_t} = \frac{V_{\max}}{\sqrt{2}}$$

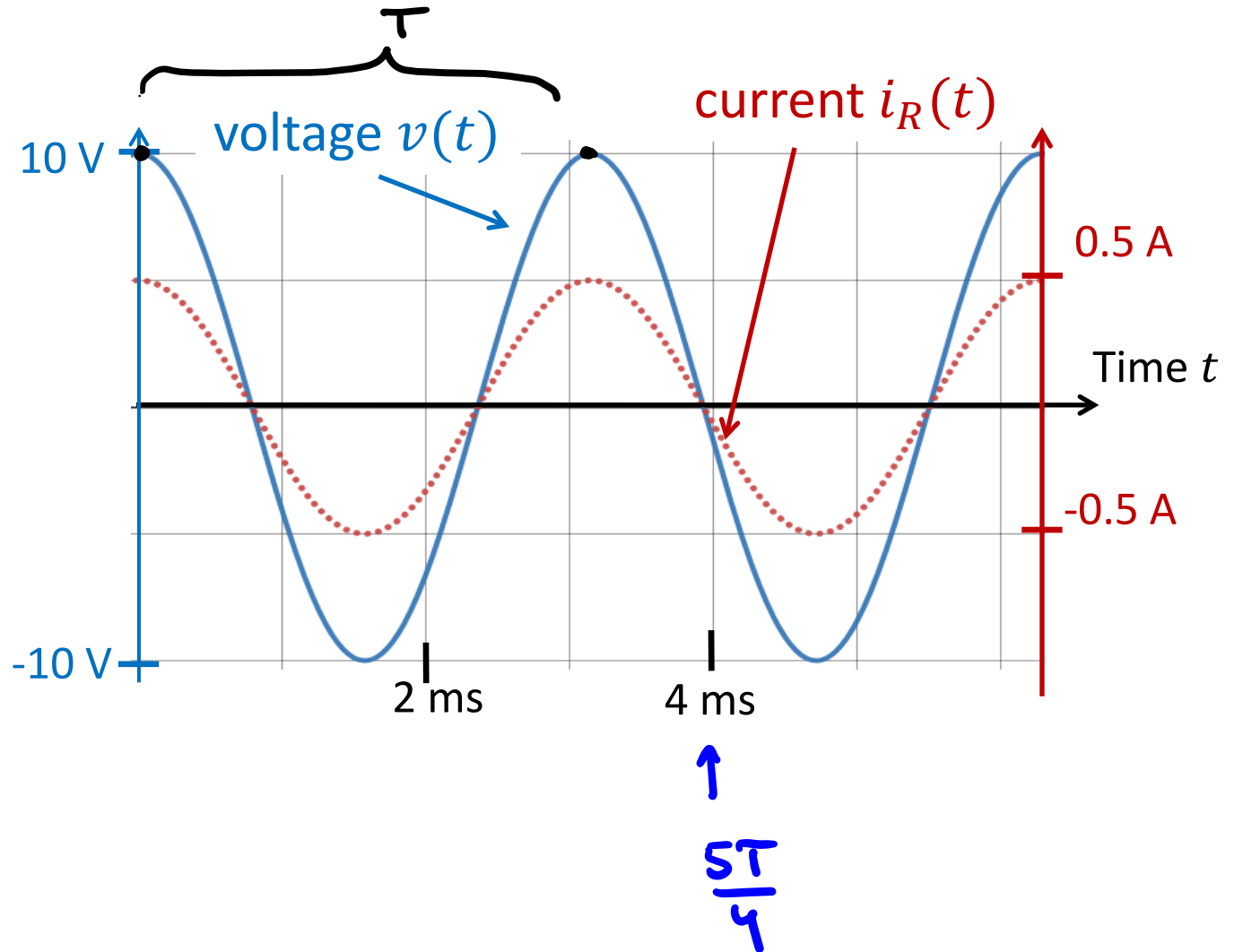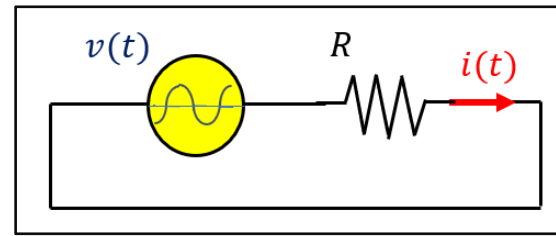
Q: The figure shows the source voltage and current in an AC R -circuit. What is the frequency of the source EMF in Hz? (Pick the closest answer)



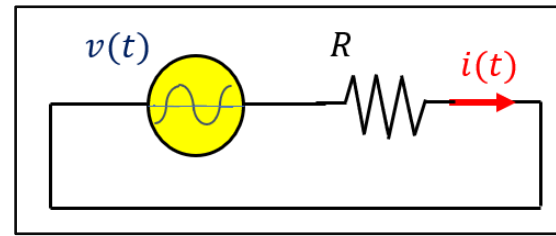
- A. 1000 Hz
- B. 320 Hz
- C. 250 Hz
- D. 100 Hz
- E. 60 Hz

$$f = \frac{1}{T}$$

Q: The figure shows the source voltage and current in an AC R -circuit. What is the frequency of the source EMF in Hz? (Pick the closest answer)



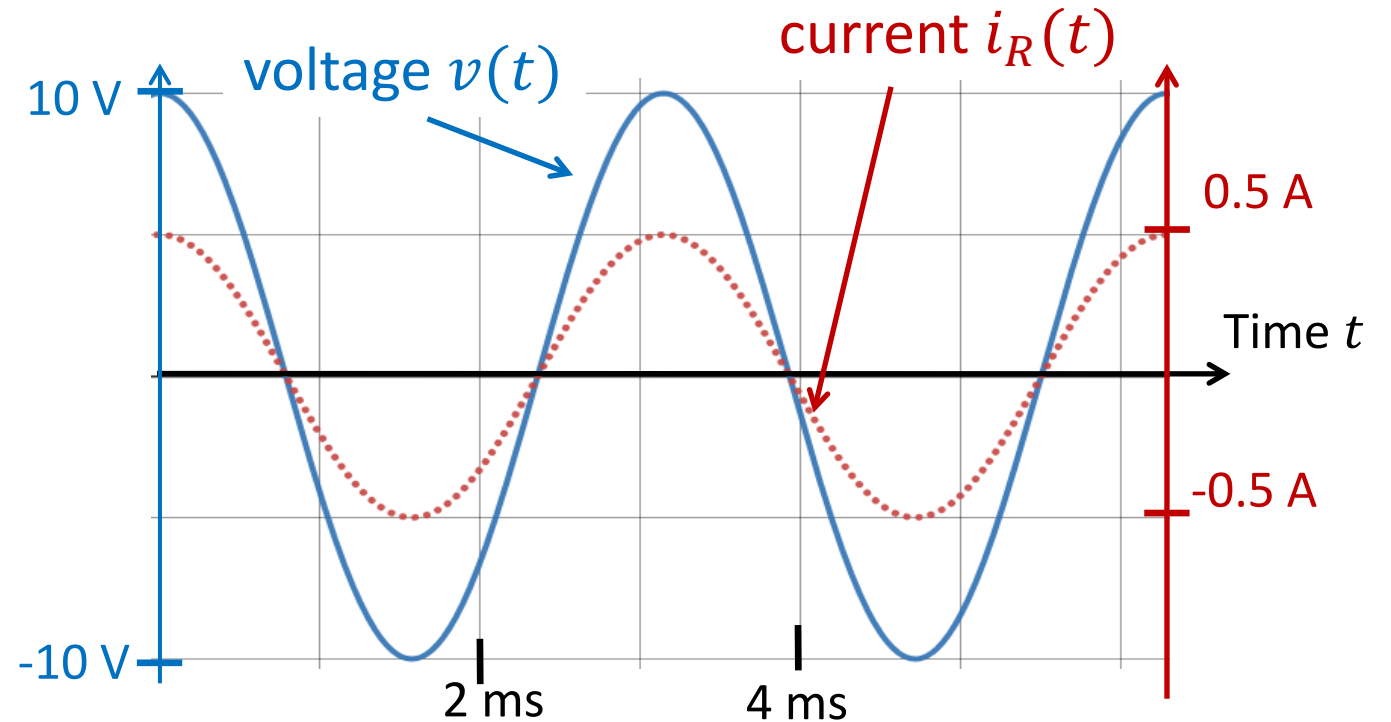
- A. 1000 Hz
- ☒ B. 320 Hz
- C. 250 Hz
- D. 100 Hz
- E. 60 Hz




$$\frac{5T}{4} \approx 4 \text{ ms} \Rightarrow T \approx 3.2 \text{ ms}$$

$$f = \frac{1}{T} \approx \frac{1}{3.1 \text{ ms}} \approx 313 \text{ Hz}$$

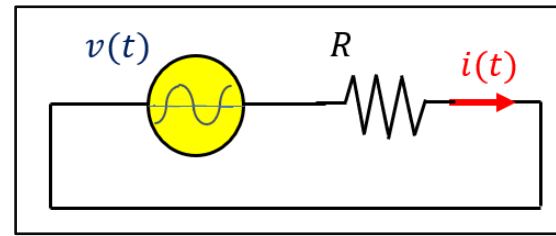Q: The figure shows the source voltage and current in an AC R -circuit. What is the value of resistance R at $t = 6\text{ ms}$? (Pick the closest answer)





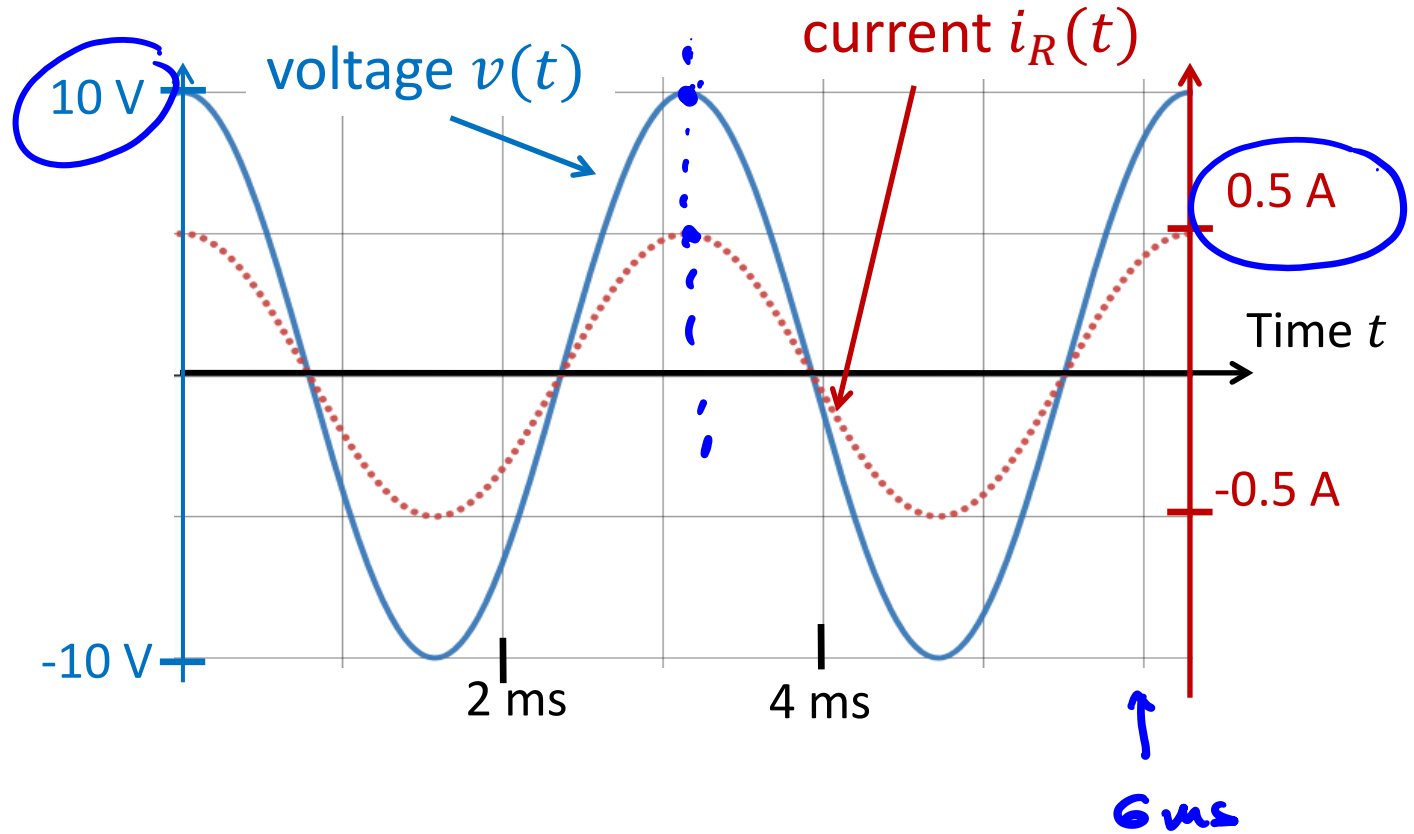- A. Instantaneously, at $t = 6\text{ ms}$, R is undefined
- B. $0\ \Omega$
- C. $5\ \Omega$
- D. $10\ \Omega$
- E. $20\ \Omega$



$$\Delta V_R = IR$$

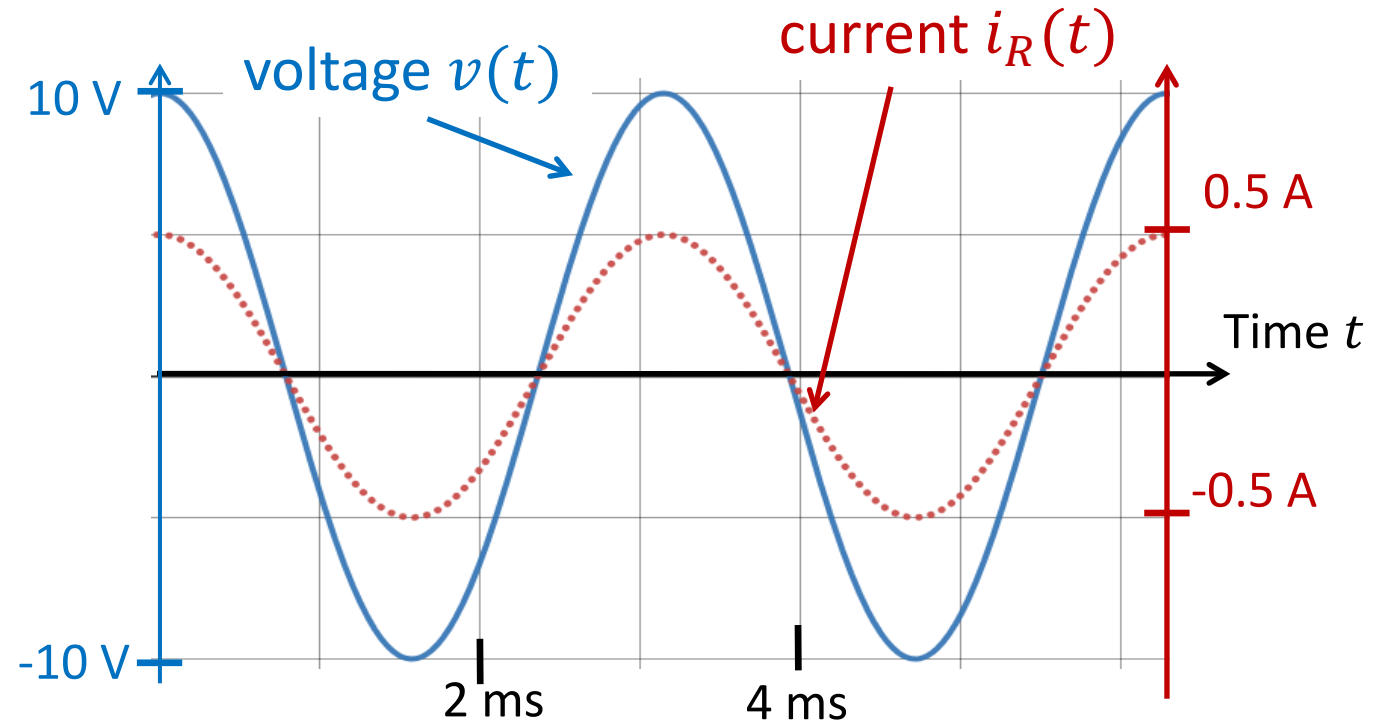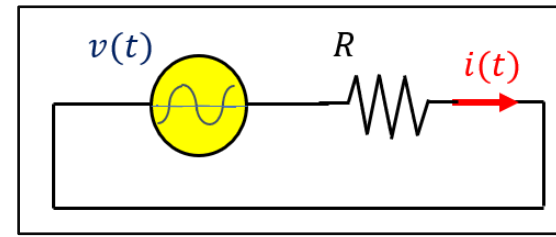
Q: The figure shows the source voltage and current in an AC R -circuit. What is the value of resistance R at $t = 6\text{ ms}$? (Pick the closest answer)



- A. Instantaneously, at $t = 6\text{ ms}$, R is undefined
- B. $0\ \Omega$
- C. $5\ \Omega$
- D. $10\ \Omega$
- ☒ E. $20\ \Omega$

- No matter which moment of time we analyze, the resistance is always $R = V/I$.
- At max, we have: $R = 10\text{ V}/0.5\text{ A} = 20\ \Omega$

AC circuit: purely “R” = Resistive

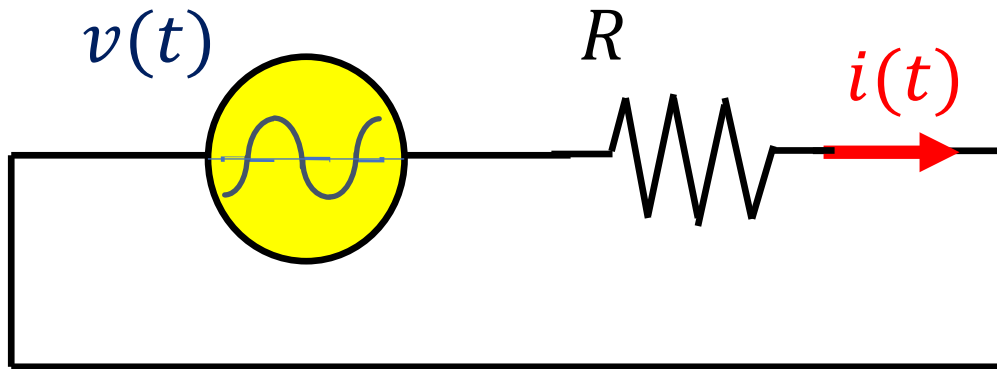

$$v(t) = V_{max} \cos(\omega t)$$

$\rightarrow I_{max}$


- Circuit analysis:

$$v(t) - i(t)R = 0$$

$$i(t) = \frac{v(t)}{R} = \left(\frac{V_{max}}{R} \right) \cos(\omega t)$$

- The current through the Resistor is “in phase” with the oscillating Voltage

AC circuit: purely “L” = Inductive

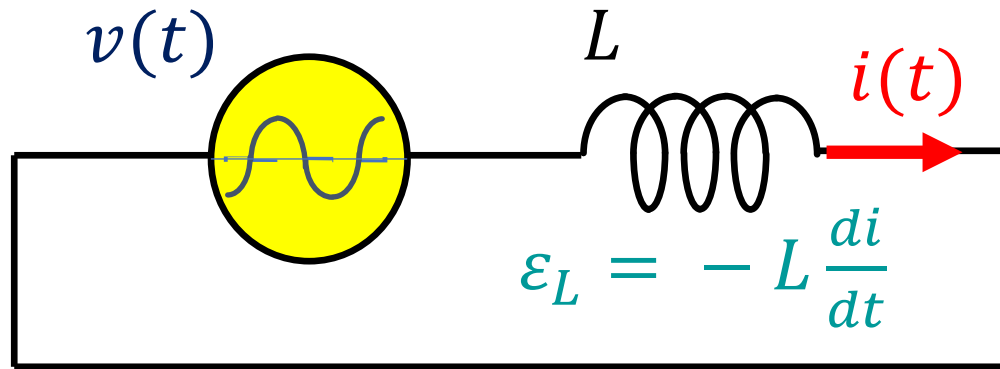

$$v(t) = V_{max} \cos(\omega t)$$

$$\sin \alpha = \cos \left(\alpha - \frac{\pi}{2} \right)$$

- Circuit analysis:

$$v(t) - L \frac{di(t)}{dt} = 0$$


$$V_{max} \cos(\omega t) - L \frac{di(t)}{dt} = 0$$

$$\frac{di(t)}{dt} = (V_{max}/L) \cos(\omega t)$$

$$i(t) = \left(\frac{V_{max}}{\omega L} \right) \sin(\omega t) = \left(\frac{V_{max}}{\omega L} \right) \cos \left(\omega t - \frac{\pi}{2} \right)$$

- The current through the inductor is “by $\frac{\pi}{2}$ behind” the oscillating voltage

AC circuit: purely “L” = Inductive

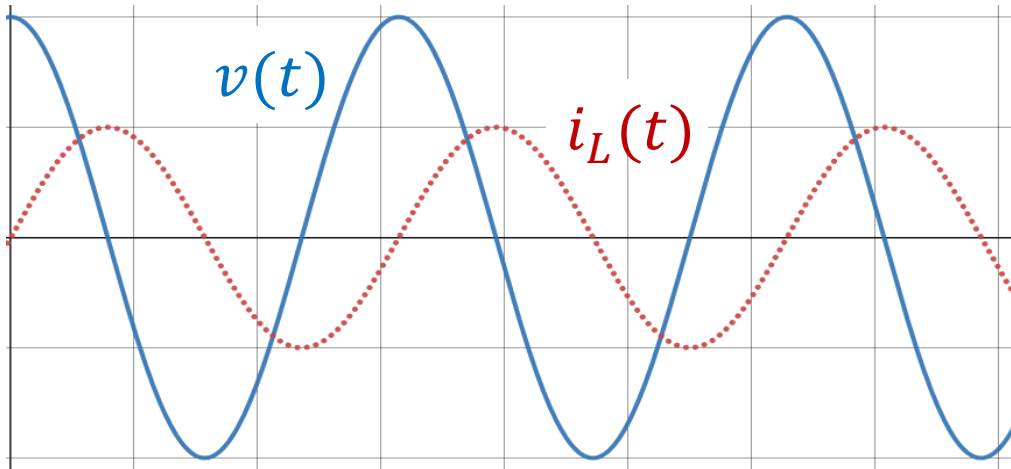

$$v(t) = V_{max} \cos(\omega t)$$

$$i(t) = \left(\frac{V_{max}}{X_L} \right) \cos \left(\omega t - \frac{\pi}{2} \right)$$

- We say: the current $i(t)$ lags behind the voltage, or “the voltage leads the current”.


- Note: V_{max} and I_{max} occur at different times!

$$X_L = \omega L$$

“Inductive resistance”

➤ Units: Ohm

AC circuit: purely “C” = Capacitive

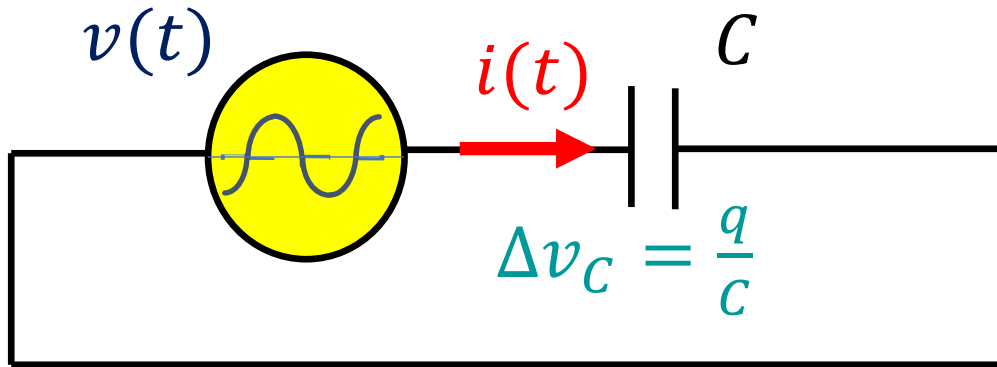

$$v(t) = V_{max} \cos(\omega t)$$

$$-\sin \alpha = \cos\left(\alpha + \frac{\pi}{2}\right)$$

- Circuit analysis:

$$v(t) - q(t)/C = 0$$

$$V_{max} \cos(\omega t) - q(t)/C = 0$$


$$i(t) = \frac{dq(t)}{dt} = -(\omega C V_{max}) \sin(\omega t)$$

$$i(t) = -(\omega C V_{max}) \sin(\omega t) = (\omega C V_{max}) \cos\left(\omega t + \frac{\pi}{2}\right)$$

- The current through the capacitor is “by $\frac{\pi}{2}$ ahead” the oscillating voltage

AC circuit: purely “C” = Capacitive

$$I_{max} = \omega C V_{max}$$

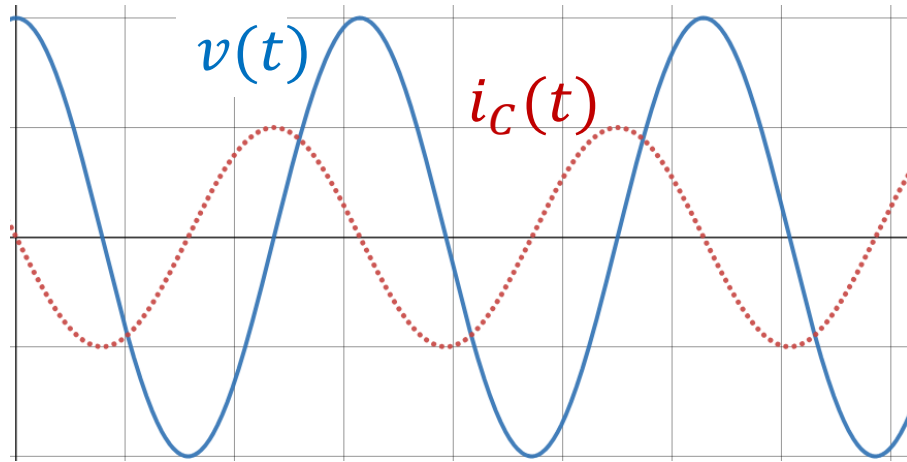

leads

- We say: the current $i(t)$ ~~lags behind~~ the voltage, or “the voltage ~~lags~~ the current”.
lags behind

$$V(t) = V_{max} \cos(\omega t)$$

$$i(t) = \left(\frac{V_{max}}{X_C} \right) \cos \left(\omega t + \frac{\pi}{2} \right)$$

\equiv


$$X_C = \frac{1}{\omega C}$$

“Capacitive resistance”

➤ Units: Ohm


- Note: V_{max} and I_{max} occur at different times!

R-circuit

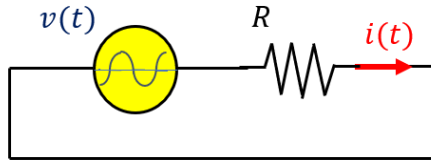


$$i(t) = \left(\frac{V_{max}}{X_R} \right) \cos(\omega t)$$

$$X_L = R$$

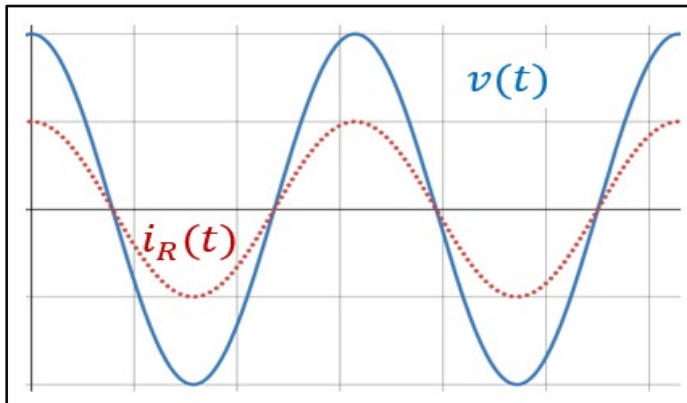


- Current in phase with voltage

L-circuit

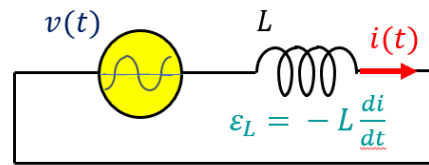


$$i(t) = \left(\frac{V_{max}}{X_L} \right) \cos \left(\omega t - \frac{\pi}{2} \right)$$

$$X_L = \omega L$$

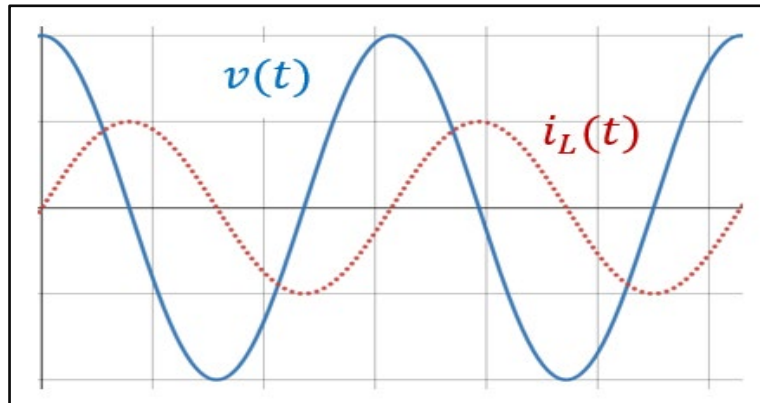


- Current lags behind voltage by $\frac{\pi}{2}$ (voltage leads current)

C-circuit

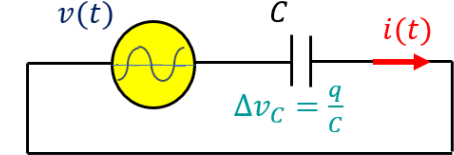


$$i(t) = \left(\frac{V_{max}}{X_C} \right) \cos \left(\omega t + \frac{\pi}{2} \right)$$

$$X_C = \frac{1}{\omega C}$$

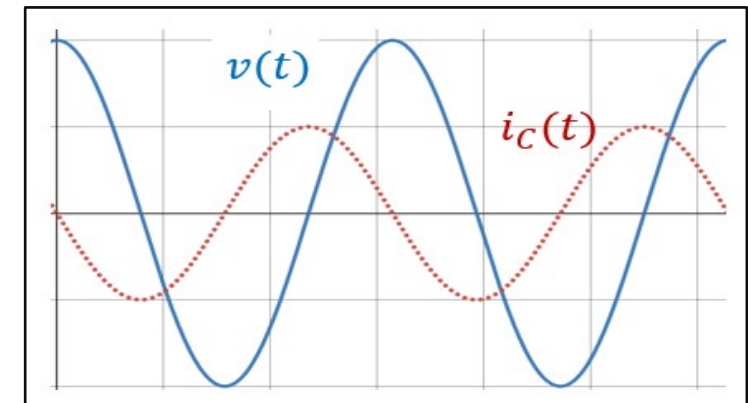


- Voltage lags behind current by $\frac{\pi}{2}$ (current leads voltage)

R-circuit

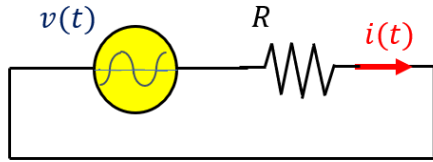


$$i(t) = \left(\frac{V_{max}}{X_R} \right) \cos(\omega t)$$

$$X_L = R$$

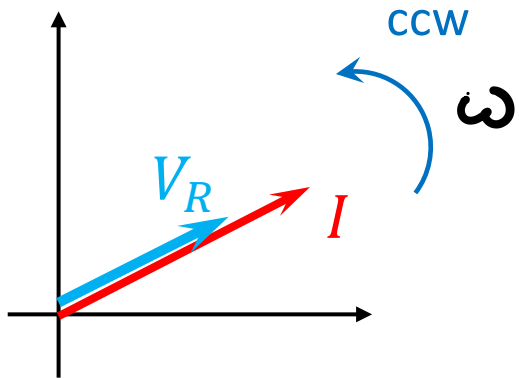


- Current is in phase with voltage

L-circuit

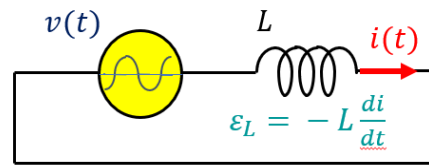


$$i(t) = \left(\frac{V_{max}}{X_L} \right) \cos \left(\omega t - \frac{\pi}{2} \right)$$

$$X_L = \omega L$$

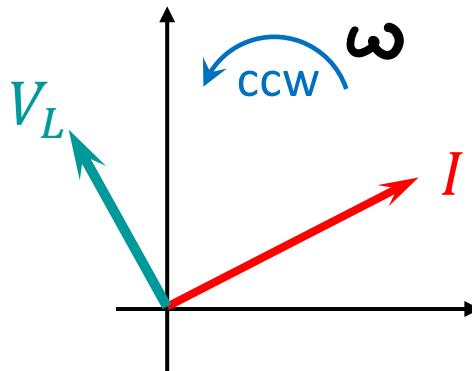


- Current lags behind voltage by $\frac{\pi}{2}$ (voltage leads current)

C-circuit

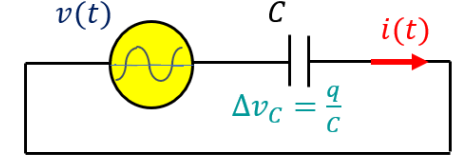

$$i(t) = \left(\frac{V_{max}}{X_C} \right) \cos \left(\omega t + \frac{\pi}{2} \right)$$




$$X_C = \frac{1}{\omega C}$$

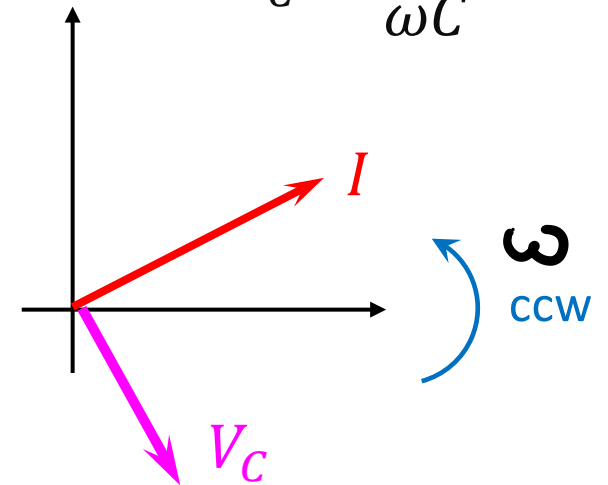

- Voltage lags behind current by $\frac{\pi}{2}$ (current leads voltage)


Phasors

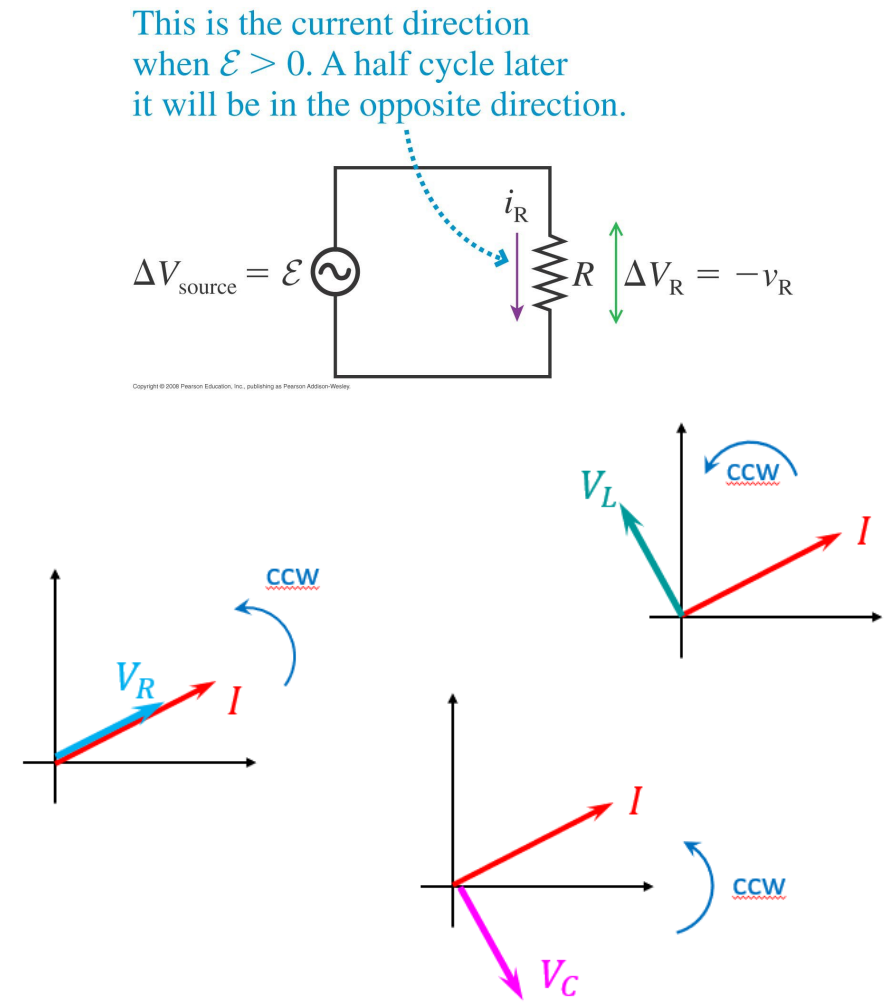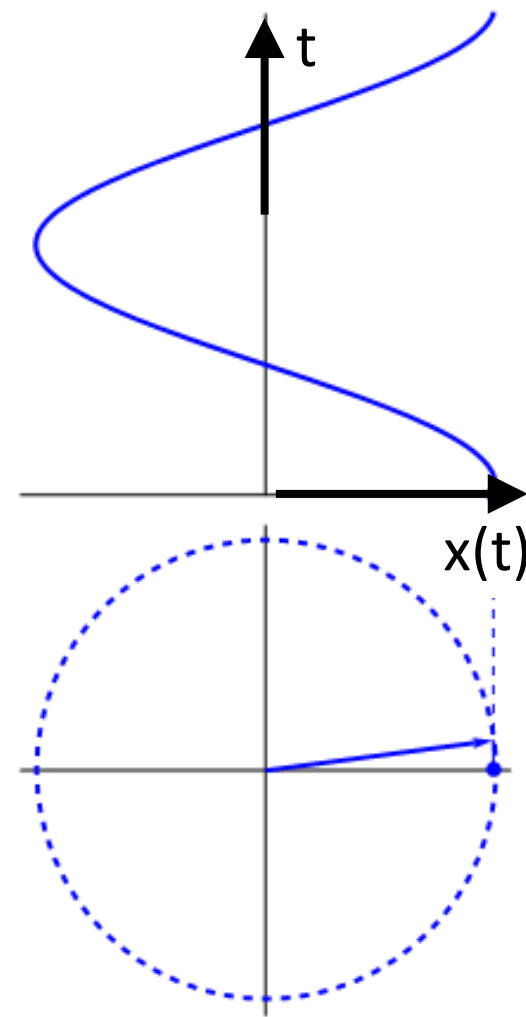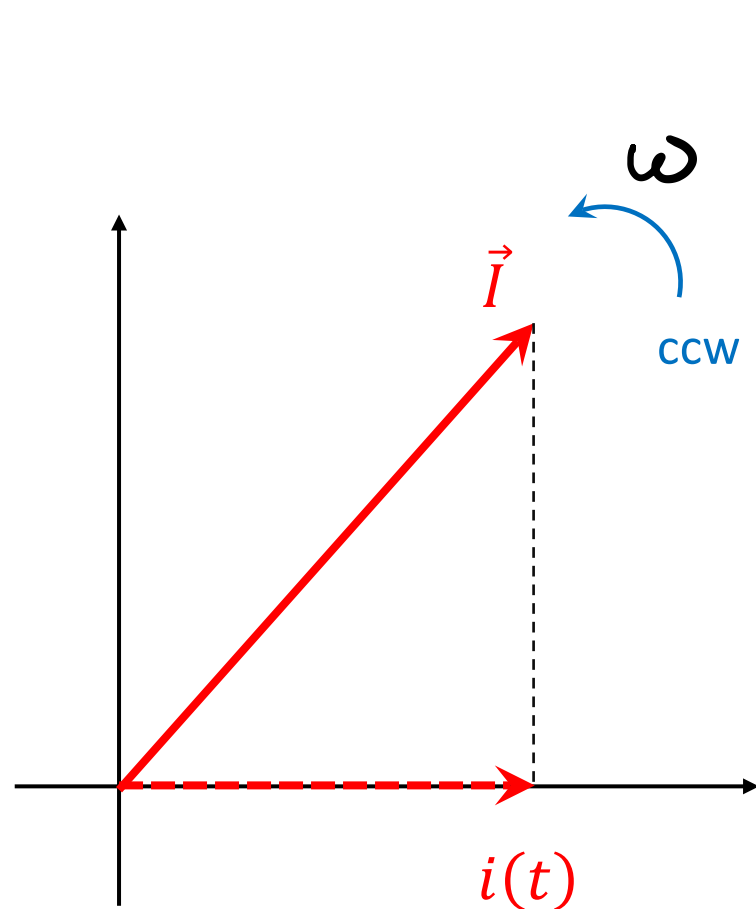- AC current is represented by a vector performing CCW rotation $i(t) = I_{max} \cos \omega t$



Phasors

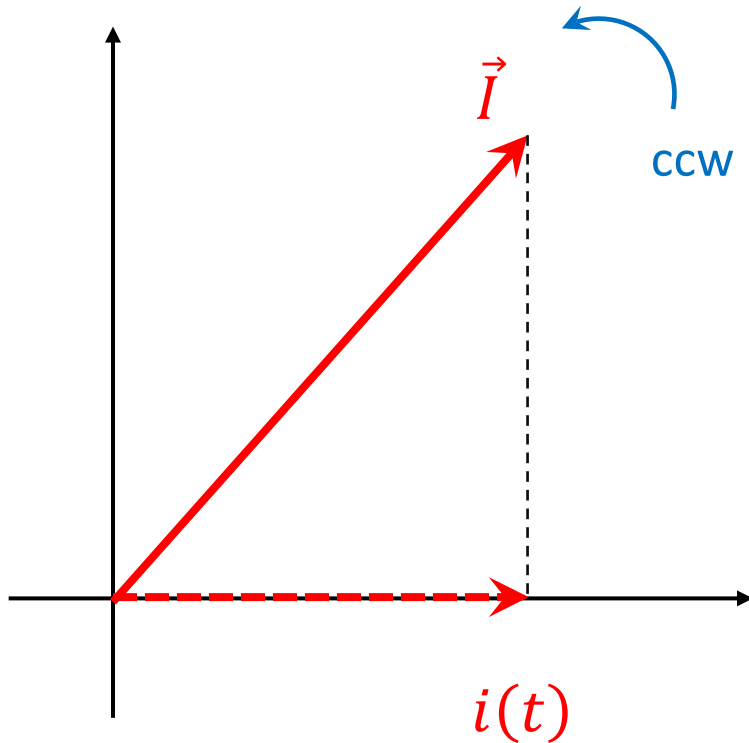- Here comes the idea of **phasors** – abstract vectors, that help us to account for the **phases (= delays)** for voltages and currents in AC circuits.
- AC current is represented by a vector performing CCW rotation






- Its length is equal to maximum current, I_{max}
- It rotates with the angular frequency ω of the source voltage
- Its projection onto the horizontal axis at time t is equal to the current at that instant:

$$i(t) = I_{max} \cos \omega t$$

Phasors

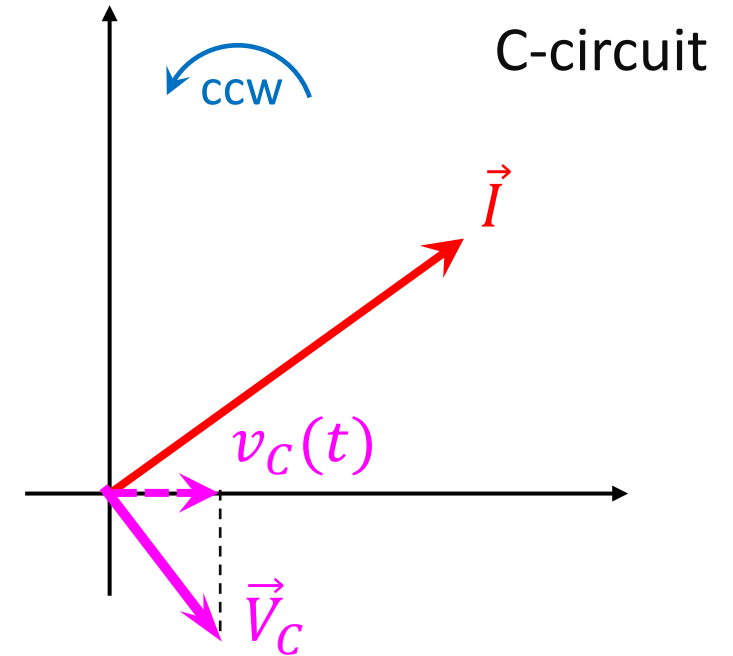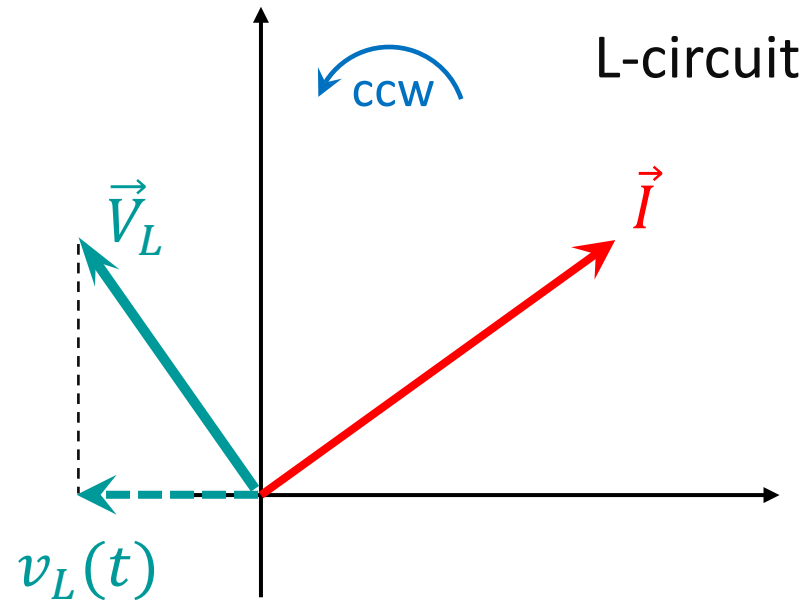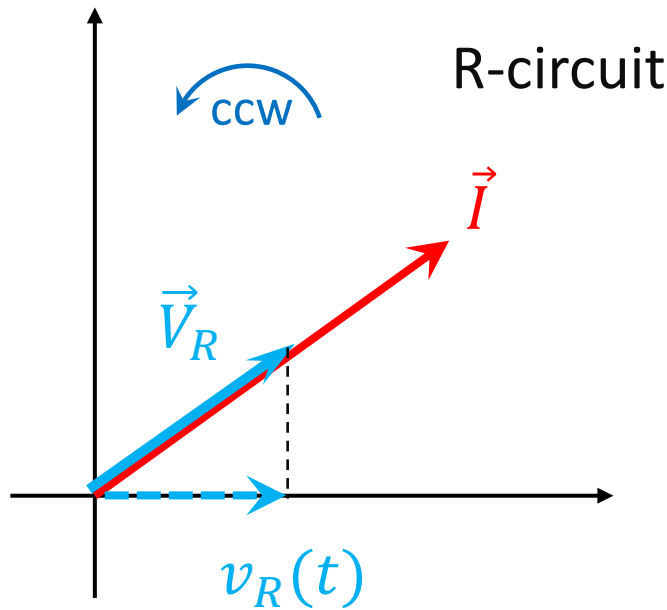- We can also invent **phasors** for the voltages: $\vec{V}_R, \vec{V}_L, \vec{V}_C$
- Their projections on the horizontal axis will represent instantaneous voltages across R, L, and C in the direction opposite to the current.



- Resistor voltage phasor:

- In phase with I_R
- $V_R = I_R \underline{R}$

- Inductor voltage phasor:


- $\pi/2$ ahead of I_L
- $V_L = I_L \underline{X_L}$ ($X_L = \underline{\omega L}$)

- Capacitor voltage phasor:

- $\pi/2$ behind I_C
- $V_C = I_C \underline{X_C}$ ($X_C = \underline{1/\omega C}$)

AC RLC series circuit

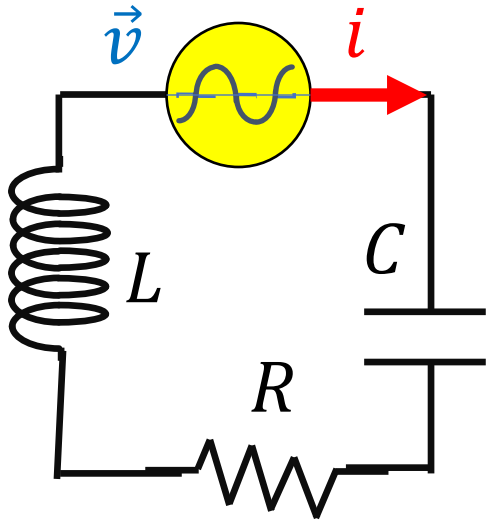- Phasors help us to add up voltages when combining different elements in an AC circuit




- Q: What is common for all these elements?
- A: They have the same current!

- Let's combine all the voltage phasors in one diagram:

- Q: How can we find the relationship between source voltage and the current?

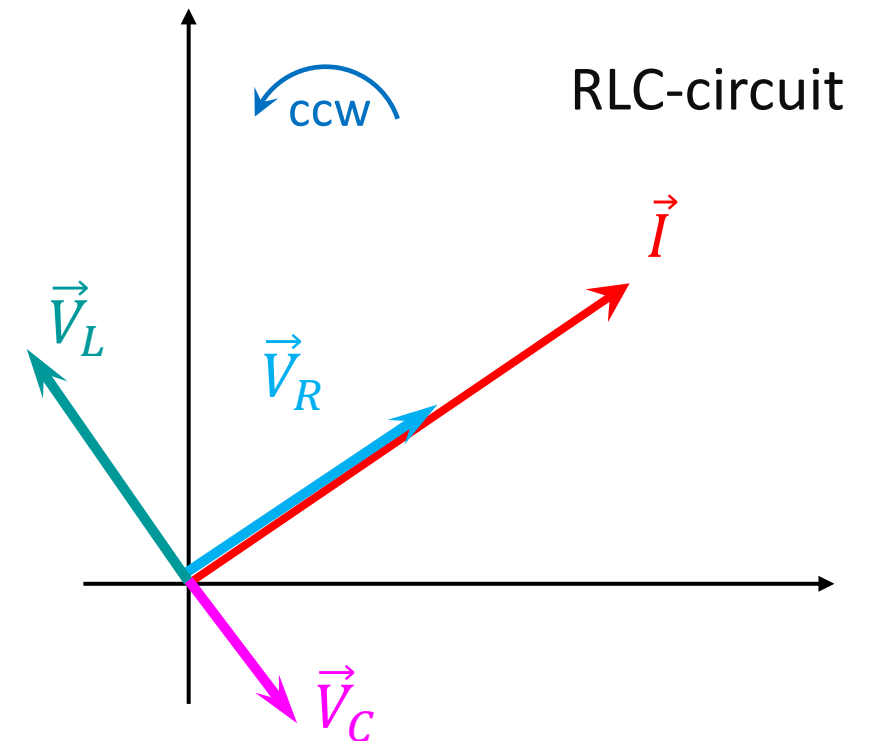- A: $\vec{V} = \vec{V}_L + \vec{V}_C + \vec{V}_R$ 😊



Q: What is the magnitude of the source voltage phasor, $\vec{V} = \vec{V}_L + \vec{V}_C + \vec{V}_R$?


A. $V = V_R + V_L + V_C$

B. $V = V_R + (V_L - V_C)$

C. $V = \sqrt{V_R^2 + (V_L + V_C)^2}$


D. $V = \sqrt{V_R^2 + (V_L - V_C)^2}$

E. ☹️

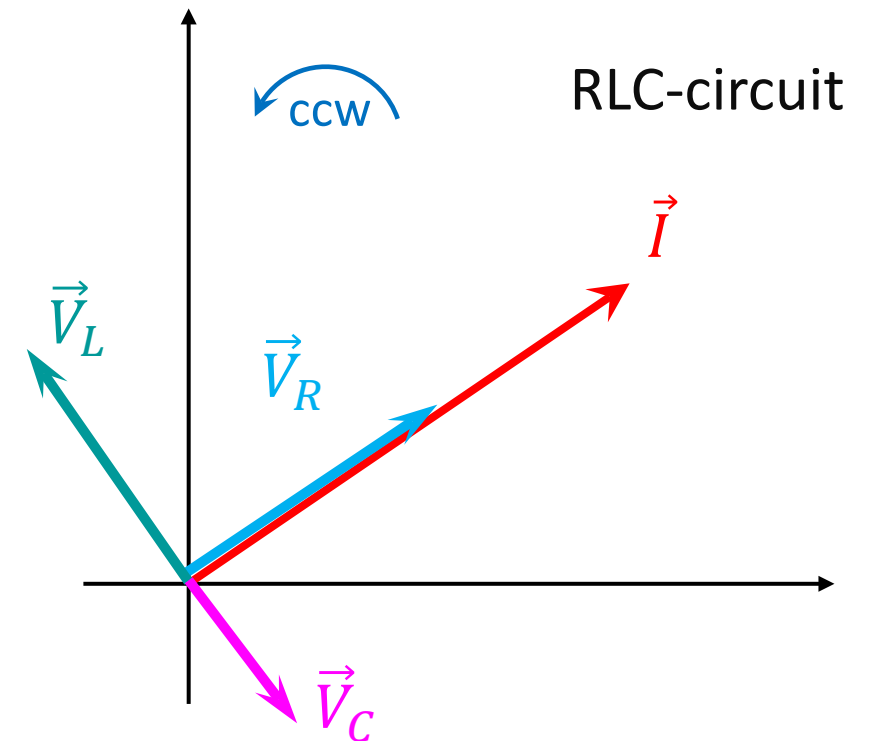

AC RLC series circuit: Impedance
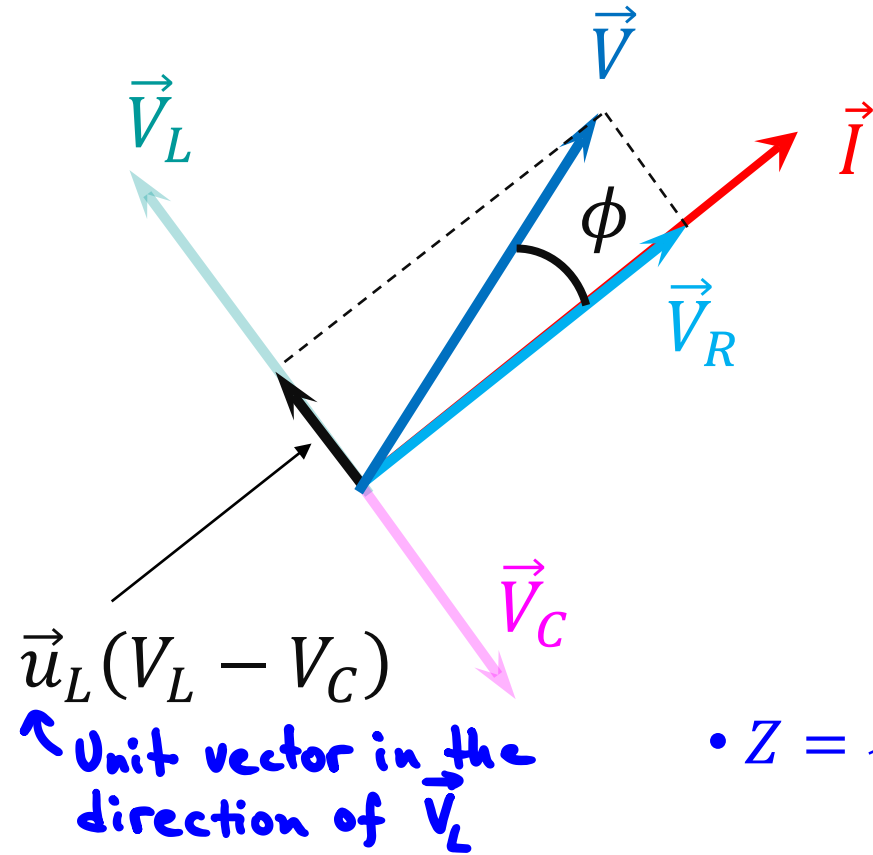
$$\vec{V} = \vec{V}_L + \vec{V}_C + \vec{V}_R$$



$$V_{max} = \sqrt{V_R^2 + (V_L - V_C)^2}$$

$$= \sqrt{(X_R I_{max})^2 + (X_L I_{max} - X_C I_{max})^2}$$

$$= I_{max} \sqrt{X_R^2 + (X_L - X_C)^2} \equiv I_{max} Z$$

$$V_R = X_R I_{max}$$

$$V_L = X_L I_{max}$$

$$V_C = X_C I_{max}$$

• $Z = \sqrt{X_R^2 + (X_L - X_C)^2}$ is called **the impedance**.

• $\tan(\phi) = \frac{X_L - X_C}{X_R}$ is **the phase** between the current and the source voltage

• So: if $i(t) = I_{max} \cos \omega t$, then $v(t) = (I_{max} Z) \cos(\omega t + \phi)$.

