

## Physics 158 HW-2 Hand-In Jan 21

### Problem 1

Difficulty: ★☆☆


If the switch is open,

- a) Find all currents and potentials at the labelled points.

If the switch is then closed,

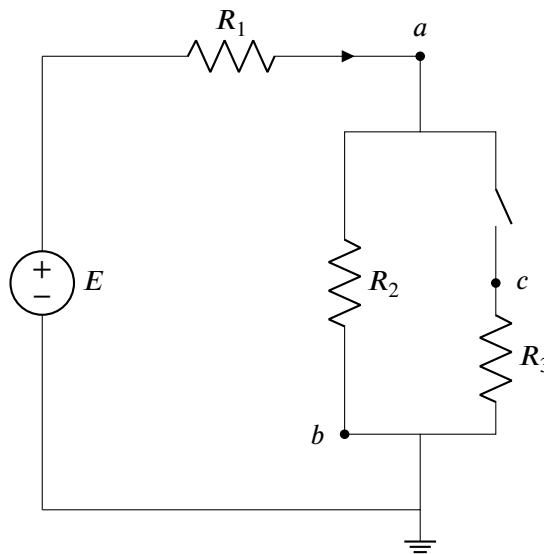- b) Find all currents and potentials at the labelled points.

$$E = 12 \text{ V}, R_1 = 7 \Omega, R_2 = 4 \Omega, R_3 = 10 \Omega$$



### Solution:

- a) When the switch is open, there is a short circuit in the branch with  $R_3$  so the circuit will act as a series circuit containing  $R_1$ ,  $R_2$ , and  $E$ . The potential and voltage at point  $c$  will be 0.

The equivalent resistance will be  $R_{\text{eq}} = R_1 + R_2$ . The current can be computed from Ohm's law:

$$E = I_a R_{\text{eq}}$$
$$I_a = I_b = \frac{E}{R_{\text{eq}}} = \frac{E}{R_1 + R_2} = \frac{12 \text{ V}}{11 \Omega} = 1.09 \text{ A}$$

Point  $b$  is connected to ground so the potential of point  $b$  will be  $0\text{ V}$ . The potential of point  $a$  can be computed as the voltage drop across  $R_2$ .

$$V_{R_2} = V_{ab} = V_a - V_b = V_a$$

$$V_{R_2} = I_a R_2 = \frac{12}{11} \text{ A} \cdot 4 \Omega = 4.36 \text{ V}$$

- b) When the switch is closed,  $R_2$  and  $R_3$  will be in parallel. We can compute the equivalent resistance for the circuit as

$$\frac{1}{R_{23}} = \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{4} + \frac{1}{10} = \frac{7}{20} \Rightarrow R_{23} = \frac{20}{7} \Omega = 2.67 \Omega$$

$$R_{\text{eq}} = R_1 + R_{23} = 7 + \frac{20}{7} = \frac{69}{7} \Omega$$

Then we can compute the total current as

$$E = I_a R_{\text{eq}} \Rightarrow I_a = \frac{E}{R_{\text{eq}}} = \frac{12 \text{ V}}{\frac{69}{7} \Omega} = 1.22 \text{ A}$$

We can use this to compute the voltage across  $R_1$

$$V_{R_1} = I_a R_1 = 8.52 \text{ V}$$

Then we can use Kirchhoff's voltage law to find the remaining voltages

$$V_{R_2} = V_{R_3}$$

$$V_E = V_{R_1} + V_{R_2} \Rightarrow V_{R_2} = V_{R_3} = V_E - V_{R_1} = 3.48 \text{ V}$$

From this we can get that the potential at  $c$  and the potential at  $a$  will be  $V_a = V_c = 3.48 \text{ V}$  while the potential at  $b$  will be  $0 \text{ V}$  as in part a.

We can also use the voltages across the resistors to compute the currents in each branch.


$$I_b = \frac{V_{R_2}}{R_2} = \frac{3.48}{4} = 0.87 \text{ A}$$

$$I_c = \frac{V_{R_3}}{R_3} = \frac{3.48}{10} = 0.35 \text{ A}$$
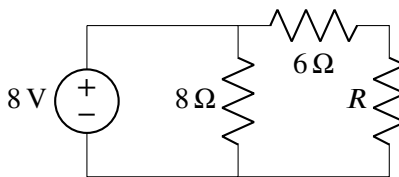
## Problem 2

Difficulty: ★☆☆

If the total power dissipated in the circuit is  $15\text{ W}$ , what is the value of  $R$ ?



**Solution:**

The total power dissipated in the circuit will be the sum of the power dissipated in each resistor. We know that the power dissipated across a resistor is  $P = IV$ . We also know  $V = IR$  and can rearrange to get  $P = \frac{V^2}{R}$ .

The voltage across the  $8\ \Omega$  resistor is  $8\text{ V}$  so power across that resistor will be

$$P_1 = \frac{(8\text{ V})^2}{8\ \Omega} = 8\text{ W}$$

The sum of the power across the remaining two resistors will be  $P_{\text{total}} - P_1 = 15\text{ W} - 8\text{ W} = 7\text{ W}$ .

We can combine resistor  $R$  and the  $6\ \Omega$  to get an equivalent resistor with value  $R + 6$ . The voltage across this equivalent resistor will be  $8\text{ V}$  and will have a power usage of  $7\text{ W}$ . We can then solve for  $R$  as


$$7\text{ W} = \frac{(8\text{ V})^2}{R + 6\ \Omega}$$

$$R = \frac{(8\text{ V})^2}{7\text{ W}} - 6\ \Omega = \boxed{3.14\ \Omega}$$

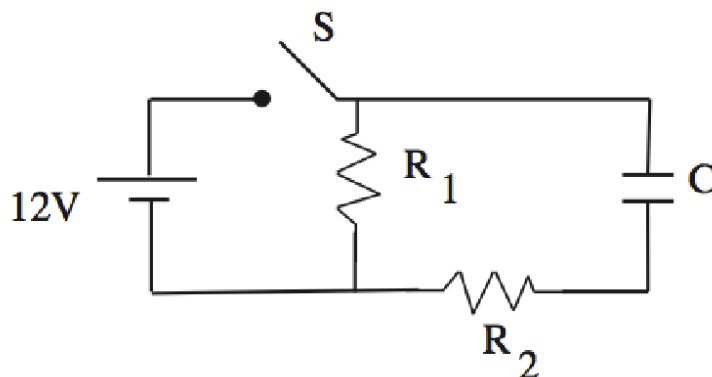**Problem 3**

Difficulty: ★★☆☆

In the circuit shown below the switch has been open for a long time and there is no charge on the capacitor. Take  $R_1 = 2\ \Omega$ ,  $R_2 = 4\ \Omega$ ,  $C = 2\text{ F}$ .



- The switch  $S$  is now closed. Find all currents just after the switch is closed.
- Find all currents after the switch has been closed for a very long time.
- After the switch has been closed for a very long time it is reopened. Calculate the current through  $R_2$  as a function of time.

**Solution:**

- The capacitor will initially act as a wire so we can analyze the circuit as two resistors in parallel. Due to Kirchhoff's loop law, we can say that each resistor must have a voltage drop of  $12\text{ V}$  and we can get the current of each from Ohm's law:

$$I_1 = \frac{\varepsilon}{R_1} = \frac{12}{2} = \boxed{6\text{ A}}$$

$$I_2 = \frac{\varepsilon}{R_2} = \frac{12}{4} = \boxed{3 \text{ A}}$$

- b) After the switch has been closed for a long time, the capacitor will be fully charged and act as a short circuit. The circuit can then be analyzed as the loop going through the battery and  $R_1$

$$I_1 = \frac{\varepsilon}{R_1} = \frac{12}{2} = \boxed{6 \text{ A}}$$

$$\boxed{I_2 = 0 \text{ A}}$$

- c) After the switch is opened the current will flow through the loop containing  $R_1$ ,  $R_2$ , and  $C$ . We can write the voltage loop equation as

$$0 = V_C + V_{R_1} + V_{R_2}$$

$$0 = \frac{q}{C} + iR_1 + iR_2$$

We know that  $i = \frac{dq}{dt}$  and can take the derivative of both sides to get a 1st order differential equation and solve for  $i(t)$

$$0 = \frac{i}{C} + \frac{di}{dt}(R_1 + R_2)$$

$$\frac{di}{dt} = -\frac{i}{(R_1 + R_2)C}$$

$$\frac{di}{i} = -\frac{dt}{(R_1 + R_2)C}$$

$$\int \frac{di}{i} = -\int \frac{dt}{(R_1 + R_2)C}$$

$$\ln |i| = -\frac{t}{(R_1 + R_2)C} + \text{Constant}$$

$$i = i_0 e^{-\frac{t}{(R_1 + R_2)C}}$$

We can solve for the initial current by using our same voltage loop equation and knowing that the initial voltage across the capacitor is 12 V from the charge stored on it. The capacitor will be discharging so the potential in the equation can be thought of as negative.

$$0 = V_C + i_0(R_1 + R_2)$$

$$0 = -12 + 6i_0 \Rightarrow i_0 = 2 \text{ A}$$


Plugging this all in we get,

$$\boxed{i(t) = 2e^{-\frac{t}{12}} \text{ Amps}}$$
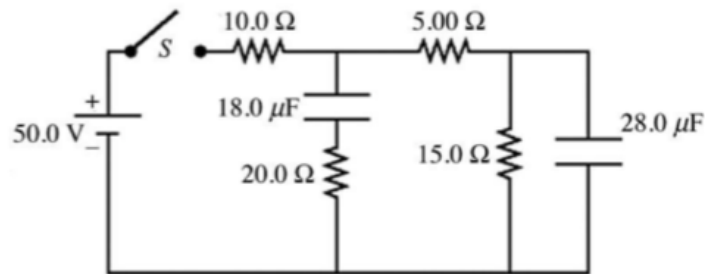
## Problem 4

Difficulty: ★★☆☆


The circuit shown below initially has no charge on the capacitors and the switch S is originally open.



- Just after closing the switch S, find all the currents.
- After the switch has been closed for a very long time, find all the currents.
- After the switch S has been closed for a very long time, find the potential difference across the  $28.0 \mu\text{F}$  capacitor.

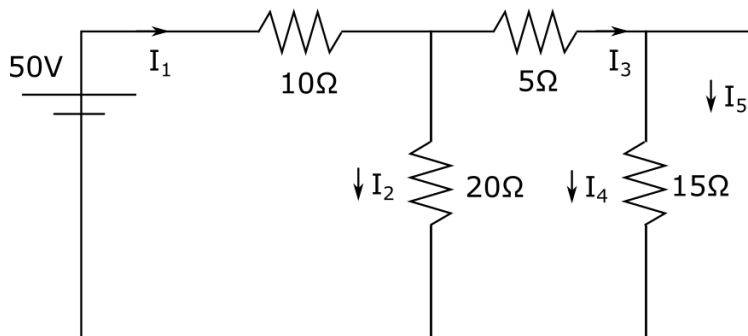**Solution:**

- just after we close the switch there is NO charge on the Capacitors. Hence we have the following circuit:



Note the Capacitors act like a wire when uncharged


$$K_1 \Rightarrow \text{Hence } \underline{I_4 = 0}, I_1 = I_2 + I_3, I_3 = I_4 + I_5 = I_5$$

$$K_2 \Rightarrow 50 - 10I_1 - 20I_2 = 0$$

$$0 = -5I_3 + 20I_2$$

You now have 3 equations and 3 unknowns. Solve

EQUIVALENT Circuit

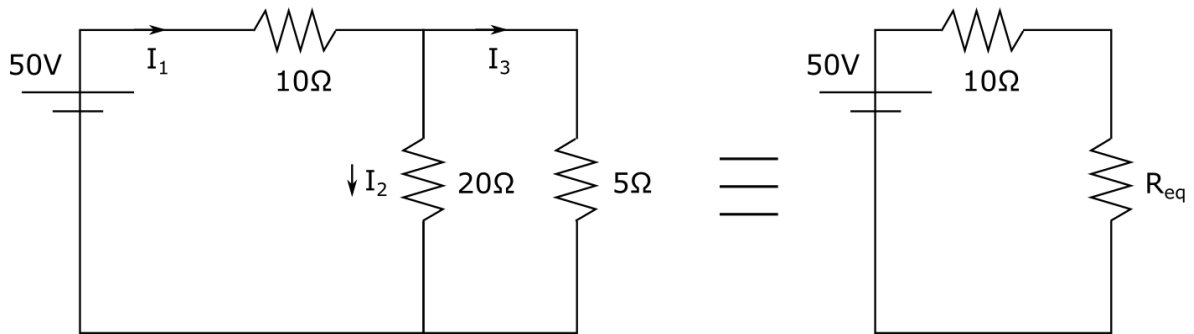

$$\frac{1}{R_{eq}} = \frac{1}{20} + \frac{1}{5} = \frac{1}{20} + \frac{4}{20} = \frac{5}{20} = \frac{1}{4}$$

$$\rightarrow R_{eq} = 4\Omega$$

Hence  $I_1 = \frac{50V}{14\Omega}$ , Since  $I_1 = I_2 + I_3$  and  $20I_2 = 5I_3$  we have

$$I_1 = \frac{50}{14} \text{ Amps} = 3.57 \text{ A} = I_2 + 4I_2 = 5I_2$$


$$\therefore I_2 = \frac{10}{14} \text{ Amps} = 0.714 \text{ A}$$

and finally

$$I_3 = 4I_2 = \frac{40}{14} \text{ Amps} = 2.86 \text{ A}$$

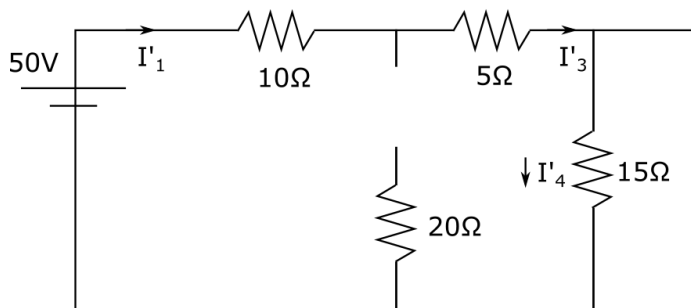b) after a long time the Capacitors are fully charged

$$\therefore I'_2 = 0, I'_5 = 0 \Rightarrow I'_1 = I'_3 = I'_4$$



$$\therefore \frac{50V}{30\Omega} = I'_1 = \frac{5}{3} \text{ Amp}$$


c)  $V_{28\mu F} = V_{15\Omega} = I'_4(15\Omega) = \frac{5}{3}(15) = \underline{25V}$

5. ( Difficulty: \*\* )

Given the following circuit with resistors  $R_1 = 1.0\Omega$ ,  $R_2 = 2.0\Omega$ ,  $R_3 = 3.0\Omega$ ,  $R_4 = 4.0\Omega$ ,  $R_5 = 5.0\Omega$ , and  $R_6 = 6.0\Omega$ , with  $\mathcal{E}_1 = 10.0V$ ,  $\mathcal{E}_3 = 10.0V$ , and  $\mathcal{E}_5 = 15.0V$ .

(a) What is the current  $I_2$  passing through resistor  $R_2$  ??

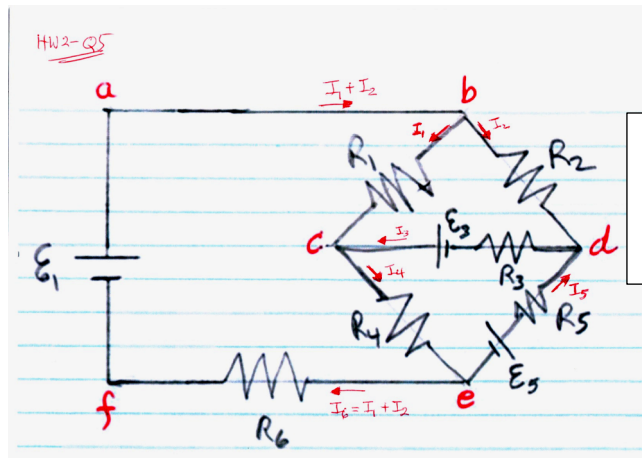(b) What is the current  $I_5$  passing through resistor  $R_5$  ?? ( give both magnitude and direction )



Apply K1 Junction rule at c  $\rightarrow I_4 = I_1 + I_3$   
 Apply K1 Junction rule at d  $\rightarrow I_5 = I_3 - I_2$   
 Apply K1 Junction rule at e  $\rightarrow I_6 = I_4 - I_5 = I_1 + I_3 - (I_3 - I_2)$   
 $I_6 = I_1 + I_2$

Apply K2 Loop rule to abcefa, abdefa, bdcba ( all CW )

$$\mathcal{E}_1 - I_1 R_1 - I_4 R_4 - I_6 R_6 = 0 = \mathcal{E}_1 - I_1 R_1 - (I_1 + I_3) R_4 - (I_1 + I_2) R_6$$

$$\mathcal{E}_1 - I_2 R_2 + I_5 R_5 - \mathcal{E}_5 - I_6 R_6 = 0 = \mathcal{E}_1 - I_2 R_2 - (I_3 - I_2) R_5 - 15 - (I_1 + I_2) R_6$$

$$0 - I_2 R_2 - I_3 R_3 + \mathcal{E}_3 + I_1 R_1 = \mathcal{E}_3 - I_2 R_2 - I_3 R_3 + I_1 R_1$$

Substitute the known values for  $R_i$  and  $\mathcal{E}_i$  and write in standard form

$$11 I_1 + 6 I_2 + 4 I_3 = 10$$

$$-6 I_1 - 13 I_2 + 5 I_3 = 5$$

$$I_1 - 2 I_2 - 3 I_3 = -10$$

Solve using Cramer's Rule as ratio of Determinants

$$I_1 = \frac{\begin{vmatrix} 10 & 6 & 4 \\ 5 & -13 & 5 \\ -10 & -2 & -3 \end{vmatrix}}{\begin{vmatrix} 11 & 6 & 4 \\ -6 & -13 & 5 \\ 1 & -2 & -3 \end{vmatrix}} = \frac{10(49) - 6(35) + 4(140)}{11(49) - 6(13) + 4(25)} = \frac{-280}{561} = \boxed{-0.50A}$$

Solve for  $I_2 = 0.847A \searrow$ ,  $I_3 = 2.60A \leftarrow$

Hence  $I_4 = 2.10A \searrow$ ,  $I_5 = 1.75A \nearrow$  as shown