

Announcements:

- Deadline for all HW assignments: Sunday => Wednesday




- In short: you can nominate students for an award

Lecture 11.

AC circuits and Impedance Triangle.
Practice.

Last Time:
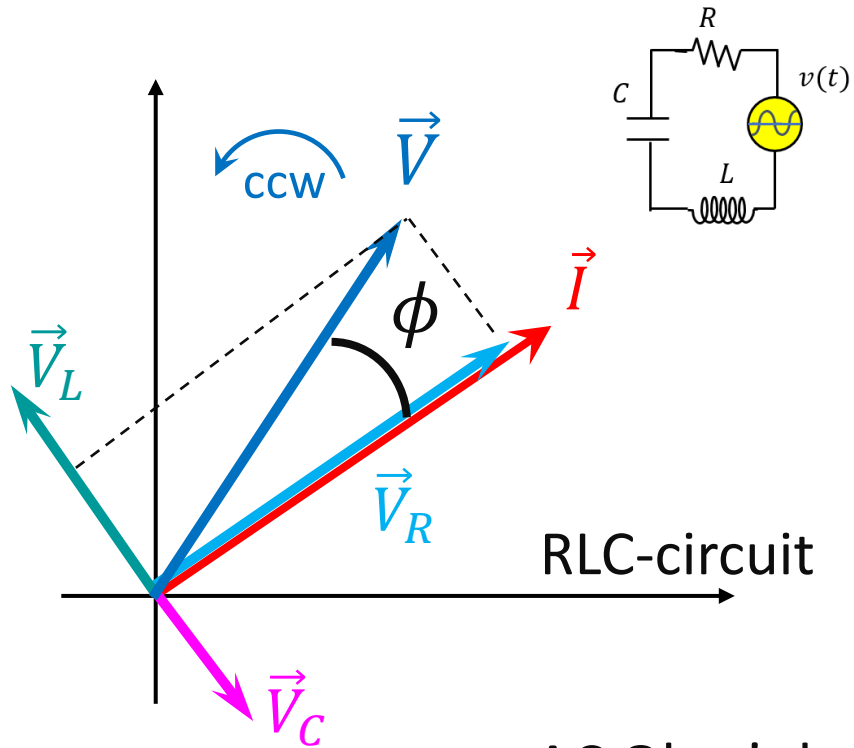
$$v_{\text{source}}(t) = V_{\text{max}} \cos(\omega t)$$



• AC Ohm's law:

$$V_{\text{max}} = IZ$$

- Phasors – abstract vectors that help us trace phase delays between the current and the voltage drops
- Their projection on the x-axis is the instantaneous voltage / instantaneous current

• “Resistances”:

$$V_R = IX_R \quad (X_R = R)$$

$$V_L = IX_L \quad (X_L = \omega L)$$

$$V_C = IX_C \quad (X_C = 1/\omega C)$$


• Impedance:
$$Z = \sqrt{X_R^2 + (X_L - X_C)^2}$$

• Phase V to I :
$$\tan \phi = \frac{X_L - X_C}{R}$$

AC RLC series circuit: Impedance Triangle

$$Z = \sqrt{X_R^2 + (X_L - X_C)^2}$$

$$\tan(\phi) = \frac{X_L - X_C}{X_R}$$

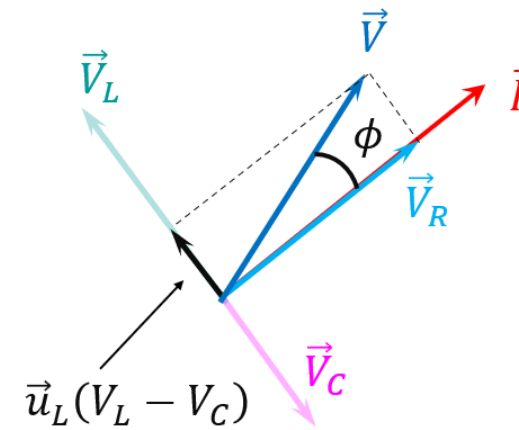

$$X_R = R$$


$$X_L = \omega L$$

$$X_C = 1/\omega C$$




$$V_{max} = I_{max} Z$$

- If $X_L > X_C$, current lags voltage:

- If $X_L < X_C$, current leads voltage:

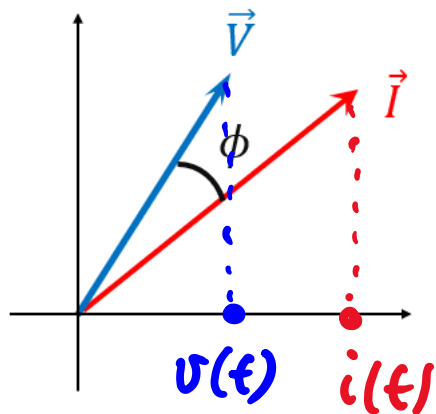

“Impedance triangles”

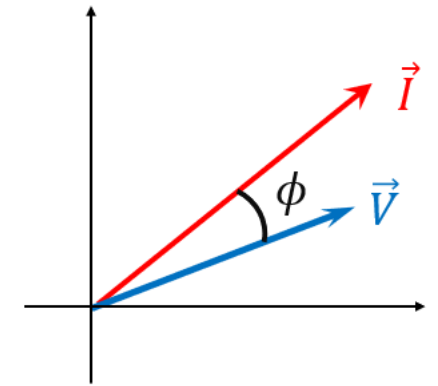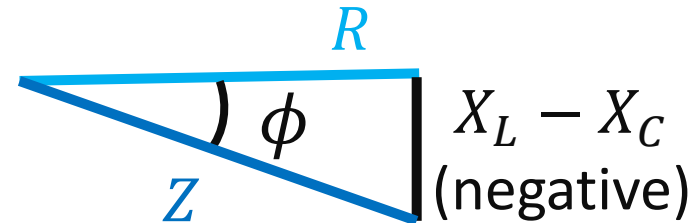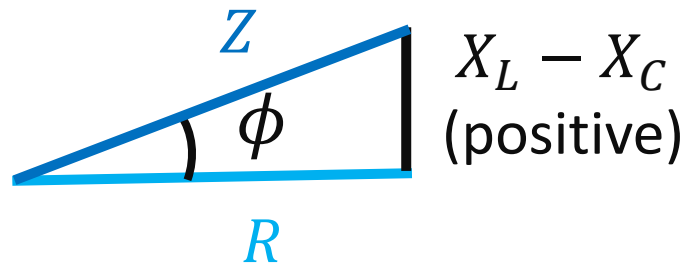

- $i(t) = I_{max} \cos \omega t$
- $v(t) = (I_{max} Z) \cos(\omega t + \phi)$


- $i(t) = I_{max} \cos \omega t$
- $v(t) = (I_{max} Z) \cos(\omega t - |\phi|)$

AC RLC series circuit: Peak and Instantaneous values

$$X_R = R$$

$$X_L = \omega L$$

$$X_C = 1/\omega C$$

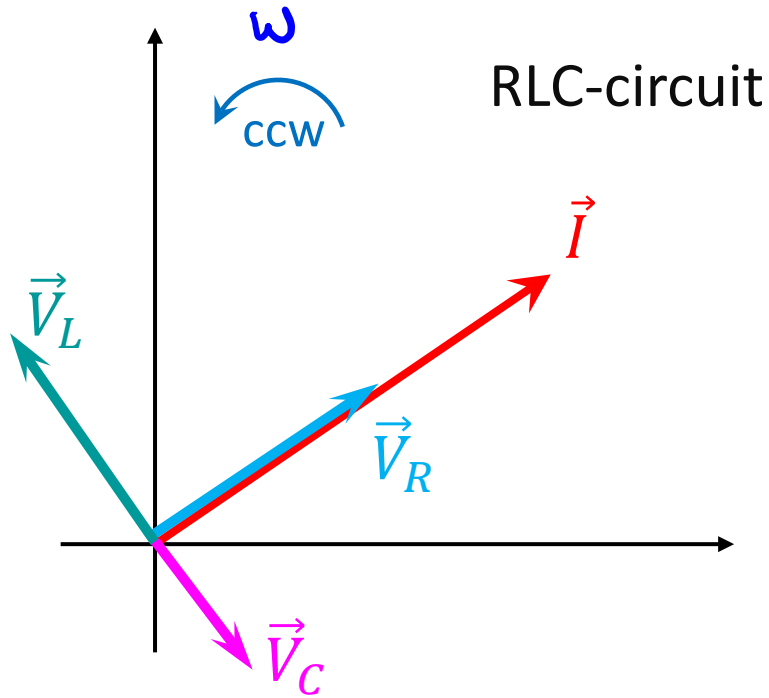

- Peak values across elements:

$$V_R = RI_{max} \quad V_L = X_L I_{max} \quad V_C = X_C I_{max}$$

➤ Note that they do not occur at the same time!

- Peak value of the source voltage: $V_{max} = I_{max} Z$





- Instantaneous values:

$$v_{\text{source}}(t) = v_R(t) + v_L(t) + v_C(t)$$


$$= V_R \cos(\omega t) + V_L \cos(\omega t + \pi/2) + V_C \cos(\omega t - \pi/2)$$

$$= V_{max} \cos(\omega t + \phi)$$
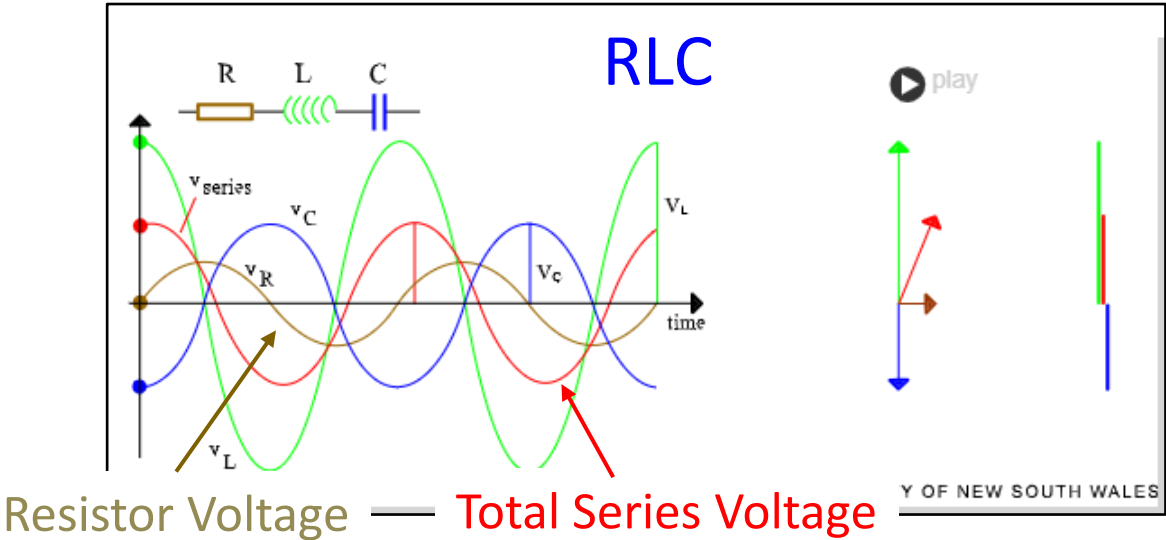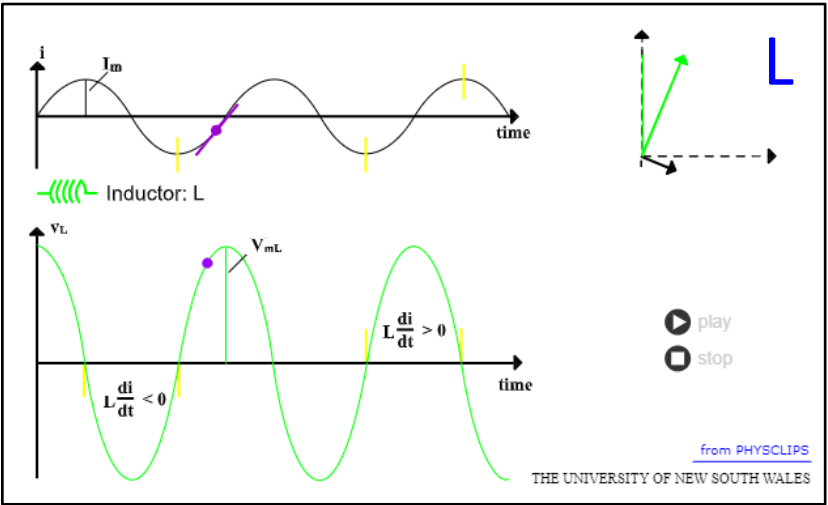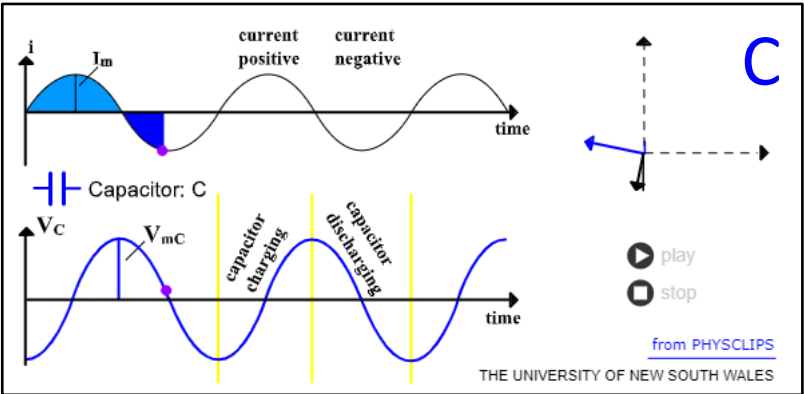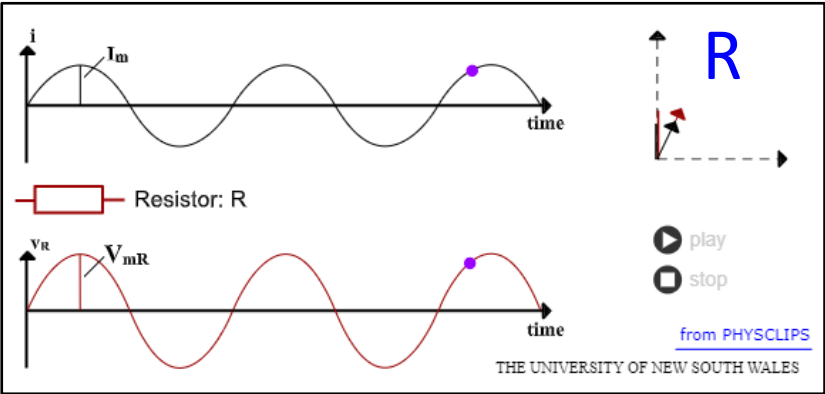
<https://www.animations.physics.unsw.edu.au/jw/AC.html>




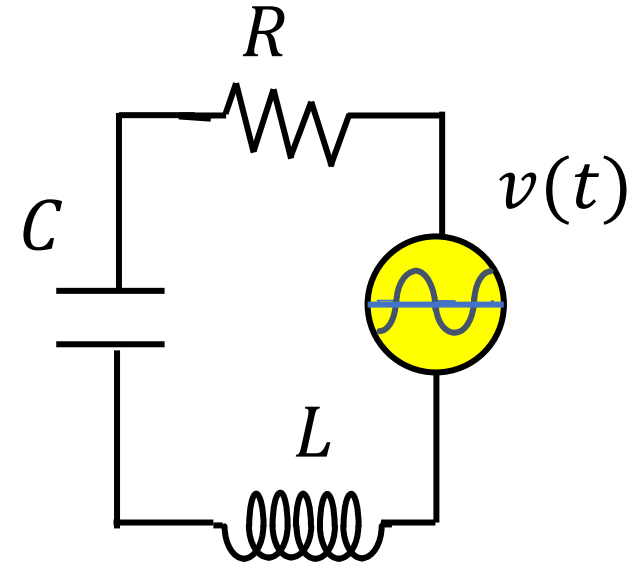Q: What statement below about an RLC circuit is accurate?



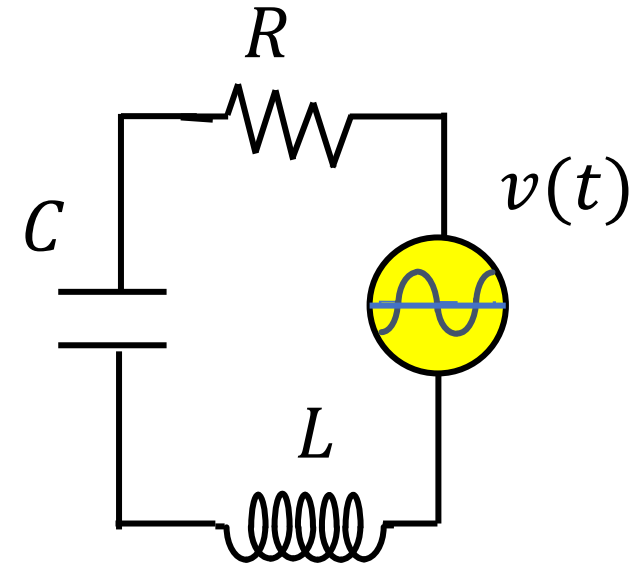- A. The instantaneous voltage v is the same across all three circuit elements
- ☒ B. The instantaneous current i is the same across all three circuit elements
- C. The instantaneous voltage v AND the current i are both the same across all three circuit elements
- D. The instantaneous voltage v AND the current i are NOT always the same across all three circuit elements
- E. Not sure

Q: What statement below about an RLC circuit is accurate?




- All three elements (R, L, and C) in the circuit are in series, so the instantaneous current through them must be the same.

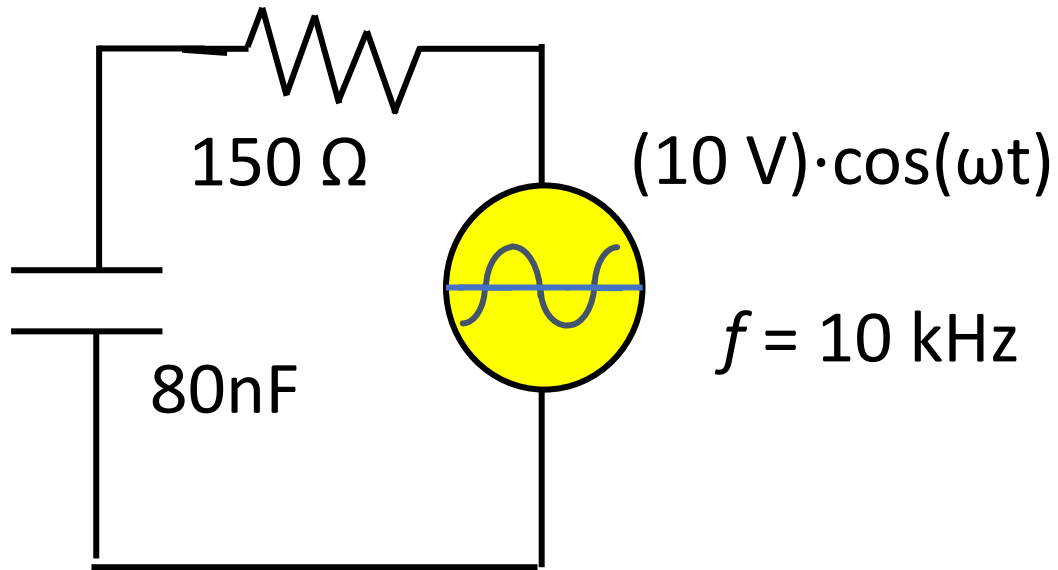- A. The instantaneous voltage v is the same across all three circuit elements
- ☒ B. The instantaneous current i is the same across all three circuit elements
- C. The instantaneous voltage v AND the current i are both the same across all three circuit elements

- The instantaneous voltages v_R , v_L and v_C don't have to be the same, but $v_{\text{source}}(t) = v_R(t) + v_L(t) + v_C(t)$ (algebraic sum at each moment of time).
- Peak voltages add up as vectors: $\vec{V}_{\text{source}} = \vec{V}_R + \vec{V}_L + \vec{V}_C$

- Q: a) What is the peak voltage across the resistor, V_R^{peak} , in this circuit?
b) What is the peak voltage across the capacitor, V_C^{peak} ?




- A. 0 V
- B. 4 V
- C. 6 V
- D. 8 V
- E. 10 V

Q: a) What is the peak voltage across the resistor, V_R^{peak} , in this circuit?

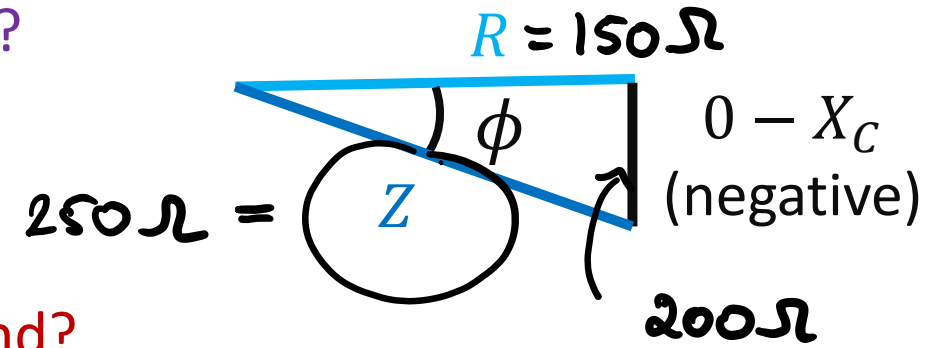
b) What is the peak voltage across the capacitor, V_C^{peak} ?

$$X_C = \frac{1}{\omega C} = 200 \Omega$$

- Start with drawing the phasor diagram!
- Who is in your diagram? Who is ahead, who is behind?
- What do you know in this diagram, what you need to find?


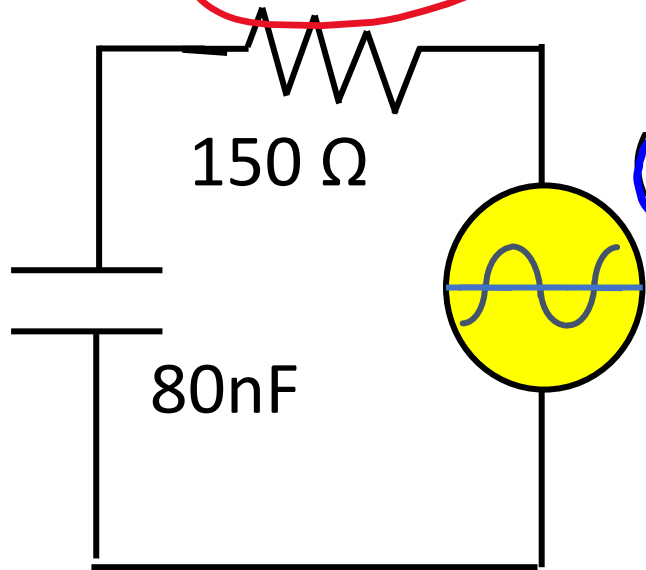
$$I_{\text{max}} = \frac{V_{\text{max}}}{Z}$$




$$V_R = I_{\text{max}} R = V_{\text{max}} \frac{R}{Z} \quad \vec{V}_R / I_{\text{max}} = R$$

$$V_{\text{max}} = (10 \text{ V}) \cdot \cos(\omega t)$$

$$f = 10 \text{ kHz}$$

$$\omega = 2\pi f = 2\pi \cdot 10^4 \frac{\text{rad}}{\text{s}}$$
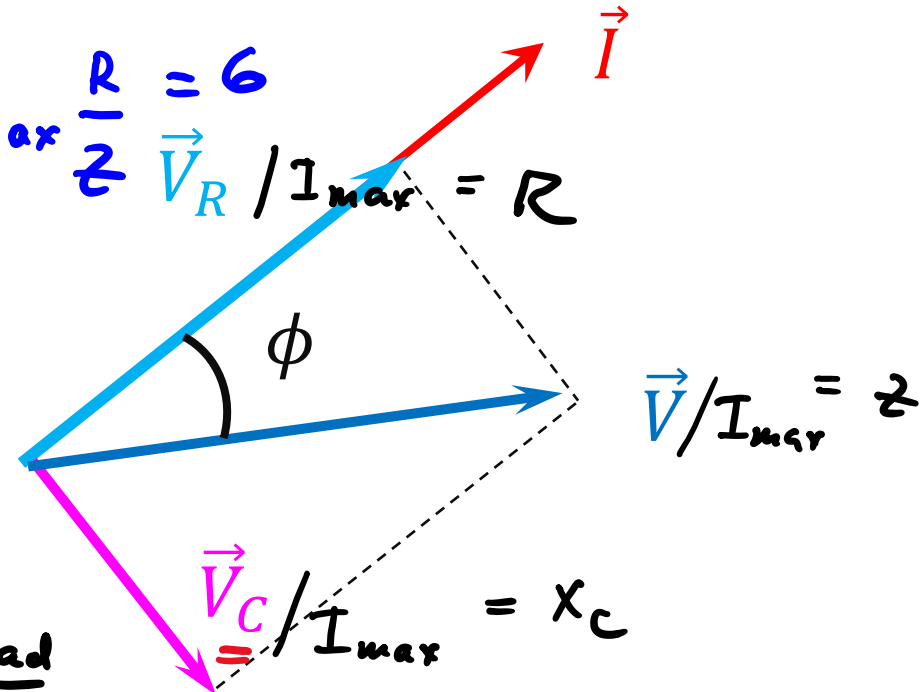
$$V_{\text{max}} \frac{X_C}{Z} = V_C = I_{\text{max}} X_C = 8 \text{ V}$$



A. 0 V

B. 4 V


C. 6 V

D. 8 V

E. 10 V

Q: a) What is the peak voltage across the resistor, V_R^{peak} , in this circuit?

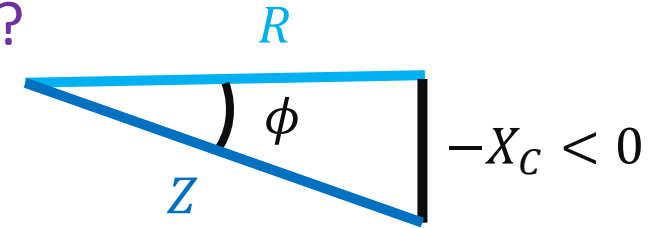
b) What is the peak voltage across the capacitor, V_C^{peak} ?



Current in the circuit is: $I_{\text{peak}} = \frac{V_{\text{peak}}}{Z}$ Both R and C affect the current !!!

$$f = 10 \text{ kHz} \Rightarrow \omega = 2\pi f$$
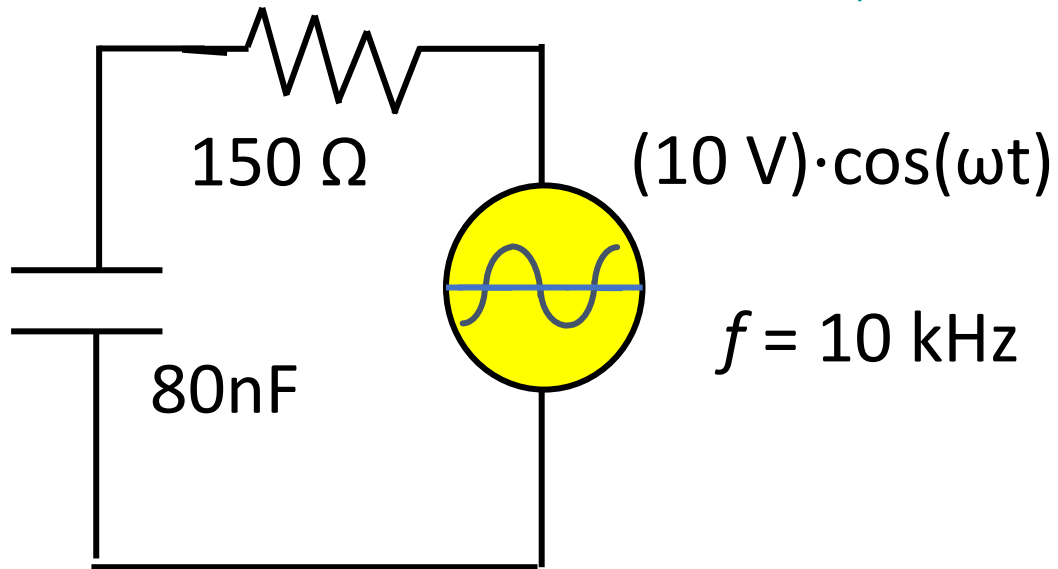
$$Z = \sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2} = \sqrt{(150)^2 + \left(\frac{1}{2\pi \cdot 10^4 \cdot 8 \cdot 10^{-8}}\right)^2} = 250 \Omega$$



$$V_R = I_{\text{peak}} R = V_{\text{peak}} \frac{R}{Z} = 10 \frac{150}{250} = 6 \text{ V}$$

$$V_C = I_{\text{peak}} X_C = V_{\text{peak}} \frac{(1/\omega C)}{Z} = 10 \frac{200}{250} = 8 \text{ V}$$


Q: For this RLC circuit:

a) Determine the impedance

b) Determine I_{peak}

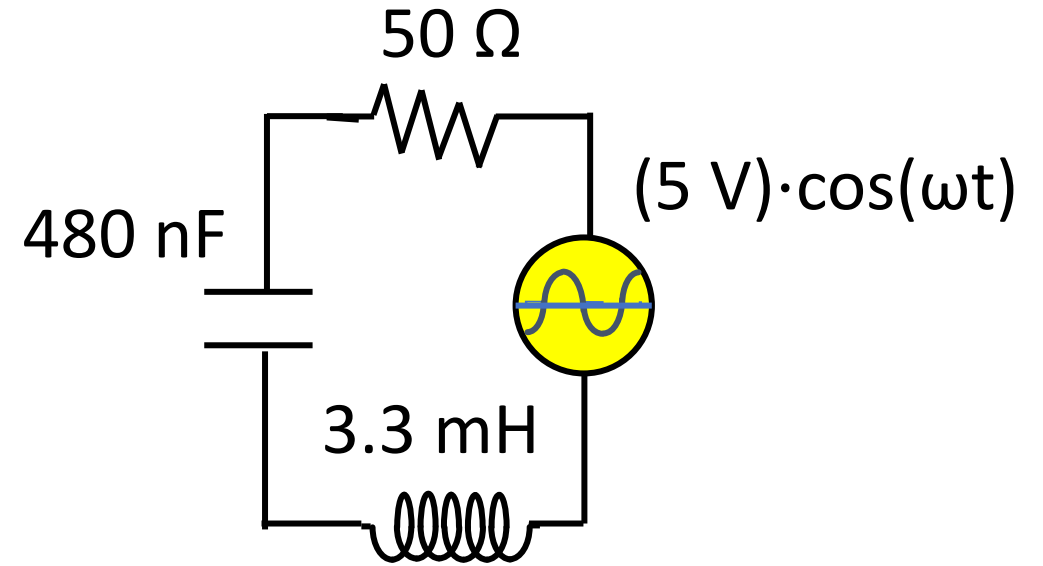c) Determine ϕ at $f = 3\text{kHz}$, 4kHz , & 5kHz .

Does the current lead or lag the voltage?



Q: For this RLC circuit:

a) Determine the impedance

b) Determine I_{peak}



c) Determine ϕ at $f = 3\text{kHz}, 4\text{kHz}, \& 5\text{kHz}$

- Set up impedance triangle:

$$X_R = R$$

$$X_L = \omega L$$

$$X_C = 1/\omega C$$

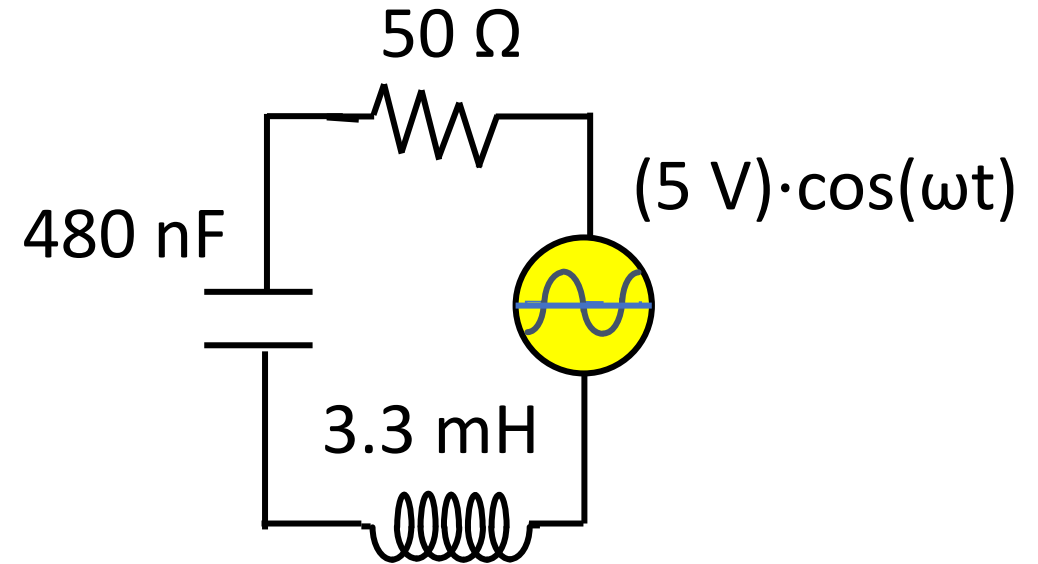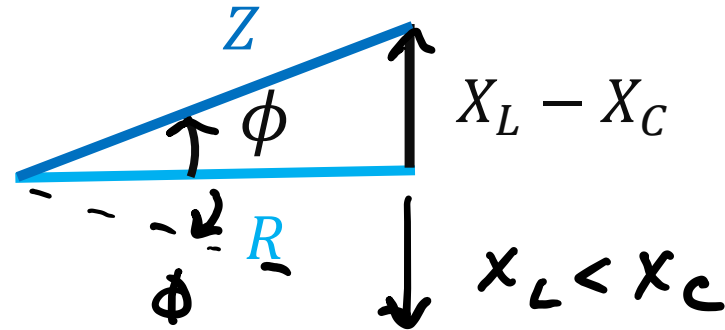

$$\omega = 2\pi f$$

- Note that angle ϕ can be positive or negative, we have to compute X_L and X_C to know for sure

- Now:

$$Z^2 = R^2 + (X_L - X_C)^2$$

$$Z(\omega) = \sqrt{(20\ \Omega)^2 + \left(\omega(3.3\ \text{mH}) - \frac{1}{\omega(480\ \text{nF})} \right)^2}$$

Q: For this RLC circuit:


a) Determine the impedance

b) Determine I_{peak}

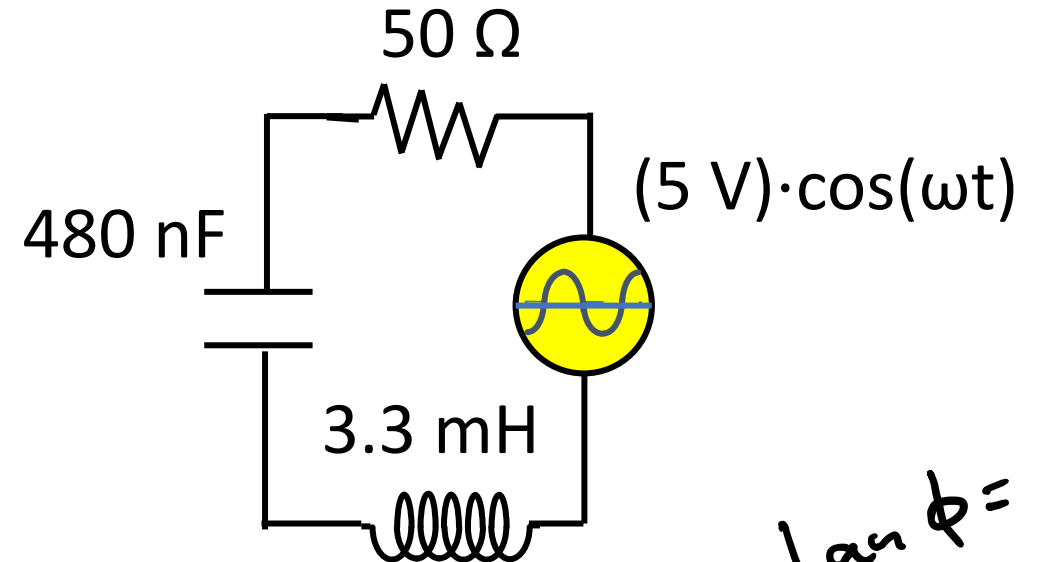
c) Determine ϕ at $f = \underline{3\text{kHz}}$, $\underline{4\text{kHz}}$, & $\underline{5\text{kHz}}$.

Does the current lead or lag the voltage?

- I_{peak} is linked to V_{peak} of the source voltage by the impedance:



$$\tan \phi = \frac{X_L - X_C}{R}$$

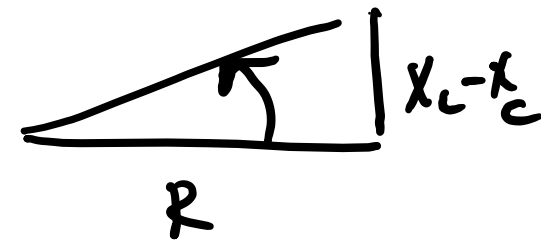

$$f \rightarrow \omega$$

$$I_{peak}(\omega) = \frac{V_{peak}}{Z} = \frac{5\text{ V}}{\sqrt{(50\ \Omega)^2 + \left(\omega(3.3\text{ mH}) - \frac{1}{\omega(480\text{ nF})}\right)^2}}$$

The peak current depends on the oscillation frequency $\omega = 2\pi f$

Q: For this RLC circuit:

a) Determine the impedance

b) Determine I_{peak}

c) Determine ϕ at $f = 3\text{kHz}$, 4kHz , & 5kHz .


Does the current lead or lag the voltage?

• Set up impedance triangle:

$$X_R = R$$

$$X_L = \omega L$$


$$X_C = 1/\omega C$$

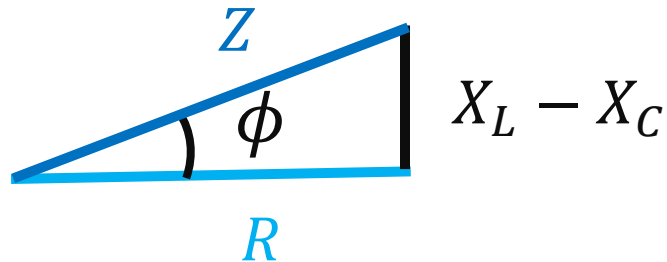


$$f \Rightarrow \omega = 2\pi f$$

• Phase:
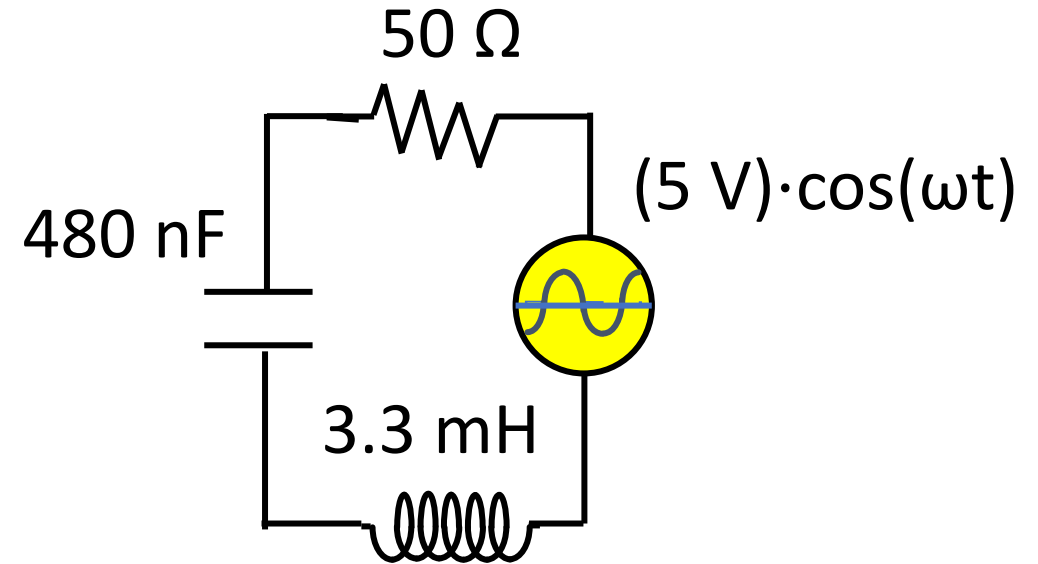
$$\phi(\omega) = \tan^{-1} \left(\frac{X_L - X_C}{R} \right)$$



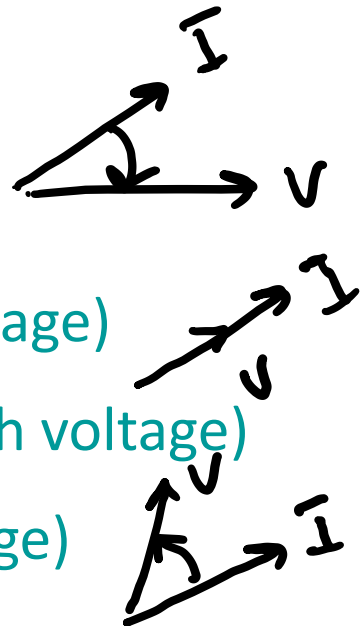- $\phi(3\text{ kHz}) = -44^\circ$ (Current leads voltage)
- $\phi(4\text{ kHz}) = 0^\circ$ (Current in phase with voltage)
- $\phi(5\text{ kHz}) = +37^\circ$ (Current lags voltage)



Q: An AC circuit with $V_{peak} = 150 \text{ V}$ and $f = 50 \text{ Hz}$ drives this RLC circuit.

a) What is the peak voltage across the resistor?

b) What is the peak voltage across the inductor?

$$f = 50 \text{ Hz} \rightarrow \omega = 2\pi f = 314.2 \frac{\text{rad}}{\text{s}}$$

$$\frac{1}{\omega C} = X_C = \dots 50 \Omega$$

$$L \cdot \omega = X_L = \dots 58.1 \Omega$$

$$Z = \dots 40.8 \Omega = \sqrt{R^2 + (X_L - X_C)^2}$$

A. 0 V

B. 4 V


C. 120 V

D. 145 V

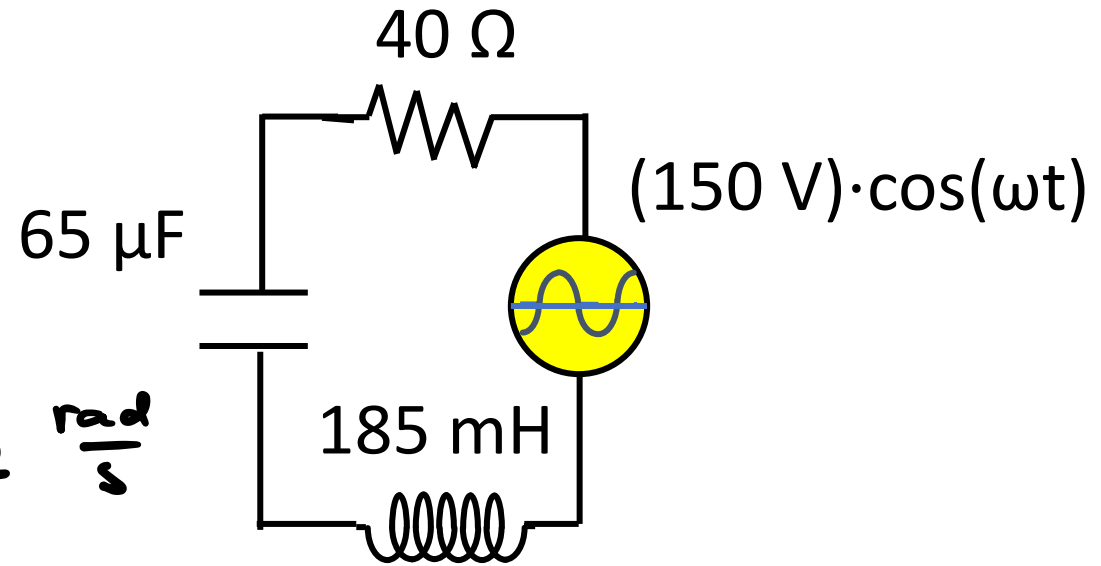E. 215 V


$$V_R = \dots V_{max} \frac{R}{Z} = 145 \text{ V}$$

$$V_L = \dots V_{max} \frac{X_L}{Z} = 215 \text{ V}$$



Q: An AC circuit with $V_{peak} = 150 \text{ V}$ and $f = 50 \text{ Hz}$ drives this RLC circuit.

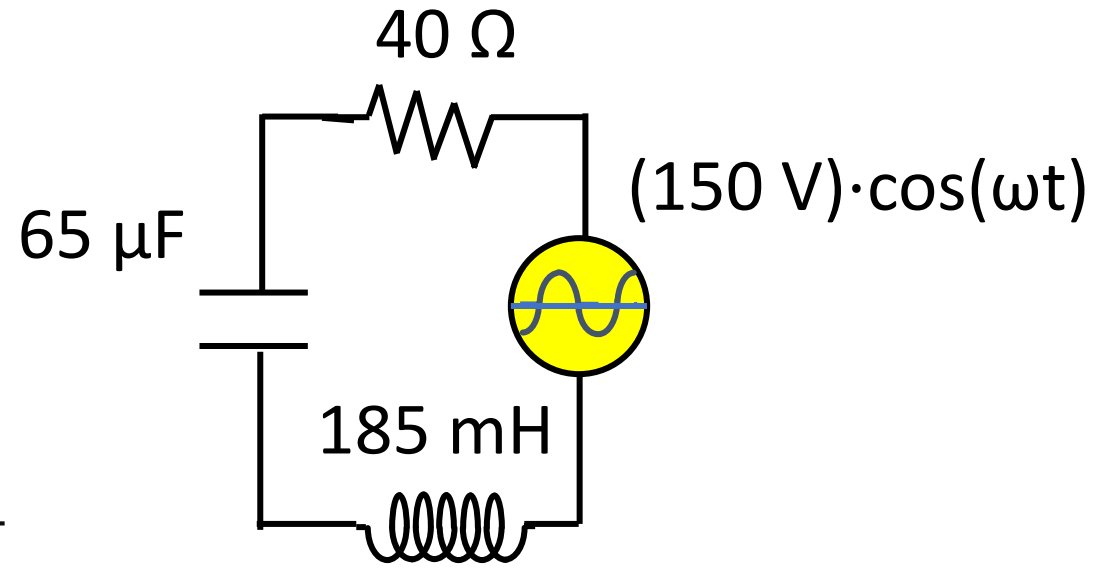- What is the peak voltage across the resistor?
- What is the peak voltage across the inductor?



- Compute I_{peak} with Ohm's law: $I_{peak} = \frac{V_{peak}}{Z}$

$$\left. \begin{array}{l} X_L = 2\pi(50)(185 \times 10^{-3}) = 58 \Omega \\ X_C = 49 \Omega \end{array} \right\} Z = \sqrt{40^2 + (58.1 - 49)^2} = 41 \Omega$$

- 0 V
- 4 V
- 120 V
- 145 V
- 215 V

- Applying Ohm's law to R and L:

$$V_R = I_{peak} R = V_{peak} \frac{R}{Z} = 150 \cdot \frac{40}{41} = 146 \cancel{\Omega} \checkmark$$

$$V_L = I_{peak} X_L = V_{peak} \frac{X_L}{Z} = 150 \cdot \frac{58}{41} = 212 \cancel{\Omega} \checkmark$$

larger
than
 $V_{max} ???$
(next time)