




- What is your personal preference in case of a longer Translink strike?

- A. Strongly prefer in-person lectures to continue 34%
- B. Simply can't get to the campus & need zoom lectures 34%
- C. No strong preference, both ways work for me. 32%

❖ We will try to come up with a solution that addresses everybody's needs, and it's good to know how your preferences split.

Q: An AC circuit with $V_{peak} = 150\text{ V}$ and $f = 50\text{ Hz}$ drives this RLC circuit.

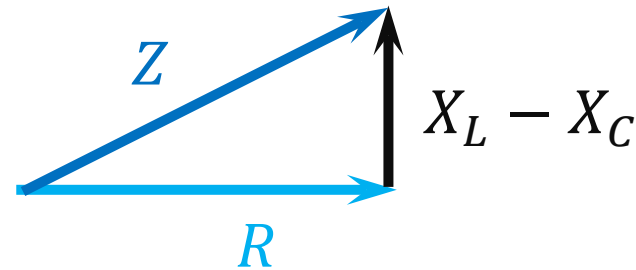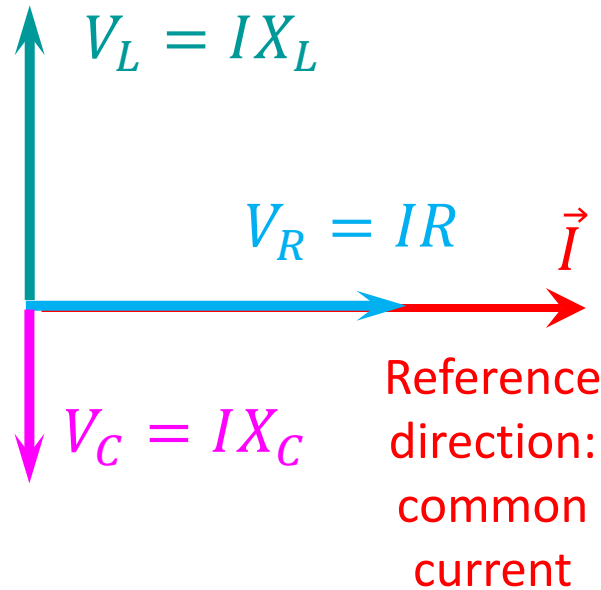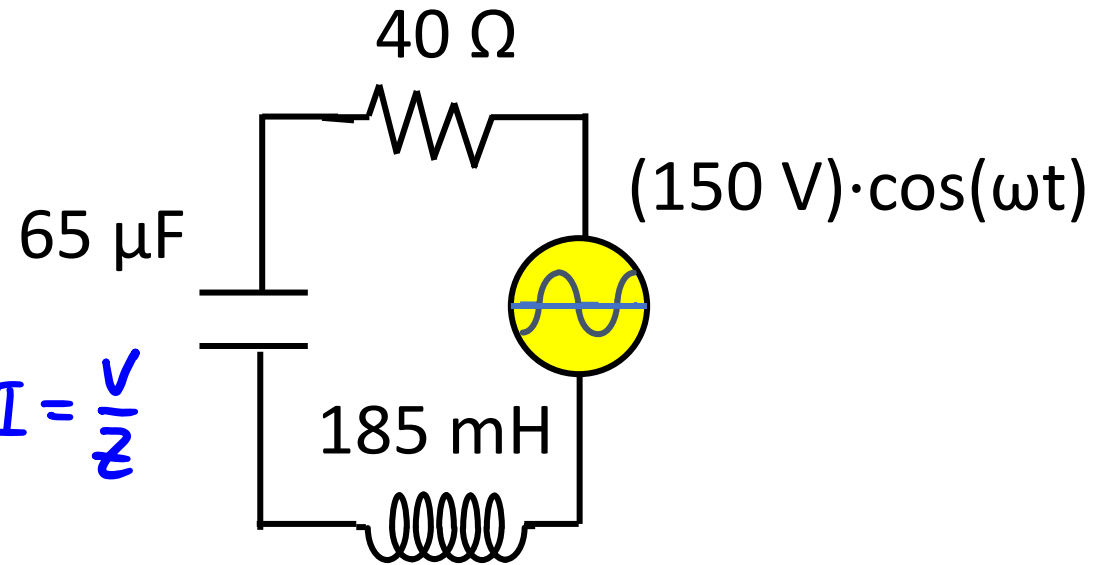- What is the peak voltage across the resistor?
- What is the peak voltage across the inductor?



$$X_L = \omega L = 58\ \Omega$$

$$X_C = \frac{1}{\omega C} = 49\ \Omega$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = 40.8\ \Omega$$

- 0 V
- 4 V
- 120 V
- 145 V
- 215 V


$$V_R = I_{max} R = V_{max} \frac{R}{Z} = 147\text{ V},$$

$$V_L = I_{max} L = V_{max} \frac{X_L}{Z} = 214\text{ V}$$

Q: An AC circuit with $V_{peak} = 150 \text{ V}$ and $f = 50 \text{ Hz}$ drives this RLC circuit.

- What is the peak voltage across the resistor?
- What is the peak voltage across the inductor?

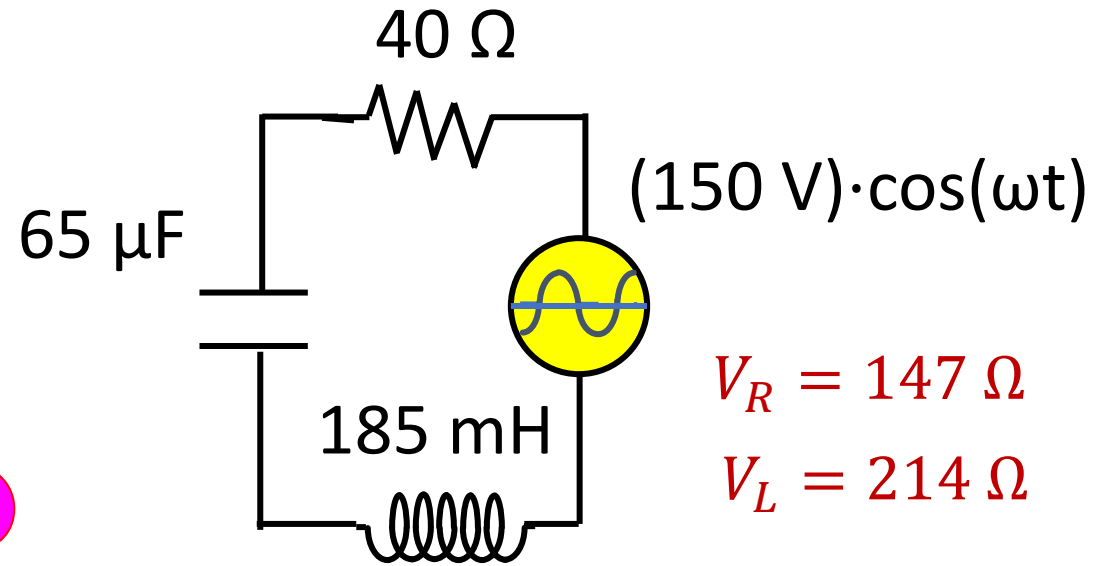! Wait!! -- How can the peak voltage across the inductor be larger than the source voltage ?? ?



ANSWER: Kirchhoff's voltage law ALWAYS applies. In this case, the addition of instantaneous voltages involves both the **amplitude** and the **phase** of the instantaneous voltages.

$$v_{\text{source}}(t) = v_R(t) + v_L(t) + v_C(t)$$

$$V_{\text{max}} \cos \omega t \quad \downarrow \quad \downarrow$$


$$V_R \cos \omega t \quad V_L \cos(\omega t + \pi/2)$$

$\nearrow V_C \cos(\omega t - \pi/2)$

When the voltage across the inductor is at max, the phases of the R and C are **negative**, and the three voltages add up to the source voltage, as it should be.

Application: electronic filters


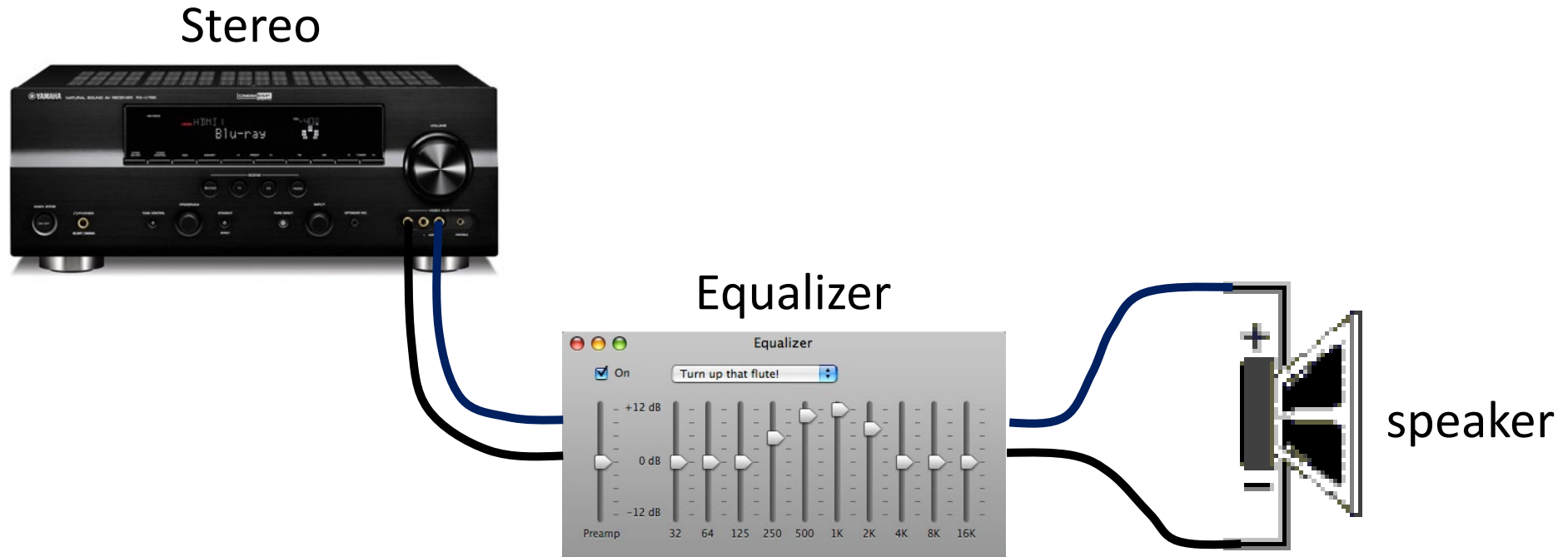
- What is the equalizer doing to the electrical signal coming out of the stereo?
- Specifically, if you want more **bass** in your music (i.e. **higher voltage for low frequencies ω**), what does the equalizer do to the output signal from the stereo ?



Q: Which of the electrical circuits below could be used as a low pass filter?


$\omega \downarrow$ ~~$\omega \uparrow$~~

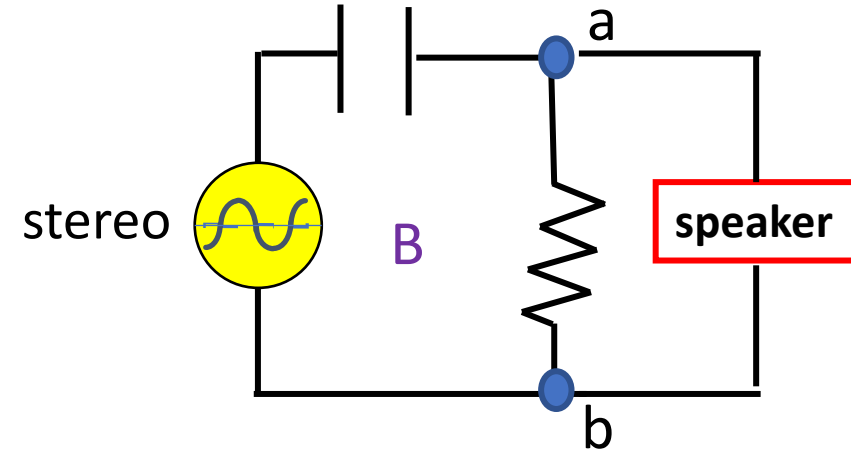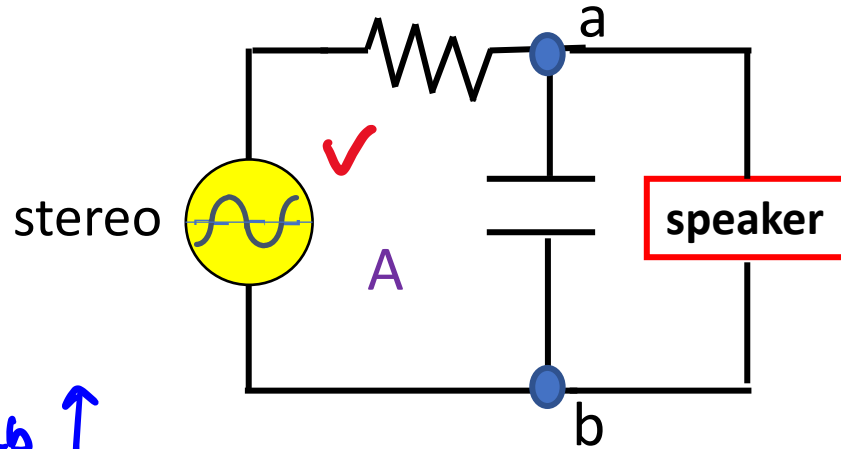"Low pass filter" : attenuate the higher frequencies = higher voltage for lower frequencies




$\Delta V_{ab} = ?$

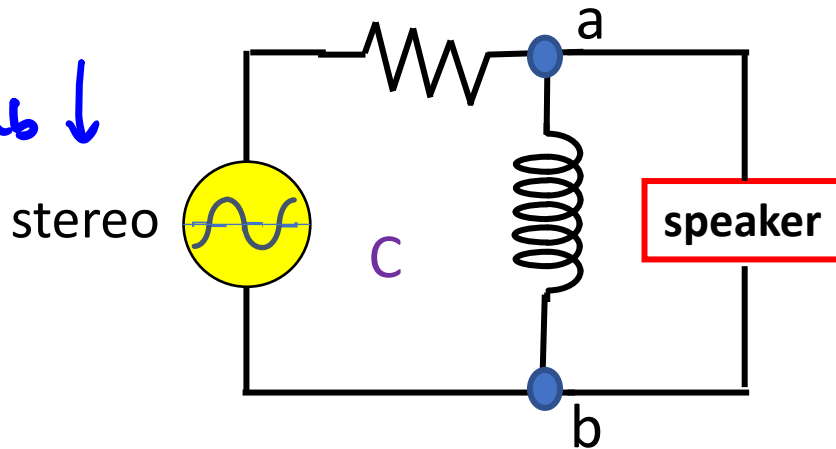$\omega \downarrow$ $\Delta V_{ab} \uparrow$



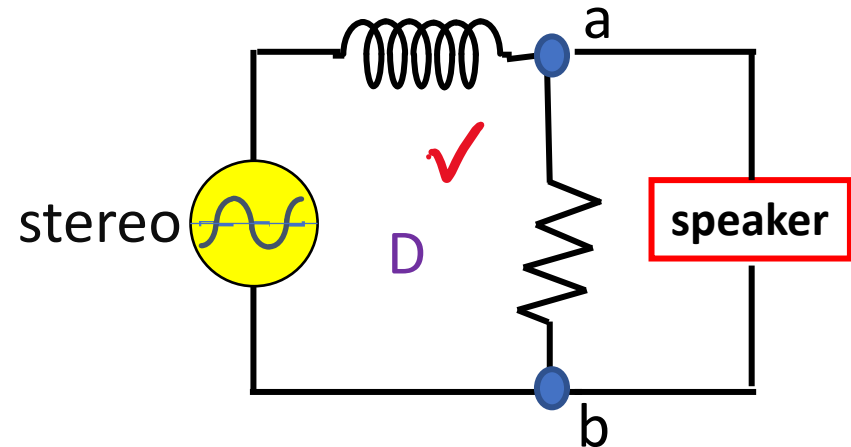~~$\omega \uparrow$~~ $\Delta V_{ab} \downarrow$



$$X_L = L\omega$$





$$X_C = \frac{1}{C\omega}$$

E. More than one could work

$$\Delta V_{R,L,C} = I X_{R,L,C}$$

Q: Which of the electrical circuits below could be used as a low pass filter?

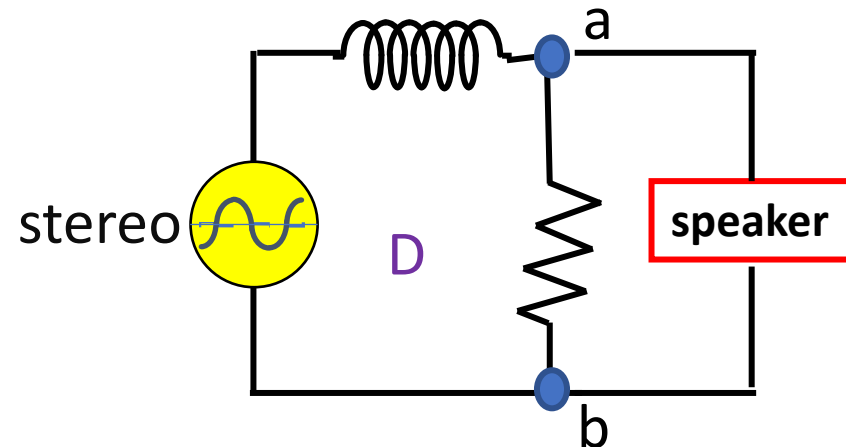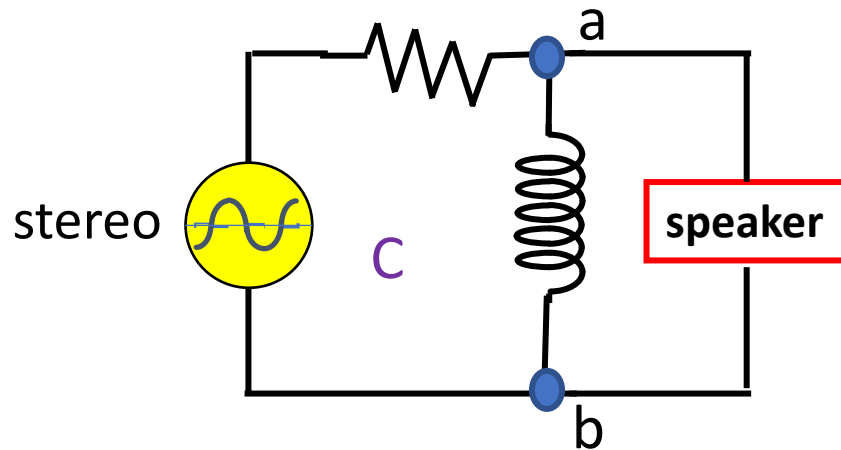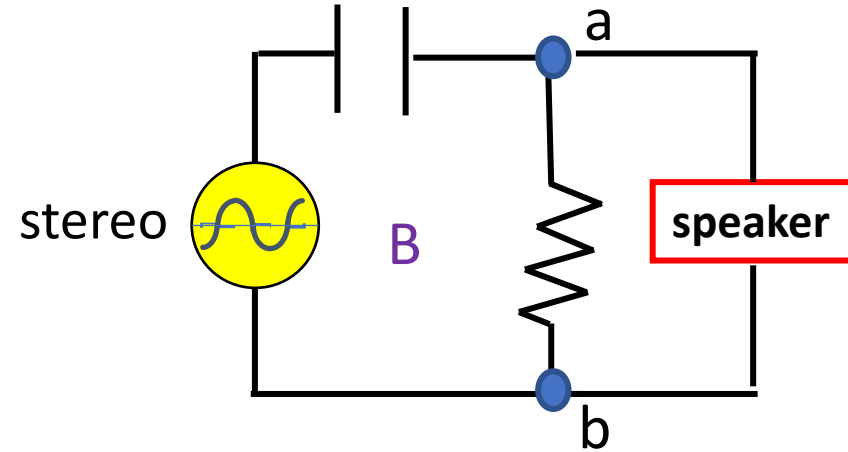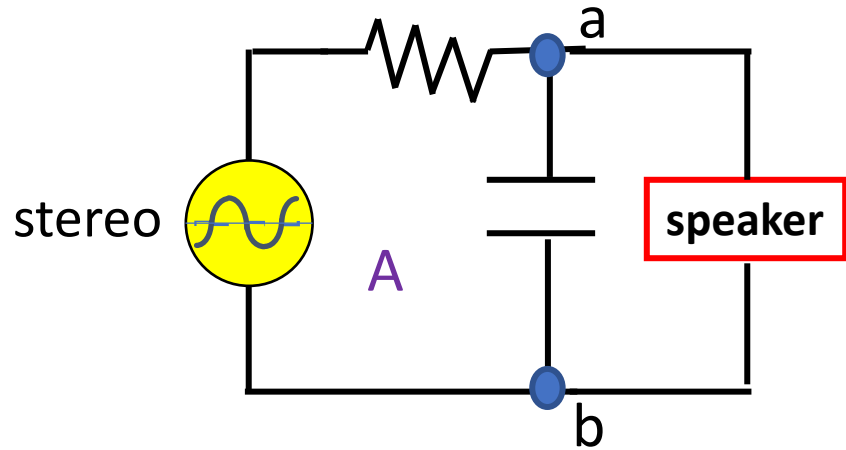"Low pass filter" : attenuate the higher frequencies = higher voltage for lower frequencies





E. More than one could work

A & D

Q: Which of the electrical circuits below could be used as a low pass filter?

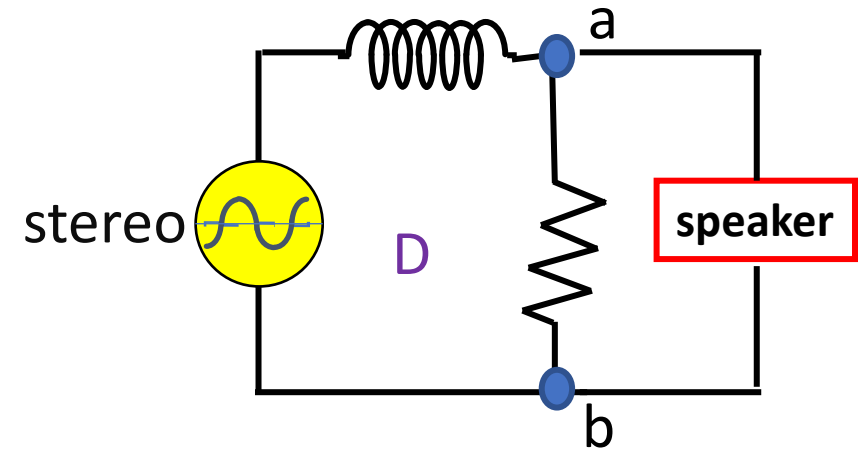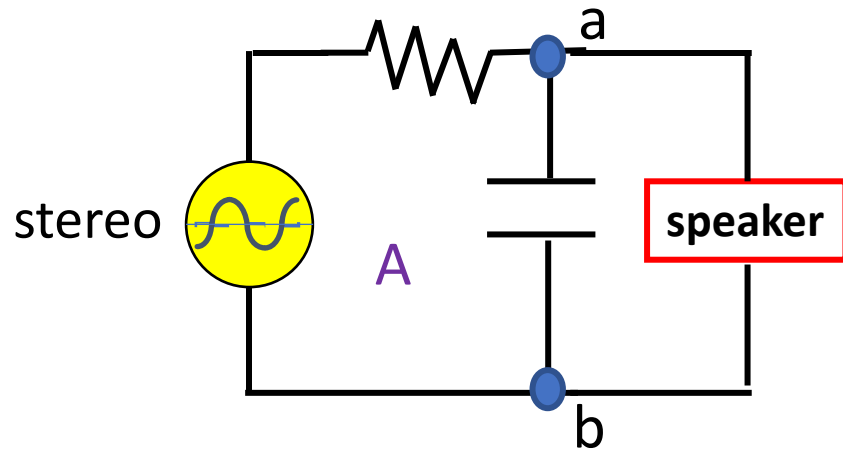”Low pass filter” : attenuate the higher frequencies = higher voltage for lower frequencies



- Voltage drops across the two circuit elements in the left loop always add up to the source voltage => it's the question about how the voltage drops will be distributed among these two elements;

- $V_{\text{speaker}} = V_{ab}$

$$X_C = \frac{1}{\omega C} \rightarrow 0 \text{ as } \omega \rightarrow \infty$$

$$X_C = \frac{1}{\omega C} \rightarrow \infty \text{ as } \omega \rightarrow 0$$

- Thus, V_{ab} is larger for low frequencies

$$X_L = \omega L \rightarrow \infty \text{ as } \omega \rightarrow \infty$$

$$X_C = \frac{1}{\omega C} \rightarrow 0 \text{ as } \omega \rightarrow 0$$



- Thus, V_{ab} is larger for low frequencies

Power dissipation in AC circuits (Ch 31.4)


$$\underline{v_R = IR}$$

- From DC circuits: $P_R = IV = I^2 R = \frac{V^2}{R}$
- For AC circuits: $\langle P \rangle = \langle i(t)v(t) \rangle_T$ (average over a period)

pure R

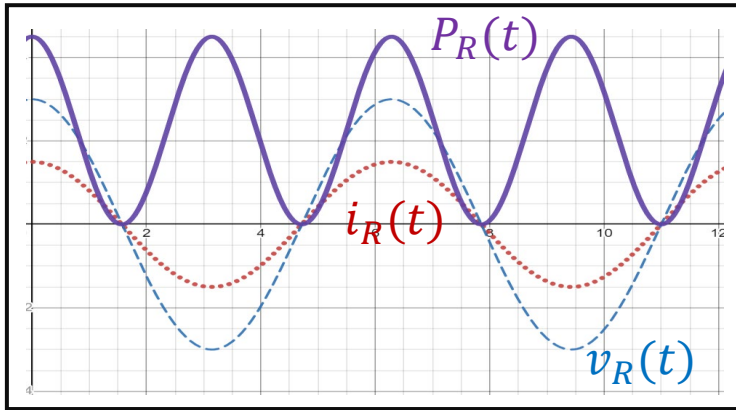
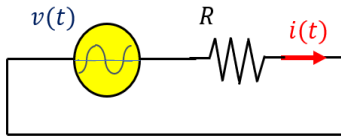


- Averages to something!

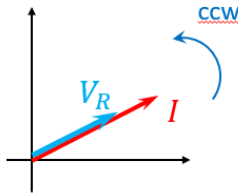


$$\langle P_R \rangle \propto \frac{1}{T} \int_0^T \cos(x) \cos(x) dx$$

pure L

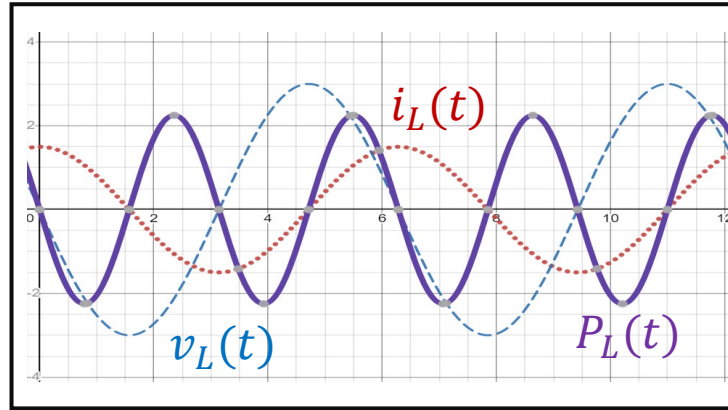
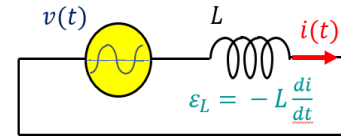


- Averages to zero!

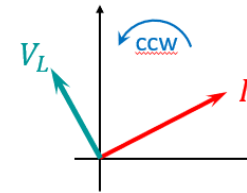


$$\langle P_L \rangle \propto \frac{1}{T} \int_0^T \cos(x) \cos(x - \frac{\pi}{2}) dx$$

pure C

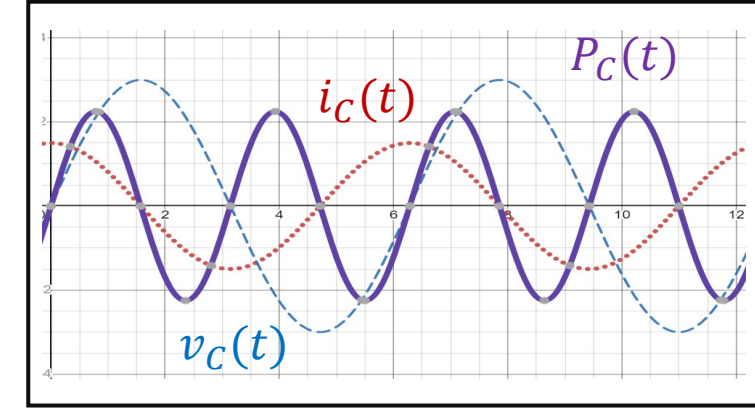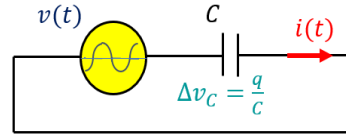


- Averages to zero!

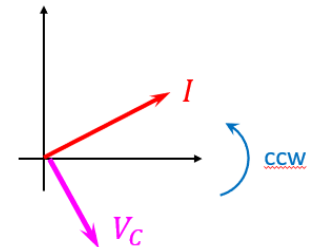

$$\langle P_C \rangle \propto \frac{1}{T} \int_0^T \cos(x) \cos(x + \frac{\pi}{2}) dx$$

Power dissipation in AC Series circuits

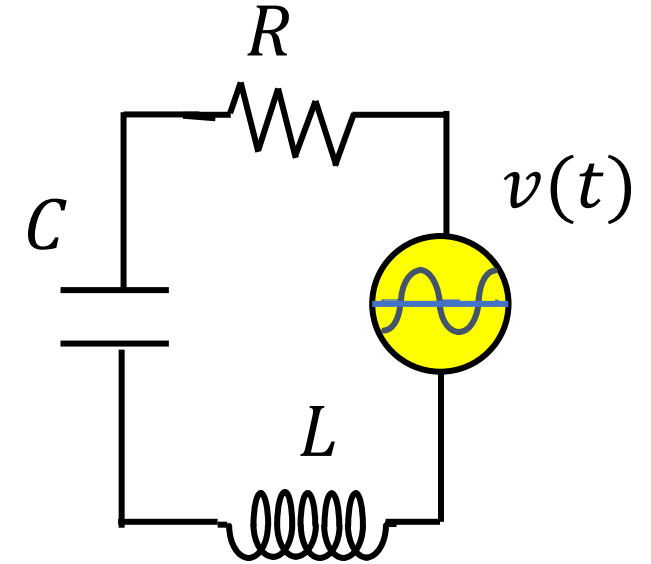
- Q: In which of these elements can the power be dissipated?
- A: Only in the resistor! The voltage phasors for R, L and C are in phase with / $\frac{\pi}{2}$ ahead / $\frac{\pi}{2}$ behind the current => the average over the period will give something / zero / zero.



$$\langle P_{RLC} \rangle = \frac{1}{T} \int_0^T v(t) i(t) dt \quad v(t) = V_{peak} \cos(\omega t) \quad i(t) = I_{peak} \cos(\omega t - \phi)$$

$$\langle P_{RLC} \rangle = \frac{V_{peak} I_{peak}}{T} \int_0^T \cos(\omega t) \cos(\omega t - \phi) dt =$$
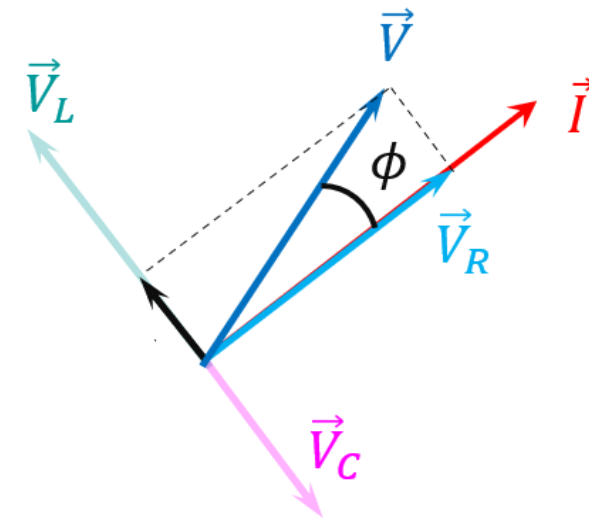
$$= \frac{V_{peak} I_{peak}}{T} \cdot \frac{1}{2} \int_0^T (\underbrace{\cos(2\omega t - \phi)}_0 + \underbrace{\cos \phi}_{const}) dt = \frac{V_{peak} I_{peak}}{2} \cos \phi$$



Power dissipation in AC Series circuits


$$\langle P_{RLC} \rangle = \frac{V_{peak} I_{peak}}{2} \cos \phi = V_{rms} I_{rms} \cos \phi$$

- $\cos \phi$: the power factor

- Note that $V_{peak} \cos \phi = V_R$


$$\langle P_{RLC} \rangle = \frac{V_R I_{peak}}{2} = \frac{I_{peak}^2 R}{2}$$

- L and C: modify voltage drop across R

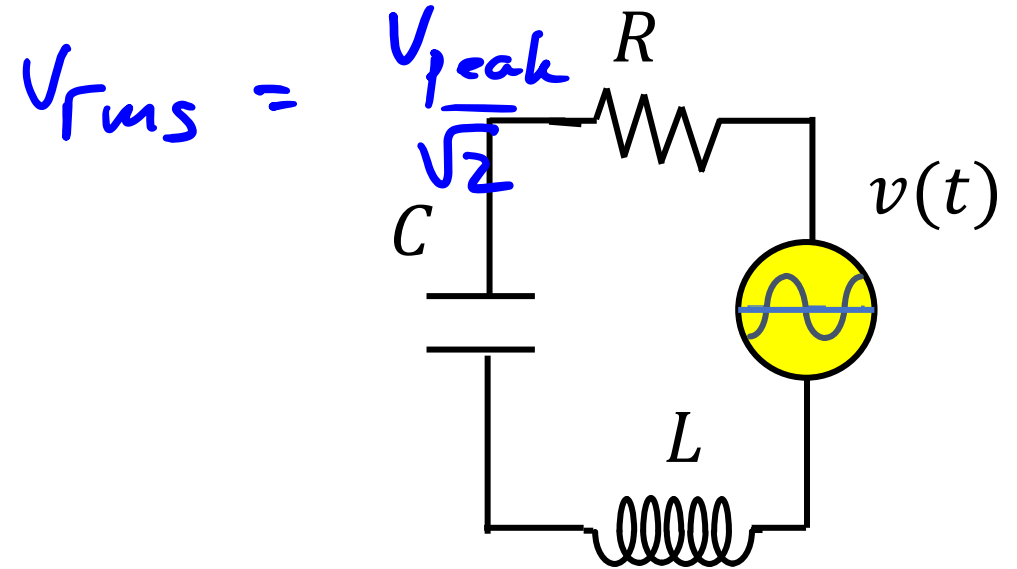

$$V_R = IR$$

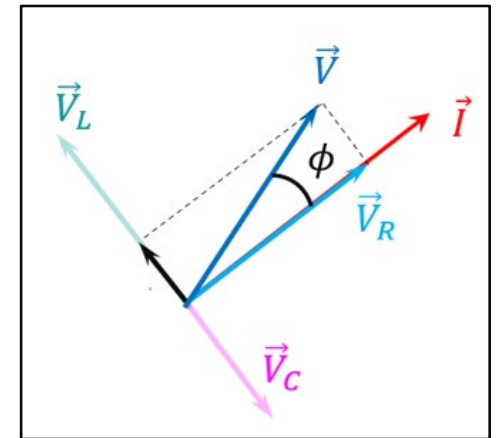- $\frac{1}{2}$ comes from averaging over the cycle, $V_R = I_{peak} R$ from the fact that **all this power dissipates in the resistor**




Resonance in AC circuits - 1

- Imagine that the frequency ω of the voltage source V_{max} is changed smoothly.
- What happens to the current in an RLC circuit?

$$I = \frac{V_{source}}{Z} = \frac{V_{source}}{\sqrt{R^2 + (X_L - X_C)^2}}$$

$$v(t) = V_{max} \cos(\omega t)$$

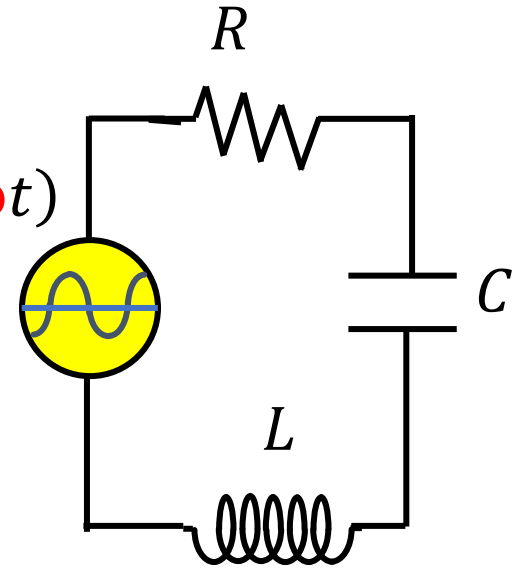

- Current as a function of ω :

$$I(\omega) = \frac{V_{source}}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$

- First of all, let's look at the limiting cases, $\omega \rightarrow 0$ and $\omega \rightarrow \infty$.

Resonance in AC circuits - 2


- Current as a function of ω :

$$I(\omega) = \frac{V_{max}}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$

$$v(t) = V_{max} \cos(\omega t)$$

- $\omega \rightarrow 0: I(\omega) \rightarrow 0$

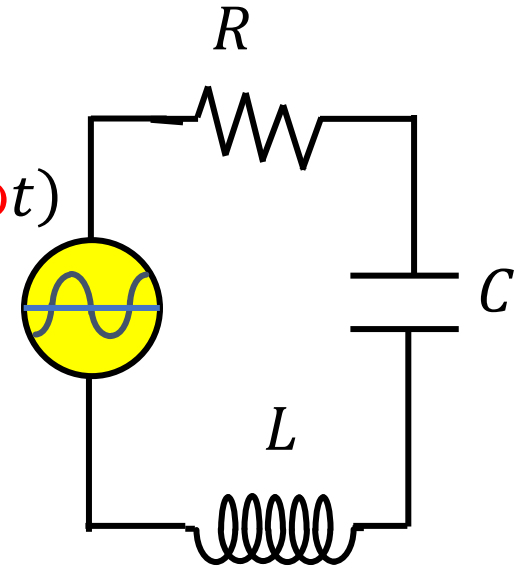- $\omega \rightarrow \infty: I(\omega) \rightarrow 0$



- Since $I = 0$ at both limits, it suggests that it must have a maximum somewhere in between!

- Maximum: $(X_L = \omega L) = (X_C = 1/\omega C)$ (the bracket in the denominator disappears)

- Hence, the maximum is reached at:

$$\omega = \omega_0 = \frac{1}{\sqrt{LC}}$$

- Resonance frequency

- At maximum:

$$I(\omega) = I_{max} = \frac{V_{max}}{R}$$


Resonance in AC circuits - 3

$$I(\omega) = \frac{V_{max}}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$

$$I_{max} = \frac{V_{max}}{R}$$

$$\omega = \omega_0 = \frac{1}{\sqrt{LC}}$$

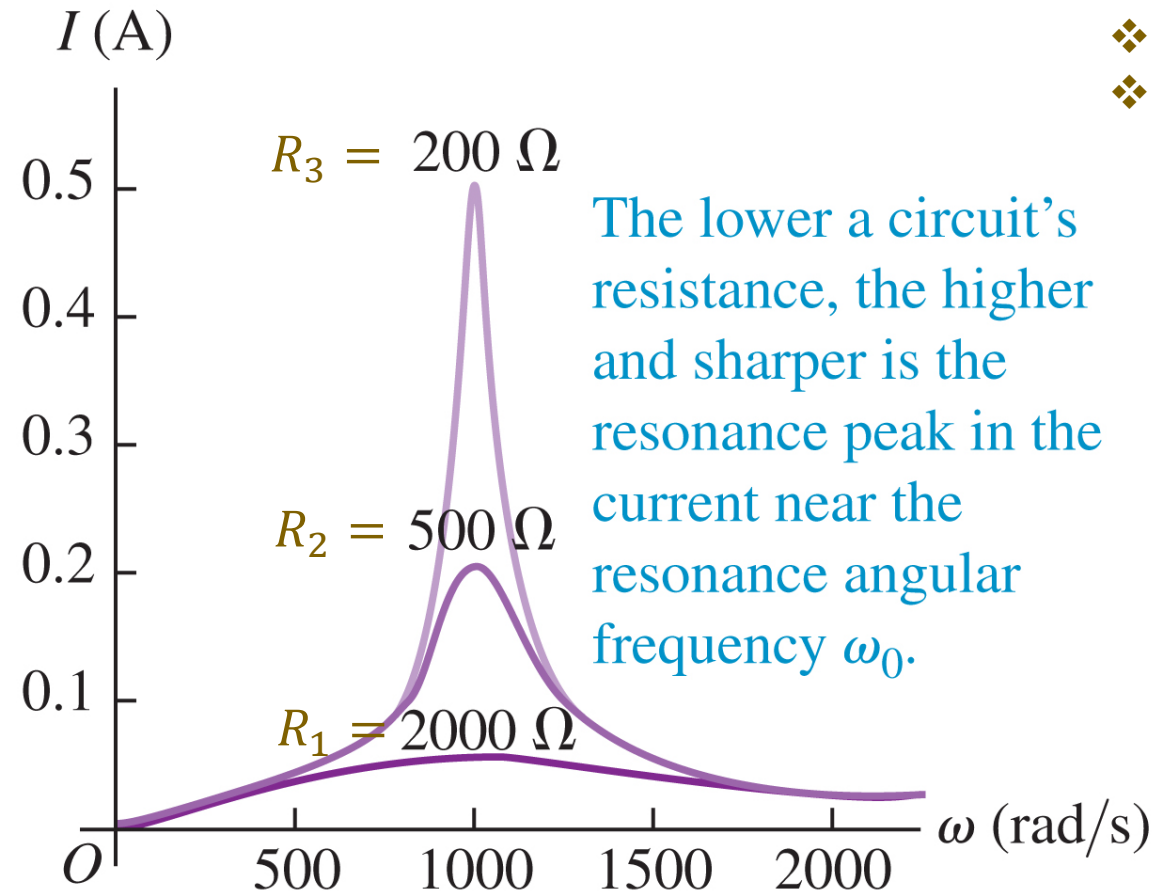- ❖ $V_{max} = 100 \text{ V}$
- ❖ $L = 2 \text{ H}$
- ❖ $C = 0.5 \mu\text{F}$



© 2020 Pearson Education, Inc.

- Q: What does the expression for ω_0 remind you of?
- A: It's the natural frequency of oscillations in an LC-circuit!


Application of resonance in AC circuits

↖ f

Q: An AM radio station picks up a 1 MHz signal with a peak voltage of 5 mV. The tuning circuit consists of a 60 μH inductor in series with a variable capacitor C . The circuit has a small resistance of 0.25Ω .

To what value should the capacitor be tuned to listen to this AM radio station? Pick the closest answer.

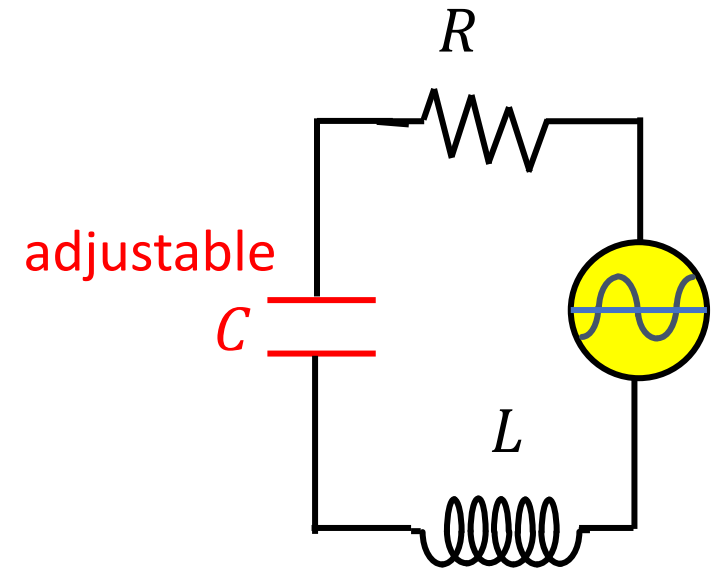- A. $1.5 \times 10^{-2} \text{ F}$
- B. $2.7 \times 10^{-3} \text{ F}$
- C. $5.0 \times 10^{-6} \text{ F}$
- D. $1.7 \times 10^{-8} \text{ F}$
- E. $4.0 \times 10^{-10} \text{ F}$



$$2\pi f = \omega_0 = \frac{1}{\sqrt{LC}}$$

Application of resonance in AC circuits


Q: An AM radio station picks up a 1 MHz signal with a peak voltage of 5 mV. The tuning circuit consists of a 60 μH inductor in series with a variable capacitor C. The circuit has a small resistance of 0.25 Ω .

To what value should the capacitor be tuned to listen to this AM radio station? Pick the closest answer.

$$\bullet \omega_0 = \frac{1}{\sqrt{LC}} = 2\pi f_{\text{station}}$$

$$\bullet C = \frac{1}{(2\pi f_{\text{station}})^2 L} = \frac{1}{(2\pi \cdot 10^6)^2 (60 \cdot 10^{-6})}$$
$$= 4.2 \cdot 10^{-10} = 420 \text{ pF}$$

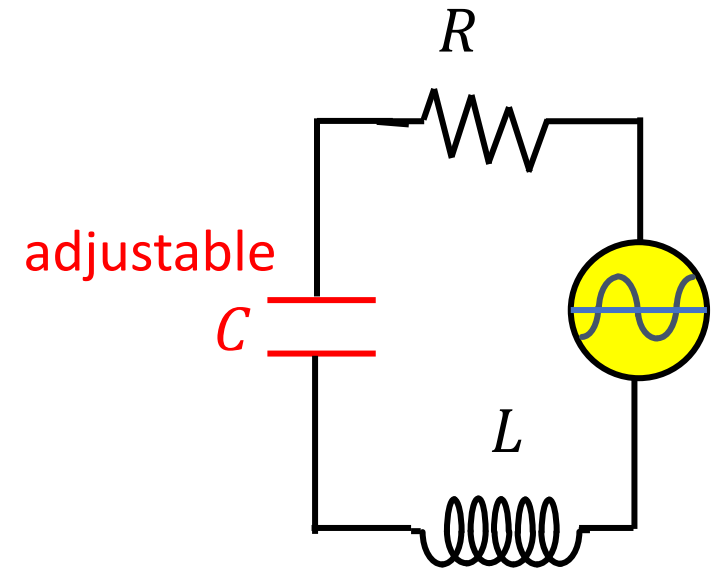- A. $1.5 \times 10^{-2} \text{ F}$
- B. $2.7 \times 10^{-3} \text{ F}$
- C. $5.0 \times 10^{-6} \text{ F}$
- D. $1.7 \times 10^{-8} \text{ F}$
- ☒ E. $4.0 \times 10^{-10} \text{ F}$



Application of resonance in AC circuits

Q: An AM radio station picks up a 1 MHz signal with a peak voltage of 5 mV. The tuning circuit consists of a 60 μH inductor in series with a variable capacitor C. The circuit has a small resistance of 0.25Ω .

What is the peak current through this circuit on resonance? Pick the closest answer.


$$C = 420 \text{ pF}$$

- A. 1 mA
- B. 20 mA
- C. 50 mA
- D. 100 mA
- E. 350 mA

@ Res:

$$I_{\text{peak}} = \frac{V_{\text{peak}}}{R}$$

adjustable

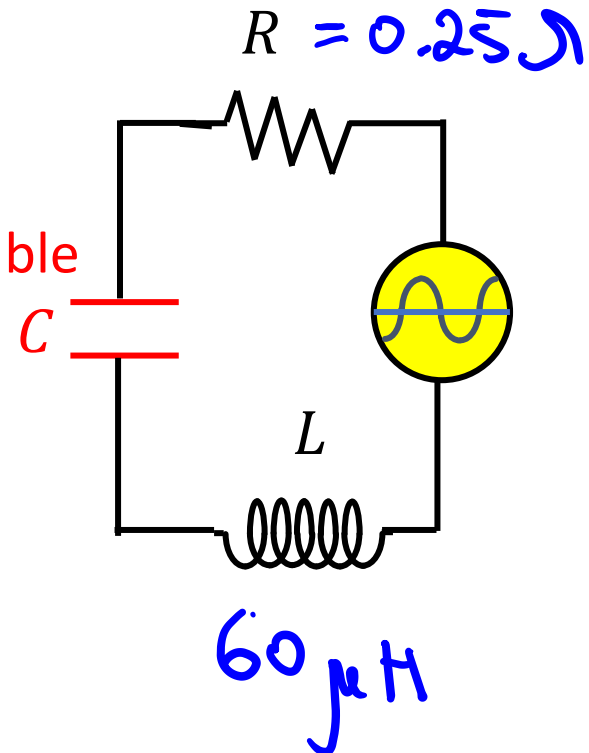


Application of resonance in AC circuits

Q: An AM radio station picks up a 1 MHz signal with a peak voltage of 5 mV. The tuning circuit consists of a 60 μH inductor in series with a variable capacitor C. The circuit has a small resistance of 0.25 Ω .



What is the peak current through this circuit on resonance? Pick the closest answer.

$$\bullet \quad I_{max} = \frac{V_{max}}{R} = \frac{5 \text{ mV}}{0.25 \Omega} = 0.02 \text{ A} = 20 \text{ mA}$$

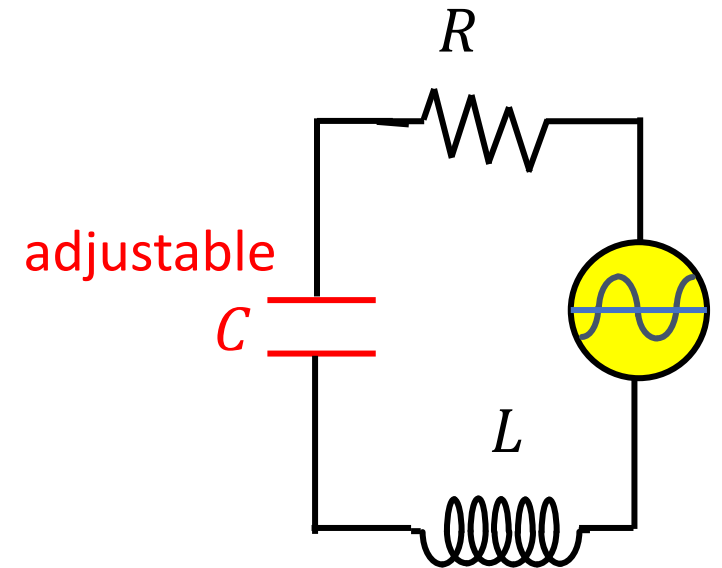- A. 1 mA
- ☒ B. 20 mA
- C. 50 mA
- D. 100 mA
- E. 350 mA



AC RLC series circuit: Summary

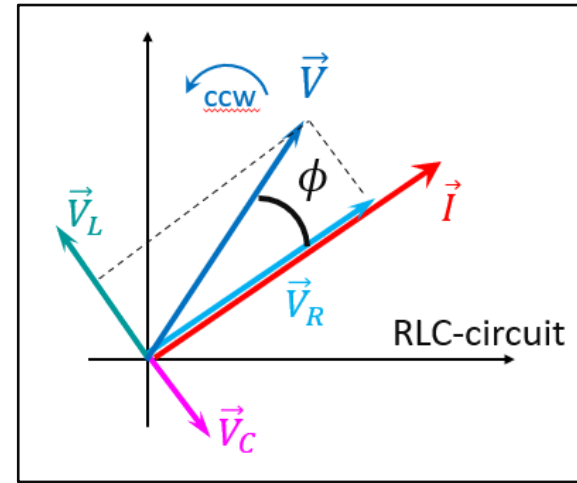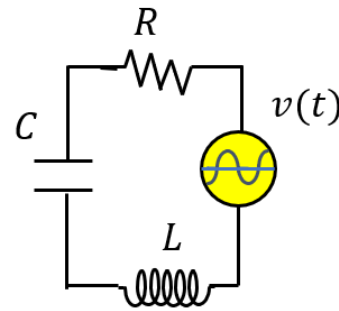


$$X_R = R$$

$$X_L = \omega L$$

$$X_C = 1/\omega C$$

$$V_{max} = I_{max} Z$$


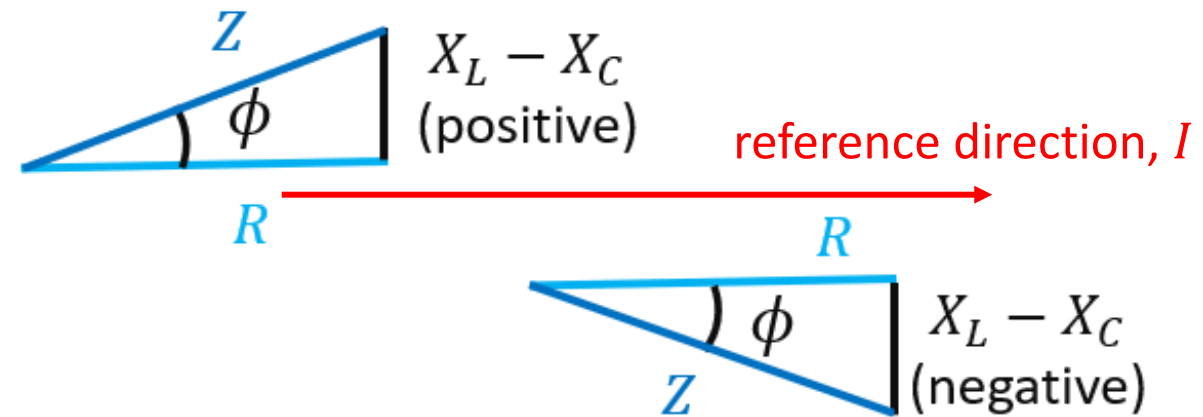
- Compute X_L, X_C
- Set up impedance triangle
 - Find the impedance Z
 - Find the phase shift ϕ between V and I
- Relations between voltages and current:
 - $V_{max} = I_{max} Z$
 - $V_R = I_{max} R = V_{max} \frac{R}{Z}$
 - $V_L = I_{max} X_L = V_{max} \frac{X_L}{Z}$
 - $V_C = I_{max} X_C = V_{max} \frac{X_C}{Z}$



- Note that the phasor diagram looks this way because the current I is common for all three elements (series)
- What if a circuit is parallel ??


AC RLC parallel circuit

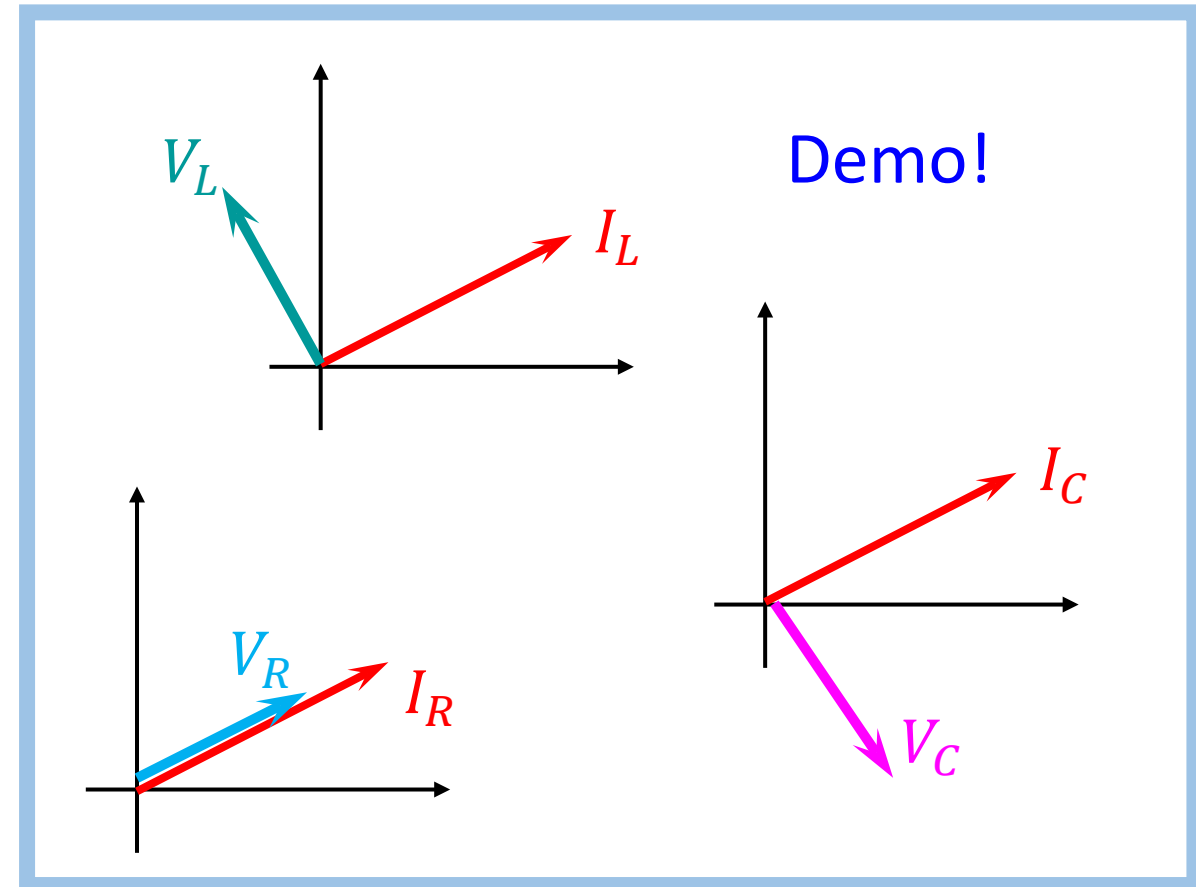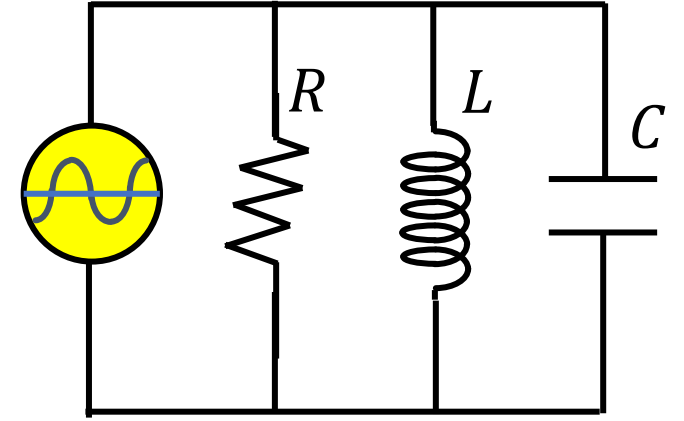- Now **voltage** across each parallel element is the same!
- **Series**: $v(t) = v_R(t) + v_L(t) + v_C(t)$ – hence we were adding up **voltages** phase shifted with respect to **common current**.
- **Parallel**: $i(t) = i_R(t) + i_L(t) + i_C(t)$ – hence we will be adding up **currents** phase shifted with respect to **common voltage**!
- Q: What the outcome would be?




AC RLC parallel circuit

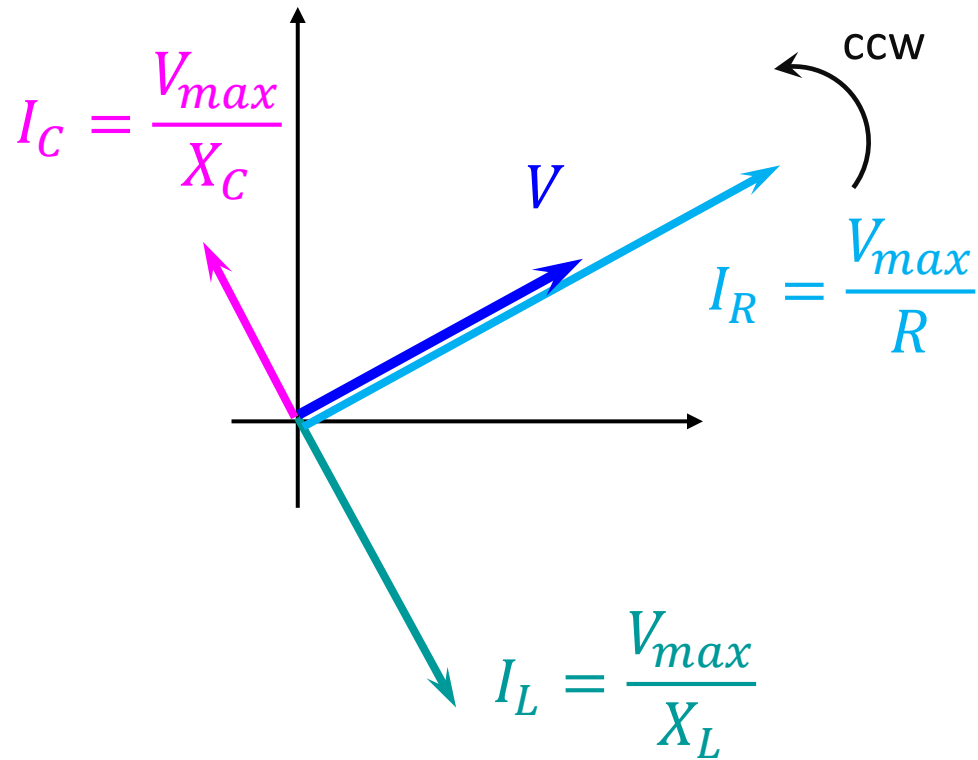
- Now let's combine the elementary phasor pairs, taking into account that they have common voltage (same magnitude and direction of \vec{V}):


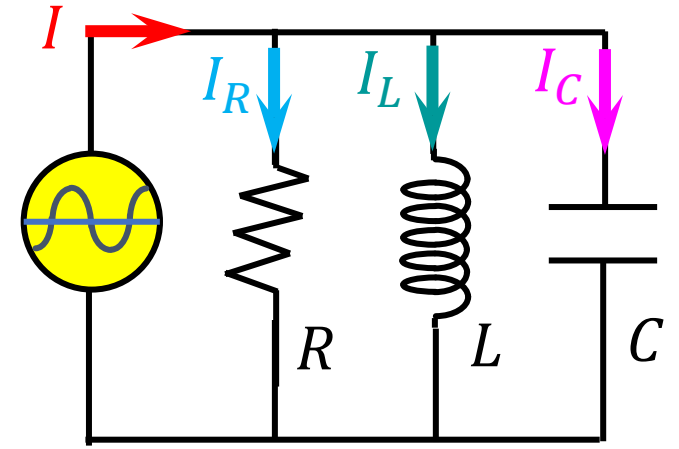
$$\vec{I} = \vec{I}_R + \vec{I}_L + \vec{I}_C$$



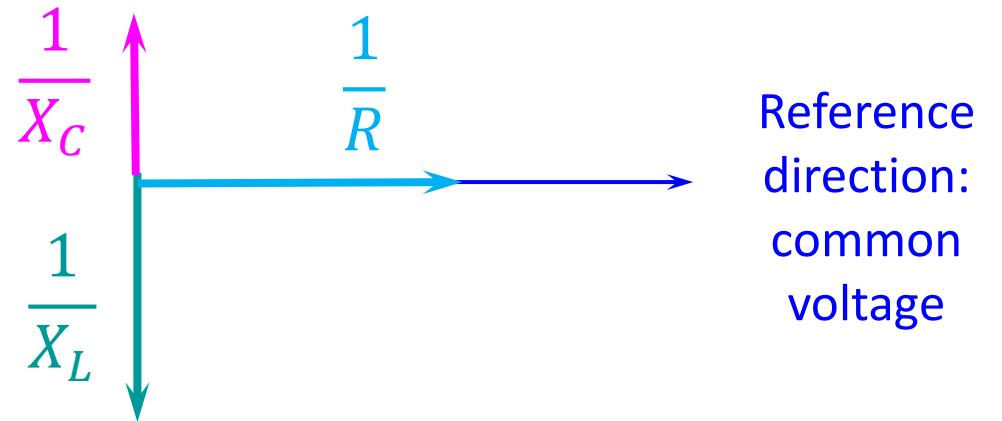- Rescale (divide by common V_{max}), rotate:



- Build the impedance triangle from reciprocal resistances!